

Name: SOLUTIONS


50 points total

EE 473

Quiz 1


Winter 2022

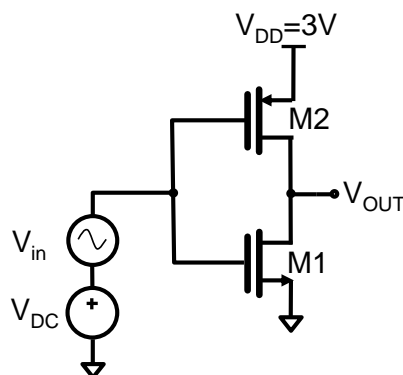- 1) Assume that M1 and M2 are in the saturation region and that V_{DC} is set to produce a DC V_{OUT} which is optimal for maximum headroom and output voltage swing. Also, assume that the drain currents of M1 and M2 are $I_D = 0.5\text{mA}$ (Total: 25 points)
 Device characteristics: $\mu_n C_{ox} = 4\text{mA/V}^2$, $\mu_p C_{ox} = 2\text{mA/V}^2$
 $(W/L)_{M1} = (10\mu\text{m}/0.5\mu\text{m})$, and $(W/L)_{M2} = (20\mu\text{m}/0.5\mu\text{m})$, $\lambda_p = \lambda_n = 0.1\text{V}^{-1}$ and $V_{THn} = 0.7\text{V}$ and $V_{THp} = 0.8\text{V}$.



- a) What is the small-signal gain $A_v = \frac{V_{OUT}}{V_{in}}$? (15 points)
 b) What is the optimal DC value of V_{OUT} to produce a maximum peak-to-peak output swing? This question is *not* asking you to compute V_{OUT} DC using the drain current equations for M1 and M2, but rather find the optimal V_{OUT} DC given the $(V_{GS} - V_{TH})$ of M1 and M2. (5 points) What is the corresponding peak output swing? (5 points)

PART a) DRAW SMALL-SIGNAL CIRCUIT.

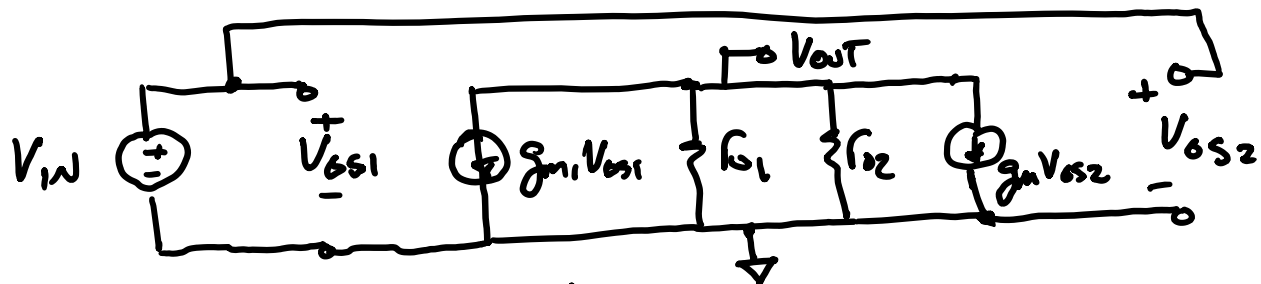

$$V_{GS1} = V_{GS2} = V_{in}$$

$$G_m = g_{m1} + g_{m2}$$

$$A_v = -(g_{m1} + g_{m2}) \cdot (r_{o1} // r_{o2})$$

$$= -(g_{m1} + g_{m2}) \cdot \left(\frac{r_{o1} \cdot r_{o2}}{r_{o1} + r_{o2}} \right)$$

$$= - \left(\frac{2I_{D1}}{(V_{GS} - V_{TH})_1} + \frac{2I_{D2}}{(V_{GS} - V_{TH})_2} \right) \cdot \frac{\frac{1}{\lambda I_{D1}} \cdot \frac{1}{\lambda I_{D2}}}{\frac{1}{\lambda I_{D1}} + \frac{1}{\lambda I_{D2}}}$$

$$I_{D1} = I_{D2} = 0.5 \text{ mA} \quad \lambda_n = \lambda_p = \lambda = 0.1$$

$$A_v = - 2I_{D0} \left(\frac{1}{(V_{GS} - V_{TH})_1} + \frac{1}{(V_{GS} - V_{TH})_2} \right) \cdot \frac{\frac{1}{\lambda I_{D0}}}{1+1}$$

$$= - \left(\frac{1}{(V_{GS} - V_{TH})_1} + \frac{1}{(V_{GS} - V_{TH})_2} \right) \cdot \frac{1}{\lambda}$$

NEED TO FIND $(V_{GS} - V_{TH})_1$ & $(V_{GS} - V_{TH})_2$. BOTH ALSO NEEDED FOR PART "B".



$$(V_{GS} - V_{TH})_1 = \sqrt{\frac{2I_{D0}}{\mu_n C_{ox} W/L}} = \sqrt{\frac{2 \cdot 0.5 \text{ mA}}{4 \text{ mA/V}^2 \left(\frac{10}{0.5} \right)}} = 111 \text{ mV}$$

$$(V_{GS} - V_{TH})_2 = \sqrt{\frac{2 \cdot 0.5 \text{ mA}}{2 \text{ mA/V}^2 \left(\frac{20}{0.5} \right)}} = 111 \text{ mV}$$

$$\therefore A_v = - \left(\frac{2}{111 \text{ mV}} \right) \frac{1}{0.1 \text{ V}^{-1}} = -180 \text{ V/V}$$

$$\boxed{A_v = -180 \text{ V/V}}$$

(b)

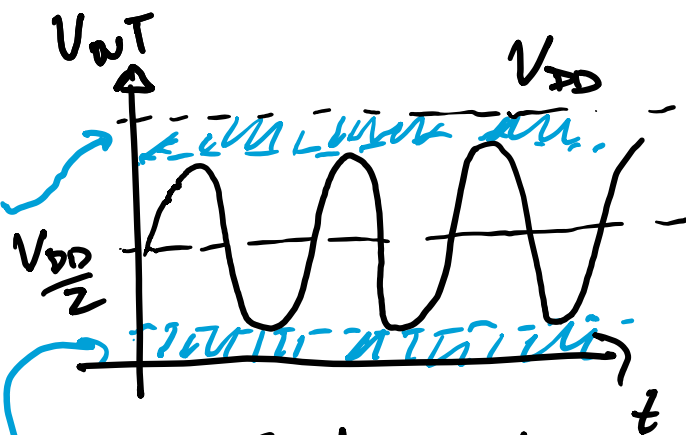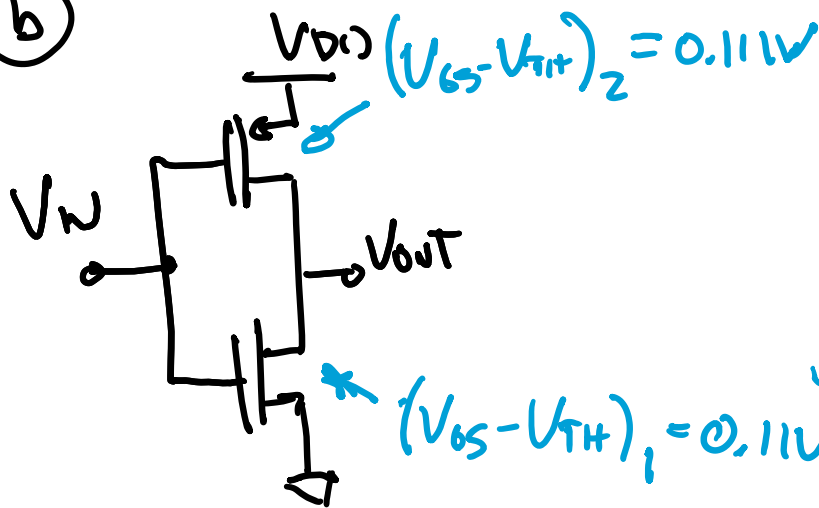


- BECAUSE $V_{DSAT1} < V_{DSAT2}$, OPTIMAL $V_{OUT DC} = V_{DD}/2$
- $V_{PK-PK MAX} = V_{DD} - 2V_{DSAT}$
 $= 3V - 2(0.11V)$

$$V_{PK-PK MAX} = 2.778V$$

- 2) For the below single-transistor amplifier, both an ideal DC current source and ideal AC current are applied to the input. It is fair to assume M_1 is in the saturation region and behaves like a "square law" device. Find the DC value of V_{OUT} (5 points) – note: ignore the body effect ($\lambda=0$) to make the calculation of the DC bias easier. Next, draw the small signal circuit for this amplifier and derive an expression for the small-signal AC transresistance (v_{out}/i_{in}), state any assumptions made to get your answer. Lastly, compute the value of the transresistance. (20 points) Note: for the AC-SS analysis you cannot ignore the body effect – e.g. $\lambda=0.01V^{-1}$
- Device characteristics: $\mu_n C_{ox} = 5mA/V^2$, $(W/L)_{M1} = (10\mu m/1\mu m)$, $\lambda=0.01V^{-1}$ and $V_t=0.7V$.


TRANSRESISTANCE v_{out}/i_{in}

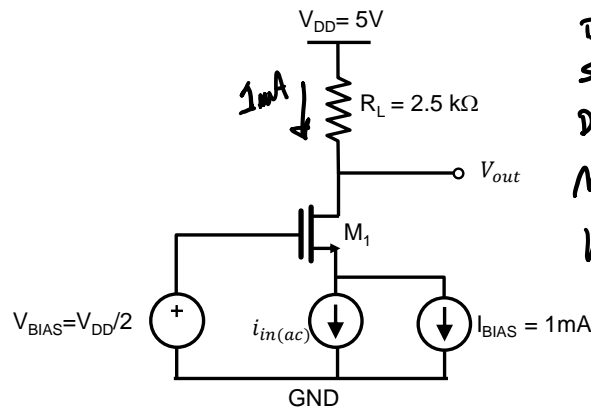

DC VALUE 0 OUT

DC CURRENT AT THE SOURCE IS 1mA. \therefore DC DRAW CURRENT OF M_1 IS 1mA.
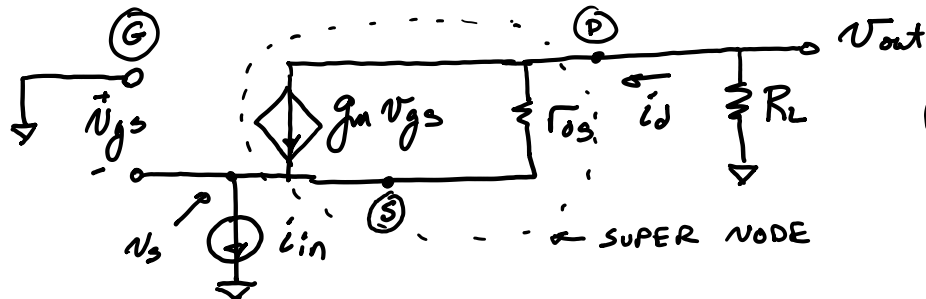
$$V_{OUT} = 5V - 1mA \cdot 2.5k\Omega = 2.5V$$




$$\begin{aligned} r_{ds} &= \frac{1}{2I_D} \\ &= \frac{1}{0.01 \cdot 1 \times 10^{-3}} \\ &= \frac{1}{1 \times 10^{-5}} = 100k\Omega \end{aligned}$$

VERY LARGE IGNORE

THIS PROBLEM CAN BE SOLVED A NUMBER OF WAYS. HOWEVER, YOU COULD REALIZE THAT WHAT CURRENT GOES IN THE SOURCE COMES OUT THE DRAIN. OR, THE g_m & r_{ds} ELEMENTS ARE IN A SUPER NODE...

$$i_d = i_{in}$$
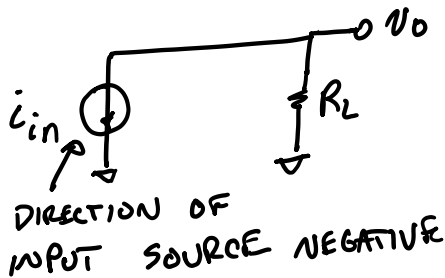
$$v_o = -(-i_{in}) \cdot R_L = i_{in} R_L$$



$$\frac{v_o}{i_{in}} = R_L = 2.5k\Omega$$

IF YOU DID NOT SEE THE SUPER NODE, A HARDER WAY TO DO THIS IS WRITE TWO KCL EQNS @ V_s & V_o

KCL @ (SOURCE)

$$V_{gs} = -V_s$$

$$i_{in} - g_m V_s + \frac{V_s - V_o}{r_{ds}} = 0$$

SOLVE FOR V_s

$$\frac{V_s}{r_{ds}} - g_m V_s = \frac{V_o}{r_{ds}} - i_{in}$$

$$V_s \left(\frac{1}{r_{ds}} - g_m \right) = \frac{V_o}{r_{ds}} - i_{in}$$

$$V_s = \frac{\frac{V_o}{r_{ds}} - i_{in}}{\left(\frac{1}{r_{ds}} - g_m \right)}$$

$$\frac{1}{r_{ds}} \ll g_m$$

$$V_s = \frac{\frac{V_o}{r_{ds}} - i_{in}}{-g_m}$$

$$V_s = \frac{i_{in} - \frac{V_o}{r_{ds}}}{g_m} \quad (1)$$

KCL @ V_o (DRAIN)

$$g_m \cdot (-V_s) + \frac{V_o - V_s}{r_{ds}} + \frac{V_o}{R_L} = 0$$

$$-g_m V_s + \frac{V_o}{r_{ds}} - \frac{V_s}{r_{ds}} + \frac{V_o}{R_L} = 0$$

SUB (1)

$$-g_m \left(\frac{i_{in} - \frac{V_o}{r_{ds}}}{g_m} \right) + \frac{V_o}{r_{ds}} - \frac{\left(i_{in} - \frac{V_o}{r_{ds}} \right)}{g_m r_{ds}} + \frac{V_o}{R_L} = 0$$

$$i_{in} - \cancel{\frac{V_o}{r_{ds}}} + \cancel{\frac{V_o}{r_{ds}}} - \frac{i_{in}}{g_m r_{ds}} - \cancel{\frac{V_o}{g_m r_{ds} \cdot r_{ds}}} + \frac{V_o}{R_L} = 0$$

IGNORE

$$\frac{i_{in}}{g_m r_{ds}} \ll i_{in} \quad \frac{V_o}{g_m r_{ds}^2} \ll \frac{V_o}{R_L}$$

$$i_{in} = -\frac{V_o}{R_L} \quad \text{DIRECTION OF } i_{in} \text{ IS NEGATIVE } \therefore$$

$$\boxed{\frac{V_o}{i_{in}} = R_L}$$

SAME AVG AS BEFORE.