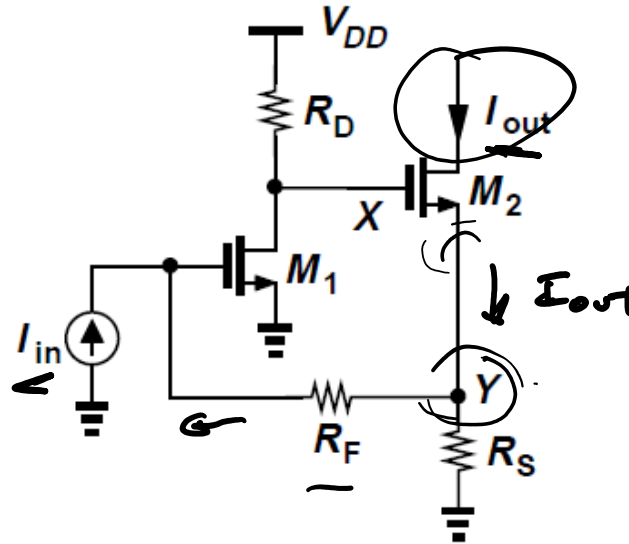


Lecture #23, March 4th, 2022



- Will focus on 10 (Stability and Compensation).
- Homework #4 due next Monday – don't wait until the day before to start the homework.
- Project 2 due this Saturday March 5th, at 11:59pm
- Today
 - Finish Feedback Basics
 - Begin Stability and Compensation


Current-Current Feedback: Example



- Above figure shows an example of current-current feedback
- Since the source and drain currents of M_1 are equal (at low frequencies), resistor R_S is inserted in the source network to monitor the output current
- Resistor R_F senses the output voltage and returns a current to the input

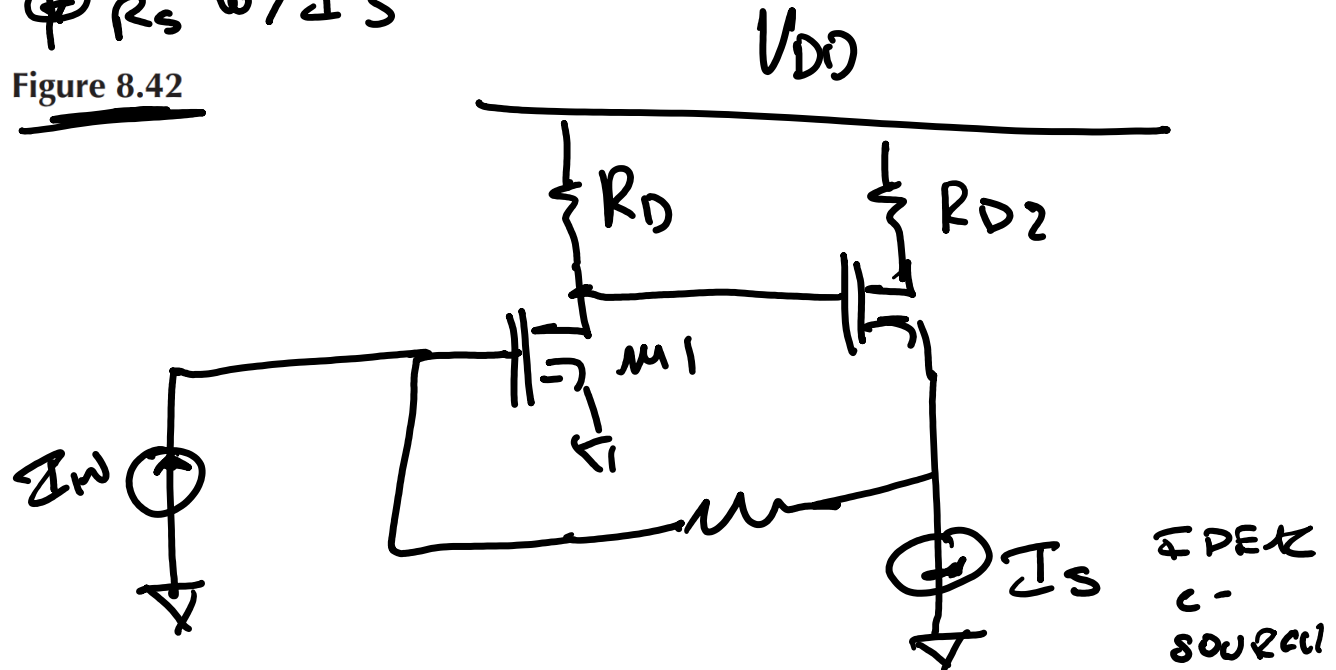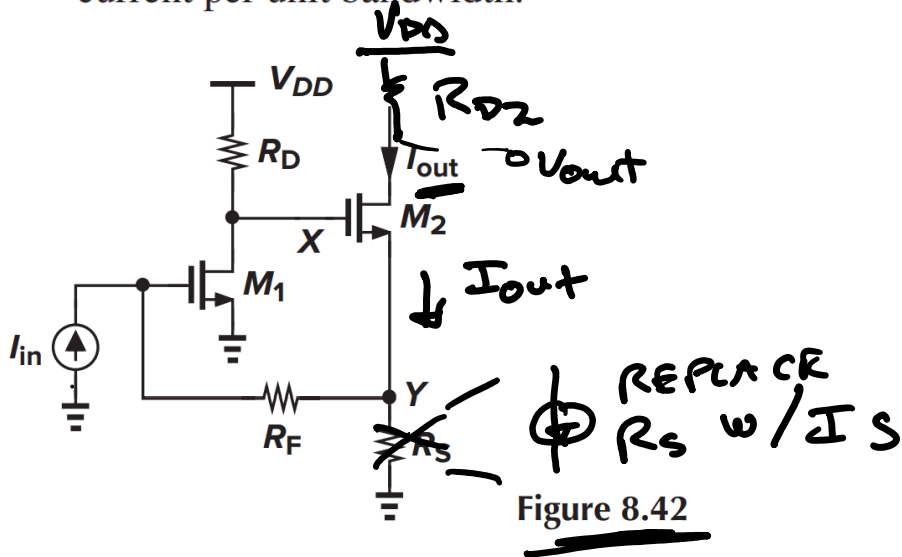- 8.7. The circuit of Fig. 8.42 can operate as a transimpedance amplifier if I_{out} flows through a resistor, R_{D2} , connected to V_{DD} , producing an output voltage. Replacing R_S with an ideal current source and assuming that $\lambda = \gamma = 0$, calculate the transimpedance of the resulting circuit. Also, calculate the input-referred noise current per unit bandwidth.



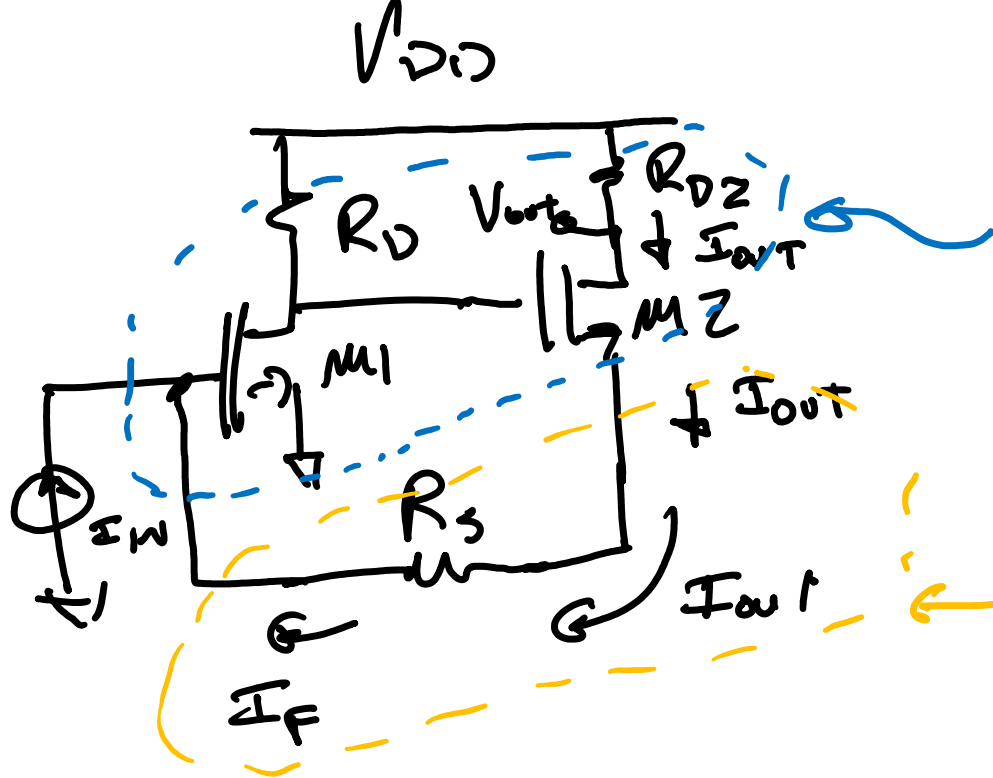

FORWARD
AMP A_I (CURRENT
AMP)

FEED BACK

$$\beta = \frac{I_F}{I_{out}}$$


$$I_F = I_{outT} \Rightarrow \beta = 1$$

CLOSED-LOOP GAIN $\frac{I_{out}}{I_{in}} \approx \frac{1}{\beta} \approx 1$



TRANSIMPEDANCE = $\frac{V_{out}}{I_{in}} = - \underbrace{\frac{I_{out}}{I_{in}}}_{1} \cdot R_{D2}$

$$\frac{V_{out}}{I_{in}} (R) = -R_{D2}$$

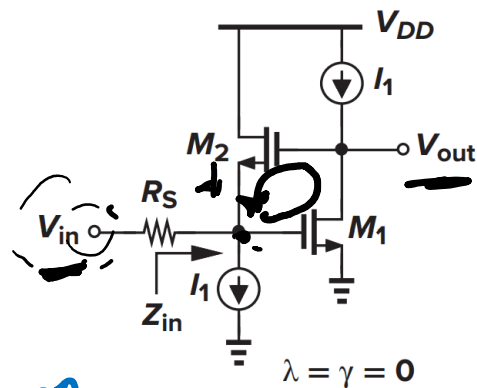8.10. Using feedback techniques, calculate the input and output impedance and voltage gain of each circuit in Fig. 8.95.



(a)

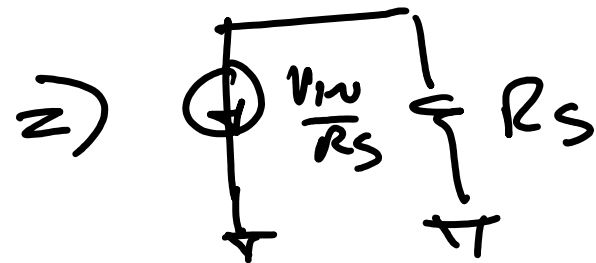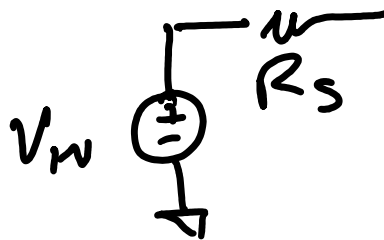


NORTON, EQ.

COMMON
DRAIN

$$A_v, \text{ closed } = \frac{A}{1 + A\beta}$$

$$V_{DD} = (95 \text{ GND})$$

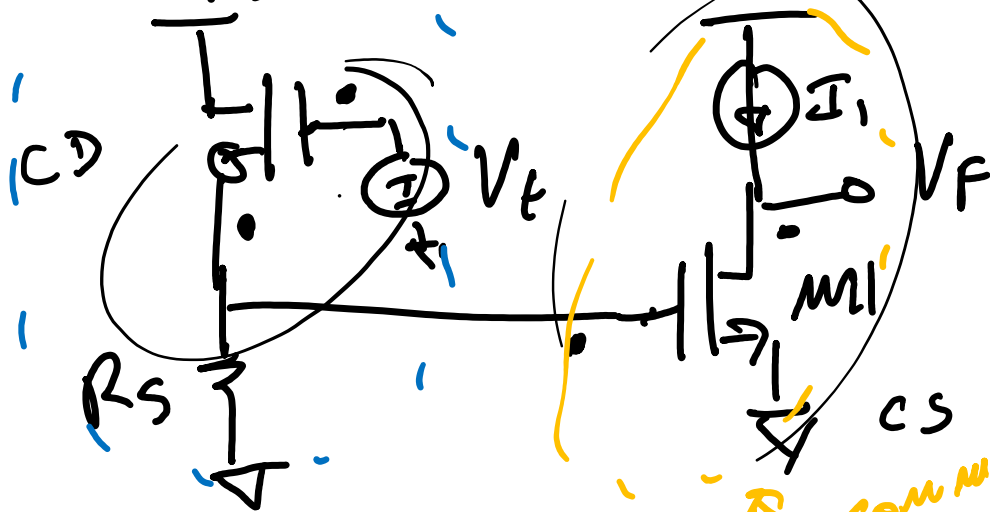

COMMON
SOURCE

$$\begin{aligned} A\beta &= A_{cd} \cdot A_{cs} \\ &= (1) \cdot (-g_{m1} \cdot r_{o1}) \\ &= -g_{m1} \cdot r_{o1} \end{aligned}$$