

Name: SOLUTIONS


50 points total

EE 473

Quiz 3

Winter 2022

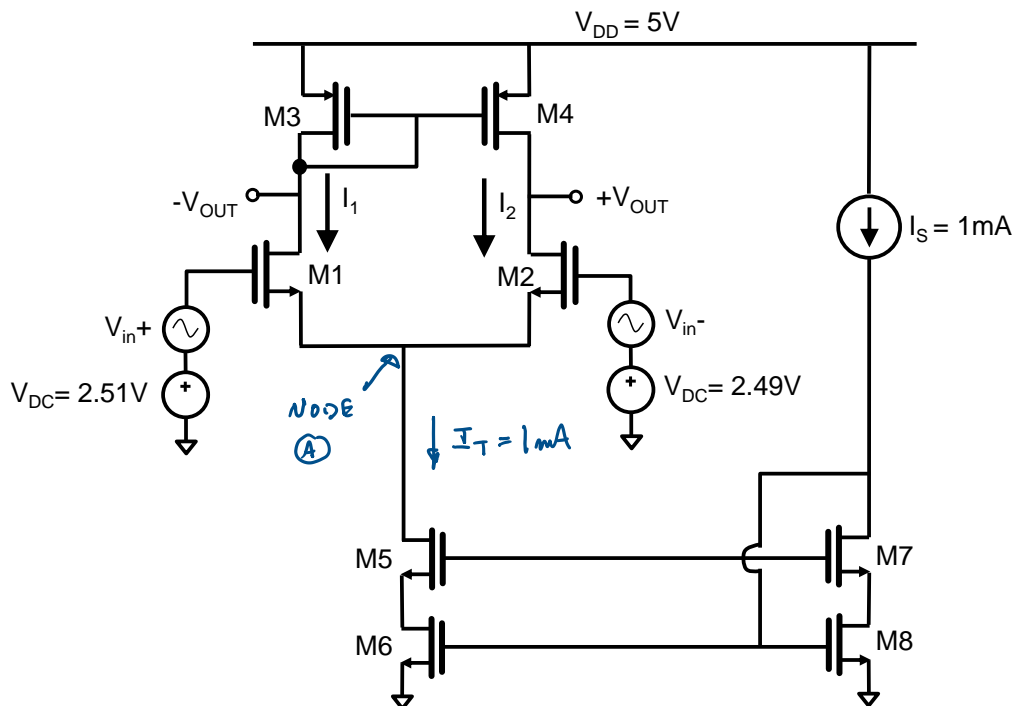- 1) a) For the below amplifier, assume all devices are in the saturation region. Find the DC current  $I_1$  and  $I_2$ . (10 points) Assume all devices in the saturation region and all device sizes are  $\frac{10\mu}{1\mu}$ . **Note:** there is a DC offset at the opamp input. Use the following parameters for the entire quiz,  $\mu_n C_{ox} = 2\text{mA/V}^2$ ,  $\mu_p C_{ox} = 1\text{mA/V}^2$ ,  $V_{TH(NMOS)} = 0.7\text{V}$  and  $V_{TH(PMOS)} = 0.8\text{V}$ ,  $\lambda_n = 0.1$ , and  $\lambda_p = 0.1$ . Ignore the body effect ( $\gamma = 0$ ).



KCL @ NODE A

$$I_T = I_1 + I_2 \quad (1)$$

FIND THE NOMINAL  $V_{GS}$  w/ NO INPUT OFFSET.

$$I_{D1} = 0.5\text{mA} \quad I_{D2} = 0.5\text{mA}$$

$$I_D = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)}{2} (V_{GS} - V_{thn})^2$$

$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{thn} = \underline{\underline{0.924\text{V}}}$$

w/ THE INPUT OFFSET

$$V_{GS1} = 0.924 + 0.01\text{V}$$

$$V_{GS2} = 0.925 - 0.01\text{V}$$

$$I_{D1} = \frac{2 \text{mA/V}^2 \left(\frac{10}{1}\right)}{2} (0.934 - 0.7)^2$$

$\uparrow$   $V_{GS} + 0.01 \text{V}$

$$= 0.55 \text{mA}$$

$$I_{D2} = \frac{2 \text{mA/V}^2 \left(\frac{10}{1}\right)}{2} (0.914 - 0.7)^2$$

$\uparrow$   $V_{GS} - 0.1 \text{V}$

$$= 0.45 \text{mA}$$

$I_{D1} = 0.55 \text{mA}$
$I_{D2} = 0.45 \text{mA}$


NEEDED  
FOR  
PART B)

$$\left\{ \begin{aligned} g_{m1} &= \frac{2 I_{D1}}{(V_{GS1} - V_{th})} = \frac{2 \cdot 0.55 \text{mA}}{(0.934 - 0.7)} = 4.7 \text{mA/V} \\ g_{m2} &= \frac{2 I_{D2}}{(V_{GS2} - V_{th})} = \frac{2 \cdot 0.45 \text{mA}}{(0.914 - 0.7)} = \underline{\underline{4.2 \frac{\text{mA}}{\text{V}}}} \end{aligned} \right.$$

b) Find the AC small-signal gain of the op amp in part a) (25 points)

TWO UNEQUAL PATHS

PATH 1

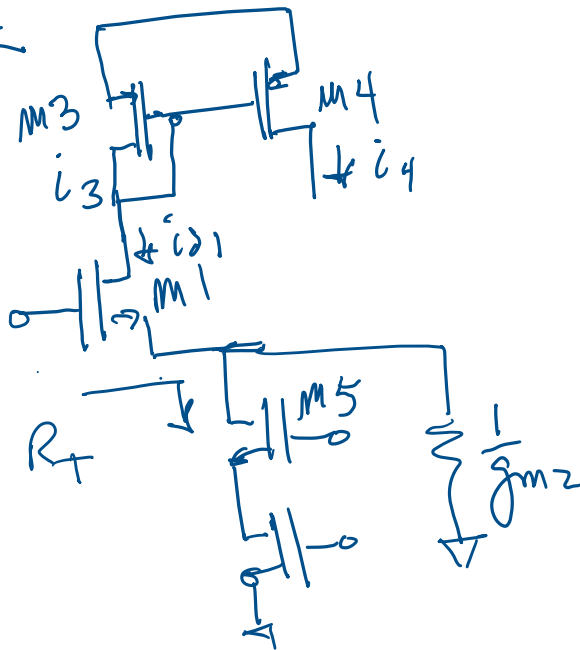

$$\underline{i_3 = i_4 = i_{d1}}$$

$$i_{d1} = \frac{g_{m1} v_{in}}{1 + g_{m1} \frac{1}{g_{m2}}}$$

ASSUME

$$\frac{1}{g_{m2}} \ll R_T$$

$$G_{m1} = \frac{g_{m1}}{1 + 2}$$

$$g_{m1} \approx g_{m2}$$


$$A_{v1} = +G_{m1} \cdot (r_{o2} \parallel r_{o4})$$

$$= \frac{4.7 \text{ mA/V}}{2} \cdot \left( \frac{1}{(0.1 \cdot I_{D2}) \cdot 2} \right)$$

$$\uparrow 0.45 \text{ mA}$$

$$\approx 26.1 \text{ V/V}$$

PATH 2

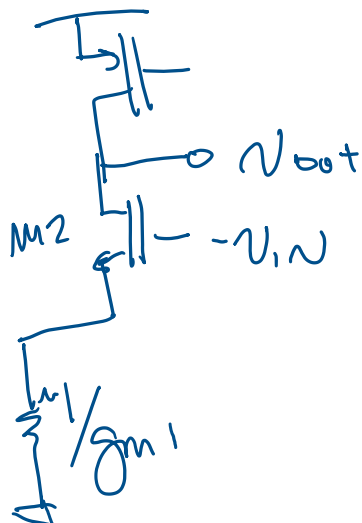


$$A_{v2} = - \left( \frac{-g_{m2} \cdot r_{o2} \parallel r_{o4}}{2} \right)$$

$$= \frac{4.2 \text{ mA}}{2} \left( \frac{1}{(0.1)(0.45 \text{ mA}) \cdot 2} \right)$$

$$= +23 \text{ V/V}$$

$$A = A_{v1} + A_{v2} \approx 49.4 \text{ V/V} \approx 50 \text{ V/V}$$

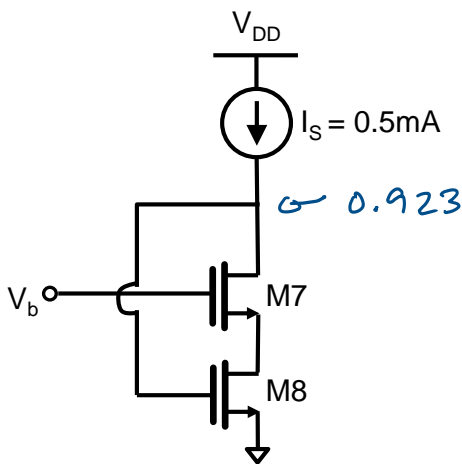- 2) Find the range of acceptable values for the bias voltage,  $V_b$  in the below circuit.  
Assume all device sizes are  $\frac{10\mu}{1\mu}$ . (15 points)



FIRST FIND  $V_{GS8}$

$$V_{GS8} = \sqrt{\frac{2 \cdot 0.5 \text{mA}}{2 \text{mA/V} \cdot \left(\frac{10}{1}\right)}} + V_{th}$$


$$\geq 0.923 \text{ V}$$

$$(V_{GS8} - V_{th}) = V_{GS7} - V_{th} = \underline{0.223 \text{ V}}$$

$$V_{DSAT7} = V_{DSAT8} = 0.223 \text{ V}$$


- $V_b$  IS LIMITED ON THE HIGH END BY PUSHING M7 INTO TRIODE

M7 IS ON THE EDGE OF TRIODE WHEN

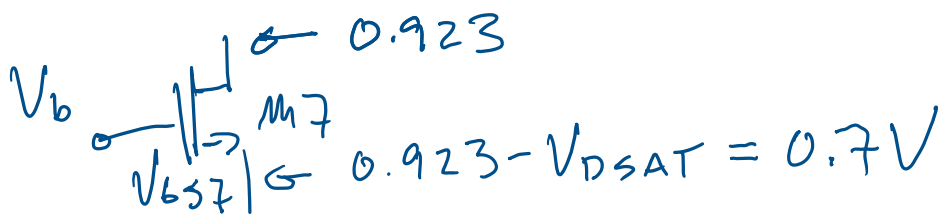

$$V_{b(HIGH)} = 0.7 + V_{GS7} = 0.7 + 0.923 \text{ V} \\ = \underline{\underline{1.623 \text{ V}}}$$

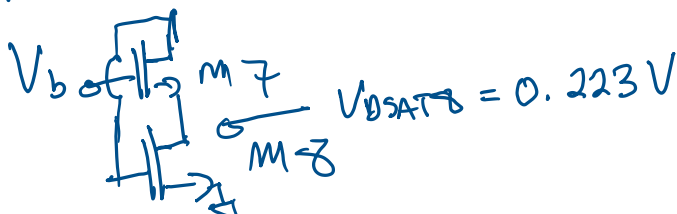- $V_b$  IS LIMITED ON THE LOW END BY KEEPING M8 IN SATURATION,



$$V_{b(LOW)} = V_{DSAT8} + V_{GS7} \\ = 0.223 + 0.923 \text{ V} \\ = 1.123 \text{ V}$$

$$\underline{1.123 \text{ V} \leq V_b \leq 1.623 \text{ V}}$$