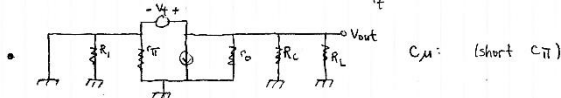


• C_{π} : $V_t = 0$ (short C_{μ})

$$R = \frac{V_t}{i_t} = 0 \Rightarrow R_{C_{\pi}} = 0$$




General form: $\frac{V_t}{i_t} = R_1 + R_2 + g_m R_1 R_2$


$$R_{C_{\mu}} = R_1 // r_{\pi} + r_o // R_C // R_L + g_m (R_1 // r_{\pi}) (r_o // R_C // R_L)$$

$$2\tau_{FH} = \omega_H = \frac{1}{0.6\pi + R_{C_{\mu}} C_{\mu}}$$

Short Circuit Time Constant C-E

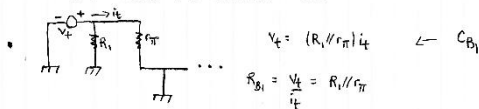

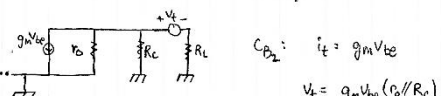$R_{B1} = \frac{V_t}{i_t} = R_1 // r_{\pi}$



$V_t = g_m V_{be} (r_o // R_C)$

$R_{B2} = \frac{V_t}{i_t} = (r_o // R_C) + R_L$

$\omega_L = \frac{1}{R_{B1} C_1} + \frac{1}{R_{B2} C_2}$

Part 2:


Find the transfer function of the circuit below in terms of k , C_1 , C_2 , R_1 , and R_2 and answer questions (a) through (c)

a) Find the transfer function of the circuit below.

b) What type of filter is this?

c) What is the DC gain of the step response for this circuit? $\text{step} = \frac{1}{s}$, $\text{gain} = \frac{1}{s} \cdot \frac{V_{out}}{V_{in}} \bigg|_{s=0}$

$-V_B/K = V_0$
 $V_B = -V_0/K$

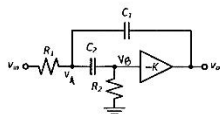

a) $\frac{V_0 - V_{in}}{R_1} + \frac{V_0 - V_0}{1/sC_1} + \frac{V_0 + V_0/K}{1/sC_2} = V_A \left[\frac{1}{R_1} + sC_1 + sC_2 \right] = \frac{V_0}{R_1} - V_0 \left[sC_1 + \frac{sC_2}{K} \right]$

$\frac{-V_0/K}{R_2} + \frac{V_0 - V_A}{1/sC_2} = 0 \Rightarrow \frac{V_0}{K} \left[\frac{1}{R_2} + sC_2 \right] = V_A \left[\frac{1}{R_2} + sC_2 \right]$

$V_A \left[1 + sC_2 R_1 + sC_2 R_2 \right] - V_0 \left[sC_2 R_1 + \frac{sC_2 R_2}{K} \right] = V_{in}$

$\frac{V_0}{K} \left[\frac{1 + sC_2 R_2}{sR_2 C_2} \right] \left[1 + sC_2 R_1 + sC_2 R_2 \right] - \frac{V_0}{K} \left[sC_2 R_1 + \frac{sC_2 R_2}{K} \right] = V_{in}$

$\frac{V_0}{K} \left[1 + sC_2 R_1 + sC_2 R_2 + s^2 C_2^2 R_1 R_2 + s^2 C_2^2 R_1 R_2 K - s^2 C_2^2 R_1 R_2 K - s^2 C_2^2 R_1 R_2 K \right] = V_{in}$


$V_0 = V_{in} \frac{sK R_2 C_2}{1 + s(C_1 R_1 + C_2 R_1 + C_2 R_2) + s^2 C_1 C_2 R_1 R_2 (1-K)}$

$\frac{V_0}{V_{in}} = \frac{sK R_2 C_2}{1 + s(C_1 R_1 + C_2 R_1 + C_2 R_2) + s^2 C_1 C_2 R_1 R_2 (1-K)}$

Find the current I_D and voltage V_D if W/L of both transistors is 20/1. Assume $V_{DD} = -0.75V$, $\lambda = 0$, and $\mu_p C_{ox} = 40 \mu A/V^2$, $V_{th} = +0.75V$, and $\mu_n C_{ox} = 100 \mu A/V^2$

$K_p = 80 \mu A/V^2$

$K_n = 200 \mu A/V^2$

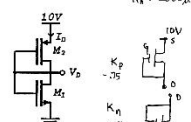

Assume in saturation:

$I_D = \frac{1}{2} (100 \cdot 10^{-6}) (V_{GS} - 0.75)^2 = \frac{1}{2} (200 \cdot 10^{-6}) (V_{GS} - 0.75)^2$

$V_{SG} = V_G - V_S = 10V - V_0$

$V_{GS} = V_G - V_S = V_0$

$V_0 = 4.04V$
 $I_D = 10.8 \mu A$

$V_{DD} = 1.29V$

$V_{DD} = 5.21V$


$V_{GS} = V_0 = 4.04V$

$V_{GS} = 10 - 4.04 = 5.96V$

$V_{GS} > V_{th}$

$V_{GS} > V_{th}$

C-B

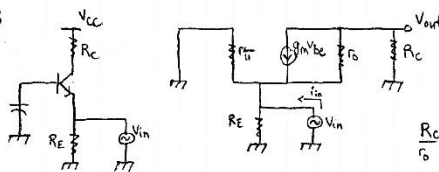

$V_{out} = -R_C (g_m V_{be} + \frac{V_{out} - V_{in}}{r_o})$

$\frac{R_C}{r_o} V_{out} + V_{out} = R_C g_m V_{in} + \frac{R_C}{r_o} V_{in}$

$V_{out} \left[1 + \frac{R_C}{r_o} \right] = V_{in} \left[g_m R_C + \frac{R_C}{r_o} \right]$

$A_v = \frac{V_{out}}{V_{in}} = \frac{r_o g_m R_C + R_C}{r_o + R_C} = \frac{R_C [1 + g_m r_o]}{R_C + r_o}$

Input Resistance:


$i_{in} = \frac{V_{in}}{R_E} + \frac{V_{in}}{r_{\pi}} + \frac{V_{in} - V_{out}}{r_o} - g_m V_{be}$

$i_{in} = V_{in} \left[\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right] + \frac{V_{out}}{r_o}$

$i_{in} = V_{in} \left[\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + \frac{1}{g_m} \right]$

$R_{in} = \frac{V_{in}}{i_{in}} = R_E // r_{\pi} // \frac{1}{g_m} // r_o$

Output Resistance:

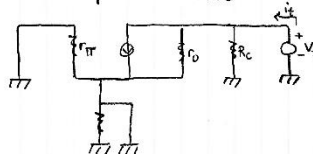

$i_t = g_m V_{be}$


$V_t = g_m V_{be} (r_o // R_C)$

$R_{out} = \frac{V_t}{i_t} = r_o // R_C$

(a) Find expressions for the voltage v_o in terms of R_L . Assume the op amp is ideal.

(b) What should be the value of R_L so that $v_o = -16V$?

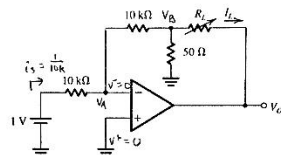(c) Now assume that the op-amp has an input offset voltage of v_{os} . Find the expressions for v_o in terms of v_{os} and R_L . Using R_L from part (b), what is the output offset voltage if $v_{os} = \pm 4mV$?



a.)

$\frac{V_0 - V_A}{10k} = \frac{1}{10k} \Rightarrow \frac{-V_B}{10k} = \frac{1}{10k} \Rightarrow V_B = -1V$

$\frac{V_0}{50} + \frac{V_B - V_0}{R_L} = 0$

$V_0 \left(\frac{1}{50} + \frac{1}{R_L} \right) = \frac{V_B}{R_L}$


$V_0 \left(\frac{R_L + 50}{50 R_L} \right) = \frac{V_B}{R_L}$

$V_0 = \frac{-R_L}{50} - 1$

b.) $-16 = \frac{-R_L}{50} - 1$

$R_L = 750 \Omega$

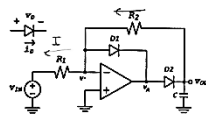Problem 3 (25 Points): Use the circuit below to answer the following questions. The op-amp is ideal. $2R_1 = R_2$.



a) Use ideal diode model and plot V_{out} vs. time for a square wave V_{in} (0 for $t < 0$, $-1V$ for $t > 0$, $0V$ for $t > 1$)

$t < 0$

$V_{in} = 0$

$V_{out} = 0$

$t > 0$

$V_{in} = -1V$

D_1 is ON, D_2 is OFF


$I = \frac{1}{R_1} = I_{D1}$

$V_{out} = \frac{R_2}{R_1} \times 1V = 2V$


depending on t_1 & time constant may or may not reach $2V$

$t_1 < t$

$V_{in} = 0$

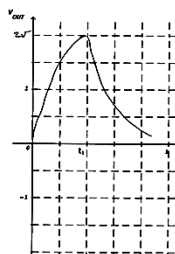

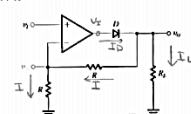Problem 3 (25 Points): For the circuit below, draw the output waveform for the input sinusoidal waveform with peak voltage of $2V$ and DC of $0V$. Assume the op-amp has a voltage gain of $10V/V$ and its output saturates at $\pm 15V$. Use constant voltage drop model for diode D with $V_{th} = 0.7V$.



V_{in} is positive

assume diode ON

$I_D = I + I_L$

$V_{in} = 10(V_{in} - V^-)$

$V_0 = V_{in} - 1V \Rightarrow V_{in} = V_0 + 1V$

$V_0 = 2R \times I = 2R \times \frac{V^-}{R} = 2V^-$

$V_0 + 1V = 10(V_{in} - V^-) \Rightarrow 2V^- + 1 = 10(V_{in} - V^-)$

$12V^- + 1 = 10V_{in} \Rightarrow V^- = \frac{10V_{in} - 1}{12}$

The current flow is positive

only if V^- is positive or $10V_{in} > 1$

or $V_{in} > 0.1V$

if V^- is negative: the current flow direction is shown on the left.


It can be seen that this violates KCL at node V_0

\Rightarrow diode turns off & V_{in} saturates to $-15V$

all currents become zero & $V_0 = 0$


Page 4 of 4

Short Circuit Time Constant (SCTC) C-C:

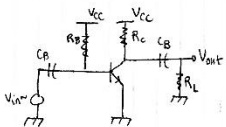


C-E

Midband gain:
(all caps are shorted)

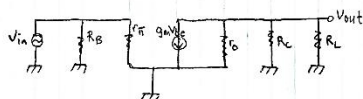


$$V_{in} = V_{be}$$
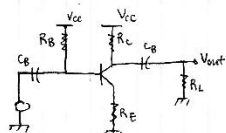
$$\frac{V_{out}}{V_{in}} = -g_m(R_C // R_L) \approx -g_m(R_C // R_L)$$



C-E with degeneration

Midband Gain

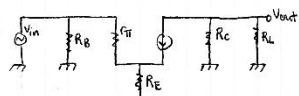


$$V_{in} = V_{be} + R_E(g_m V_{be} + \frac{V_{be}}{r_{\pi}})$$


$$V_{out} = -g_m(R_C // R_L)V_{be}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m(R_C // R_L)}{1 + g_m R_E}$$

Open Circuit Time Constant (OCTC) C-C:

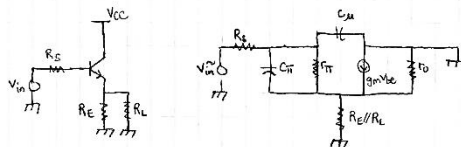

C_μ:

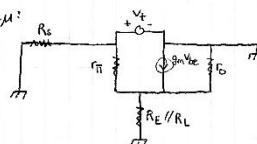

$$i_t = \frac{V_t}{r_{\pi}}$$

$$V_t = V_{be} + R_E'(g_m V_{be} + \frac{V_{be}}{r_{\pi}})$$


$$R_E' = R_E // R_L // r_o$$

$$R = \frac{V_t}{i_t} = r_{\pi} + R_E' + R_E' g_m r_{\pi} \approx r_{\pi} (1 + g_m R_E')$$

$$R_{C\mu} = R_S // R$$

$$R_{C\mu} = R_S // (r_{\pi} (1 + g_m R_E')) \approx R_S$$

C_π:

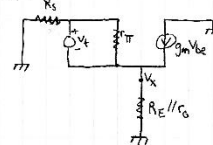

$$V_{be} = V_t$$

$$i_t = \frac{V_t}{r_{\pi}} + \frac{V_x + V_t}{R_S}$$

$$V_x = (R_E // r_o)(g_m V_t - \frac{V_x + V_t}{R_S})$$

$$i_t = V_t \left[\frac{1}{r_{\pi}} + \frac{1}{R_S} \right] + V_x \left[\frac{1}{R_S} \right]$$

$$V_x \left[\frac{1 + R_E // r_o}{R_S} \right] = [R_E // r_o] \left[g_m - \frac{1}{R_S} \right] V_t$$

$$i_t = \frac{V_t}{r_{\pi} // R_S} + \frac{[R_E // r_o] [g_m - 1/R_S]}{R_S + R_E // r_o} V_t$$


$$i_t = V_t \left[\frac{1}{r_{\pi} // R_S} + \frac{[R_E // r_o] [g_m - 1/R_S]}{R_S + R_E // r_o} \right]$$

$$R_{out} = \frac{1}{A}$$

$$W_H = \frac{1}{R_{out} C_{\mu} + R_{out} C_{\pi}}$$

Multi Stage Amplifiers


1. Simplifying Stages

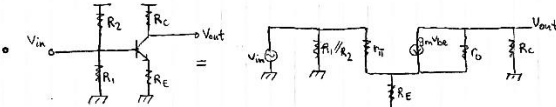

$$R_{in} = R_1 // R_2 // [r_{\pi} (1 + g_m R_E)]$$

$$R_{out} = R_C$$

$$G_m = \frac{i_{out}}{V_{in}} \bigg|_{V_{out}=0} = \frac{g_m V_{be}}{V_{be} + R_E (g_m V_{be} + \frac{V_{be}}{r_{\pi}})}$$

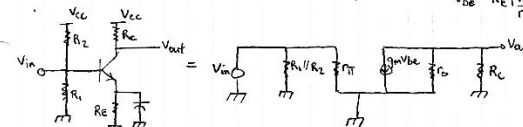


$$R_{in} = R_1 // R_2 // r_{\pi}$$


$$R_{out} = R_C$$

$$G_m = \frac{i_{out}}{V_{in}} \bigg|_{V_{out}=0} = \frac{g_m V_{be}}{V_{be}}$$

2. Multiple Stages in Cadence

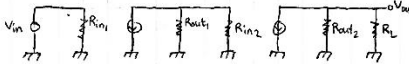
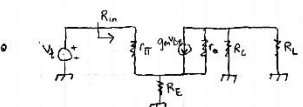
$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{in2}} \cdot \frac{V_{in2}}{V_{in1}} = -G_m (R_{out2} // R_L) + G_{m1} (R_{in2} // R_{out1})$$




C-E with degeneration

R_{in}: replace signal with test voltage
ignore any capacitors

$$i_t = \frac{V_{be}}{r_{\pi}}$$

$$V_t = V_{be} + R_E(g_m V_{be} + \frac{V_{be}}{r_{\pi}}) = V_{be} + R_E g_m V_{be} + R_E \frac{V_{be}}{r_{\pi}}$$
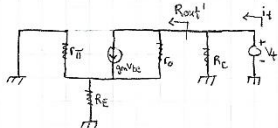
$$R_{in} = \frac{V_t}{i_t} = r_{\pi} + R_E + R_E g_m r_{\pi} \approx r_{\pi} (1 + g_m R_E)$$



C-E with degeneration

When finding R_{out}, ignore all input signals
ignore any capacitors

$$R_{out} = R_C // R_{out}'$$

$$i_t = g_m V_{be} + \frac{V_t - (-V_{be})}{r_o}$$

$$V_{be} = -(r_{\pi} // R_E) i_t \quad [\text{substitute}]$$


$$i_t = -g_m (r_o // R_E) i_t + \frac{V_t - (-r_{\pi} // R_E) i_t}{r_o}$$

$$V_t = i_t r_o + g_m (r_{\pi} // R_E) i_t r_o + (r_{\pi} // R_E) i_t$$

$$V_t = i_t [r_o + g_m (r_{\pi} // R_E) r_o + r_{\pi} // R_E]$$

$$R_{out} = \frac{V_t}{i_t} = r_o + g_m (r_{\pi} // R_E) r_o + r_{\pi} // R_E$$

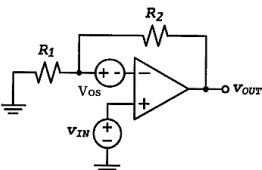
$$\text{if } R_E \ll r_{\pi} \Rightarrow R_{out} = r_o + g_m r_o R_E + R_E \approx r_o (1 + g_m R_E)$$




$$V_{out} = \frac{V_{in}}{R_1} \times R_2 + V_{in} + \frac{V_{OS}}{R_1} \times R_2 + V_{OS}$$

Summary

	C-E	C-E w/ degen.
Gain	$-g_m(R_C // R_L)$	$\frac{-g_m(R_C // R_L)}{1 + g_m R_E}$
R _{in}	$r_{\pi} // R_1 // R_2$	$r_{\pi} (1 + g_m R_E) // (R_1 // R_2)$
R _{out}	$R_C // r_o$	$R_C // r_o (1 + g_m R_E)$

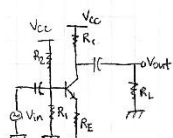

C-C

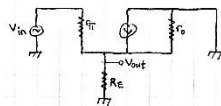

$$V_{be} = V_{in} - V_{out}$$

$$\text{KCL: } \frac{V_{in} - V_{out}}{r_{\pi}} + g_m (V_{in} - V_{out}) + \frac{0 - V_{out}}{r_o // R_E} = 0$$

$$V_{in} \left(\frac{1}{r_{\pi}} + g_m \right) = V_{out} \left(\frac{1}{r_{\pi}} + g_m + \frac{1}{R_E} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{g_m R_E}{1 + g_m R_E}$$