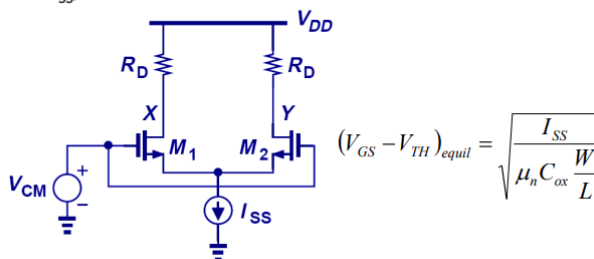


- 9.4. In the op amp of Fig. 9.21(b), $(W/L)_{1-8} = 100/0.5$, $I_{SS} = 1$ mA, and $V_{b1} = 1.7$ V. Assume that $\gamma = 0$.
- What is the maximum allowable input CM level?
 - What is V_X ?
 - What is the maximum allowable output swing if the gate of M_2 is connected to the output?
 - What is the acceptable range of V_{b2} ?

Reference: <https://inst.eecs.berkeley.edu/~ee105/sp08/lectures/lecture24.pdf>

Equilibrium Overdrive Voltage

- The **equilibrium overdrive voltage** is defined as $V_{GS} - V_{TH}$ when M_1 and M_2 each carry a current of $I_{SS}/2$.



Minimum CM Output Voltage

- In order to maintain M_1 and M_2 in saturation, the common-mode output voltage cannot fall below $V_{CM} - V_{TH}$.
- This value usually limits voltage gain.

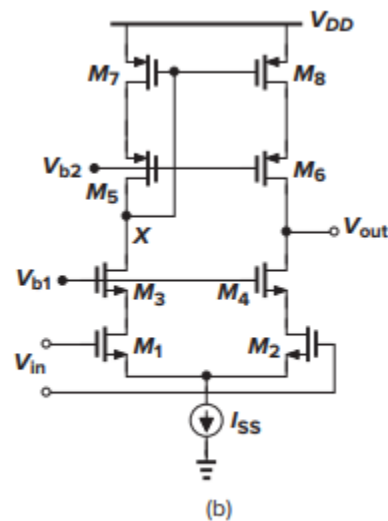
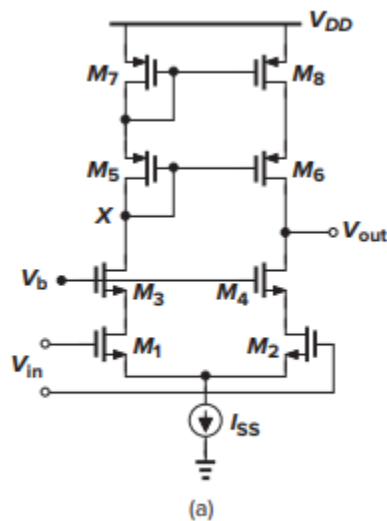
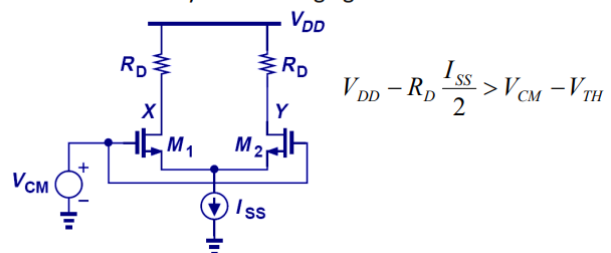


Figure 9.21 Cascode op amps with single-ended output.

9.4

Known

a) Max CM?

$$V_{CM, \max} - V_{th2} < V_{b1} - V_{gs4}$$

$$V_{CM, \max} < V_{b1} - V_{gs4} + V_{th2}$$

$$V_{gs4} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{thn} \quad \left| I_D = \frac{I_{SS}}{2} = 0.5 \text{ mA} \right.$$

$$V_{gs4} = \sqrt{\frac{2(0.5 \text{ mA})}{1.34 \text{ E-}4 (200)}} + 0.7$$

$$V_{gs4} = 0.193 + 0.7 = 0.893 \text{ V}$$

$$V_{CM, \max} < V_{b1} - V_{gs4} + V_{th2}$$

$$V_{CM, \max} < \overset{1.7}{0.893} - 0.893 + 0.7$$

$$V_{CM, \max} < 1.507 \text{ V}$$

$$\mu_n C_{ox} = 1.34 \text{ E-}4 \quad \mu_p C_{ox} = 3.83 \text{ E-}5 \quad \left. \begin{array}{l} \uparrow \\ 3.5 \times \end{array} \right\}$$

$$\frac{W}{L} = \frac{100}{0.5} = 200$$

$$\lambda = 0 \rightarrow V_{th} = V_{th0}$$

$$V_{thn} = 0.7 \text{ V}$$

$$V_{thp} = 0.8 \text{ V}$$

b) Figure A

$$V_x = V_{DD} - |V_{gs5}| - |V_{gs7}|$$

$$V_{gs7} = \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}} + V_{thp} =$$

$$V_{gs7} = 0.361 + 0.8 =$$

$$V_{gs7} = 1.161$$

$$V_x = V_{DD} - |V_{gs7}|$$

$$V_x = 3 - 1.161$$

$$V_x = 1.839 \text{ V}$$

Figure B

$$V_x = V_{DD} - |V_{gs7}|$$

$$\overset{V_x = 3}{\sqrt{\frac{2(0.5 \text{ mA})}{3.83 \text{ E-}5 (200)}}} + 0.8$$

c) Max Swing?

$$V_{out, \max} = V_{CM, \max} < 1.507 \text{ V}$$

$$V_{CM, \min} - V_{th2} > \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$

$$V_{CM, \min} > \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{thn}$$

$$V_{CM, \min} > \sqrt{\frac{2(0.5 \text{ mA})}{1.34 \text{ E-}4 (200)}} + 0.7$$

$$V_{CM, \min} > 0.139 + 0.7$$

$$V_{CM, \min} > 0.893$$

$$V_{out, \text{swing}} = V_{CM, \max} - V_{CM, \min}$$

$$V_{out, \text{swing}} = 1.507 - 0.893$$

$$V_{out, \text{swing}} = 0.614 \text{ V}$$

$$d.) \quad V_{b2, \max} - V_{th5} < |V_{DS5}|$$

$$V_{b2, \max} < |V_{DS5}| + V_{th5}$$

$$< |V_X - (V_{DD} - V_{DS7})| + V_{th5}$$

$$< |V_X - V_{DD} + V_{DS7}| + V_{th5}$$

$$< |(V_{DD} - V_{GS7}) - V_{DD} + (V_{GS7} - V_{th7})| + V_{th5}$$

$$< |V_{DD} - V_{GS7} - V_{DD} + V_{GS7} - V_{th7}| + V_{th5}$$

$$< |-V_{th7}| + V_{th5}$$

$$< 2V_{thp}$$

$$< 2(0.8)$$

$$V_{b2, \max} < 1.6 \text{ V}$$

$$V_{b2, \min} - V_{th5} > \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}} \quad | \quad I_D = \frac{I_{SS}}{2} = 0.5 \text{ mA}$$

$$V_{b2, \min} > \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}} + V_{thp}$$

$$V_{b2, \min} > \sqrt{\frac{2(0.5 \text{ mA})}{3.83 \text{ E-5} (200)}} + 0.8$$

$$V_{b2, \min} > \frac{0.361}{0.193} + 0.8$$

$$V_{b2, \min} > 1.61 \text{ V}$$

$$V_{out, \text{swing}} = V_{CM}$$

869

$$1.161 \text{ V} < V_{b2} < 1.6 \text{ V}$$

9.6. If in Fig. 9.23, $(W/L)_{1-8} = 100/0.5$ and $I_{SS} = 1 \text{ mA}$,

- (a) What CM level must be established at the drains of M_3 and M_4 so that $I_{D5} = I_{D6} = 1 \text{ mA}$? How does this constrain the maximum input CM level?
- (b) With the choice made in part (a), calculate the overall voltage gain and the maximum output swing.

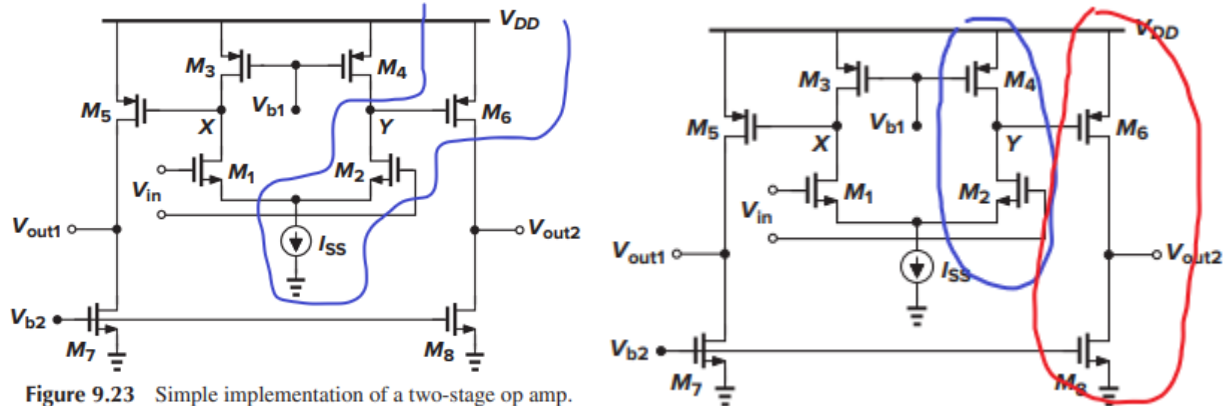


Figure 9.23 Simple implementation of a two-stage op amp.

9.6	Known
a.) $V_{CM, \max} - V_{th2} < V_{DD} - V_{GS6}$	$\mu_n C_{ox} = 1.34 \text{ E-}4$
$V_{CM, \max} < V_{DD} - V_{GS6} + V_{th2}$	$\mu_p C_{ox} = 3.83 \text{ E-}5$
$V_{GS6} = \sqrt{\frac{2I_D}{\mu_p C_{ox} (W/L)}} + V_{thp} \mid I_D = 1 \text{ mA}$	$V_{thn} = 0.7$
$V_{GS6} = \sqrt{\frac{2(1 \text{ mA})}{3.83 \text{ E-}5 (200)}} + 0.8$	$V_{thp} = 0.8$
$V_{GS6} = 0.511 + 0.8$	$\frac{W}{L} = \frac{100}{0.5} = 200$
$V_{GS6} = 1.311 \text{ V}$	
$V_{CM, \max} < V_{DD} - V_{GS6} + V_{thn}$	
$V_{CM, \max} < 3 - 1.311 + 0.7$	
$V_{CM, \max} < 2.39 \text{ V}$	
$V_{CM, \min} - V_{thn} > \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \mid I_D = 0.5 \text{ mA}$	
$V_{CM, \min} > \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} + V_{thn}$	
$V_{CM, \min} > \sqrt{\frac{2(0.5 \text{ mA})}{1.34 \text{ E-}4 (200)}} + 0.7$	
$V_{CM, \min} > 0.193 + 0.7$	
$V_{CM, \min} > 0.893 \text{ V}$	

$$b.) \quad V_{out, swing} = V_{DD} - 2V_{DSat}$$

$$V_{out, swing} = V_{DD} - |V_{DS_E}| - |V_{DS_E}|$$

$$V_{DS_E} = \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}} \quad | \quad I_D = 1 \text{ mA} = \sqrt{\frac{2(1 \text{ mA})}{3.83 \text{ E-} 5 (200)}} = 0.511 \text{ V}$$

$$V_{DS_E} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \quad | \quad I_D = 1 \text{ mA} = \sqrt{\frac{2(1 \text{ mA})}{1.34 \text{ E-} 4 (200)}} = 0.273 \text{ V}$$

$$V_{out, swing} = 3 - 0.511 - 0.273$$

$$V_{out, swing} = 2.215 \text{ V}$$

Known

$$\frac{W}{L} = \frac{100}{0.5} = 200$$

$$\lambda_n = 0.1$$

$$\lambda_p = 0.2$$

$$A_v = A_{v1} \cdot A_{v2}$$

$$A_v = g_{m2} (r_{o2} \parallel r_{o4}) \cdot g_{m6} (r_{o6} \parallel r_{o8})$$

$$g_{m2} \text{ A/K} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad | \quad I_D = \frac{I_{SS}}{2} = 0.5 \text{ mA}$$

$$g_{m2} = \sqrt{2(1.34 \text{ E-} 4)(0.5 \text{ mA})(200)} = 0.00518$$

$$g_{m6} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right) I_D} \quad | \quad I_D = 1 \text{ mA}$$

$$g_{m6} = \sqrt{2(3.83 \text{ E-} 5)(200)(1 \text{ mA})} = 0.00391$$

$$r_{o2} \text{ A/K} = \frac{1}{\lambda_n I_D} \quad | \quad I_D = 0.5 \text{ mA} = \frac{1}{(0.1)(0.5 \text{ mA})} = 20,000$$

$$r_{o8} = \frac{1}{\lambda_n I_D} \quad | \quad I_D = 1 \text{ mA} = \frac{1}{(0.1)(1 \text{ mA})} = 10,000$$

$$r_{o4} = \frac{1}{\lambda_p I_D} \quad | \quad I_D = 0.5 \text{ mA} = \frac{1}{(0.2)(0.5 \text{ mA})} = 10,000$$

$$r_{o6} = \frac{1}{\lambda_p I_D} \quad | \quad I_D = 1 \text{ mA} = \frac{1}{(0.2)(1 \text{ mA})} = 5,000$$

$$r_{o2} \parallel r_{o4} = 20 \text{ k} \parallel 10 \text{ k} = 6.67 \text{ k}$$

$$r_{o6} \parallel r_{o8} = 5 \text{ k} \parallel 10 \text{ k} = 3.33 \text{ k}$$

$$A_v = (0.00518)(6.67 \text{ k}) \cdot (0.00391)(3.33 \text{ k})$$

$$A_v = 34.54 \cdot 13.03$$

$$A_v = 450 \text{ V/V}$$

- 9.10. Suppose that in Fig. 9.88, $I_1 = 100 \mu\text{A}$, $I_2 = 0.5 \text{ mA}$, and $(W/L)_{1-3} = 100/0.5$. Assuming that I_1 and I_2 are implemented with PMOS devices having $(W/L)_P = 50/0.5$,
- Calculate the gate bias voltages of M_2 and M_3 .
 - Determine the maximum allowable output voltage swing.
 - Calculate the overall voltage gain and the input-referred thermal noise voltage.


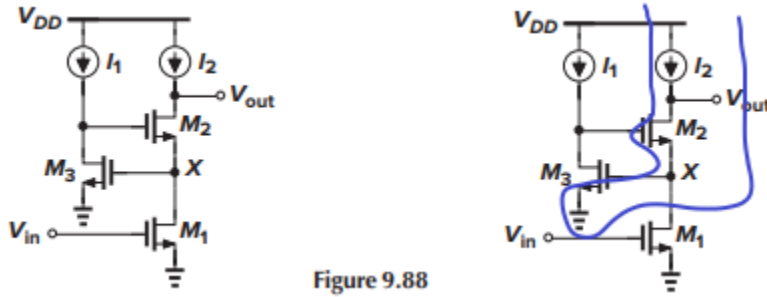


Figure 9.88

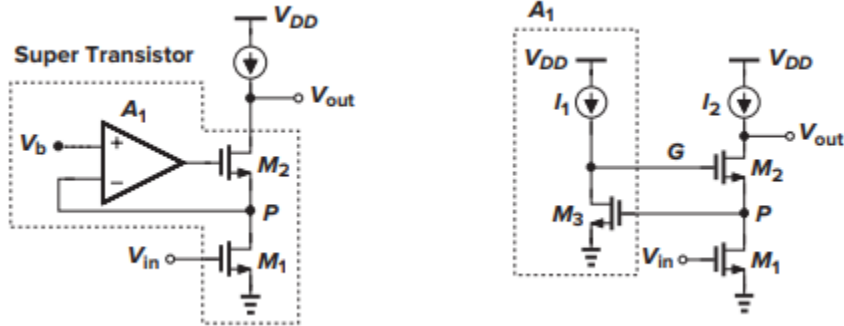

$$|A_v| \approx g_{m1}[r_{O2} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O1}]$$

$$\approx g_{m1}g_{m2}r_{O1}r_{O2}(A_1 + 1)$$

9.10

Known

a) Find V_{GS3} :

$$V_{GS3} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{thn} \quad | \quad I_D = I_1 = 0.1 \text{ mA}$$

$$V_{GS3} = \sqrt{\frac{2(0.1 \text{ mA})}{1.34 \times 10^{-4} (200)}} + 0.7$$

$$V_{GS3} = 0.086 + 0.7 =$$

$$V_{GS3} = 0.786 \text{ V}$$

Find V_{GS2} :

$$V_{GS2} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{thn} \quad | \quad I_D = I_2 = 0.5 \text{ mA}$$

$$V_{GS2} = 0.193 + 0.7$$

$$V_{GS2} = 0.893 \text{ V}$$

$$b) \quad V_{out, swing} = V_{DD} - V_{DS_{I_2}} - V_{DS_{sat_2}} - V_{GS3}$$

$$V_{DS_{sat_{I_2}}} = \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p}} \quad | \quad I_D = 0.5 \text{ mA} = \sqrt{\frac{2(0.5 \text{ mA})}{3.83 \times 10^{-5} (100)}} = 0.51 \text{ V}$$

$$V_{DS_{sat_2}} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \quad | \quad I_D = 0.5 \text{ mA} = \sqrt{\frac{2(0.5 \text{ mA})}{1.34 \times 10^{-4} (200)}} = 0.193 \text{ V}$$

$$V_{out, swing} = 3 - 0.51 - 0.193 - 0.786$$

$$V_{out, swing} = 1.51 \text{ V}$$

$$\frac{W}{L} = \frac{100}{0.5} = 200 \quad [\text{nmos}]$$

$$\frac{W}{L} = \frac{50}{0.5} = 100 \quad [\text{pmos}]$$

$$V_{thn} = 0.7$$

$$V_{thp} = 0.8$$

$$\mu_n C_{ox} = 1.34 \times 10^{-4}$$

$$\mu_p C_{ox} = 3.83 \times 10^{-5}$$

c.) Given perfect current source:

$$A_v = g_{m1} g_{m2} r_{o1} r_{o2} (A_1 + 1)$$

A_1 is replaced with NMOS CS stage

$$|A_1| = g_{m3} (r_{o3} \parallel r_{oI_1})$$

$$g_{m3} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad | I_D = I_1 = 0.1 \text{ mA}$$

$$g_{m3} = \sqrt{1.34 \text{ E-}4 (200) (0.1 \text{ mA}) 2}$$

$$g_{m3} = 0.00164 = 0.00232$$

$$g_{m1} = g_{m2} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad | I_D = I_2 = 0.5 \text{ mA}$$

$$= \sqrt{1.34 \text{ E-}4 (200) (0.5 \text{ mA}) 2}$$

$$g_{m1} = g_{m2} = 0.00366 = 0.00518$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1 (0.5 \text{ mA})} = 20,000$$

$$r_{o3} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1 (0.1 \text{ mA})} = 100,000$$

$$r_{oI_1} = \frac{1}{\lambda_p I_D} = \frac{1}{0.2 (0.1 \text{ mA})} = 50,000$$

$$|A_1| = (0.00164) (100 \text{ k} \parallel 50 \text{ k}) = 54.57 \text{ V/V}$$

$$A_v = \frac{(0.00366)^2 (20,000)^2 (54.57 + 1)}{(0.00518)^2} = 297,847 \approx 300 \text{ k V/V}$$

$$A_v \approx 297,847 \approx 300 \text{ k V/V} \quad \text{--- not correct}$$

* V_{out} is in parallel with I_2 [not perfect current source]

Known

$$\mu_n C_{ox} = 1.34 \text{ E-}4$$

$$\mu_p C_{ox} = 3.83 \text{ E-}5$$

$$\frac{W}{L} = \frac{100}{0.5} = 200 \text{ [nmos]}$$

$$\frac{W}{L} = \frac{50}{0.5} = 100 \text{ [pmos]}$$

$$\lambda_n = 0.1$$

$$\lambda_p = 0.2$$

$$A_v = g_{m1} [r_{oI_2} \parallel \underbrace{g_{m2} r_{o1} r_{o2} (A_1 + 1)}_{\text{this is massive magnitude E7}}]$$

$$r_{oI_2} = \frac{1}{\lambda_p I_D} = \frac{1}{0.2 (0.5 \text{ mA})} = 10,000$$

$$A_v \approx r_{oI_2} \parallel g_{m2} r_{o1} r_{o2} (A_1 + 1) \approx r_{oI_2}$$

$$A_v = g_{m1} r_{oI_2}$$

$$A_v = (0.00518) (10,000)$$

$$A_v \approx 51.8 \text{ V/V}$$

$$A_v \approx 51.8 \text{ V/V}$$

9.18. In this problem, we design a two-stage op amp based on the topology shown in Fig. 9.90. Assume a power budget of 6 mW, a required output swing of 2.5 V, and $L_{eff} = 0.5 \mu\text{m}$ for all devices.


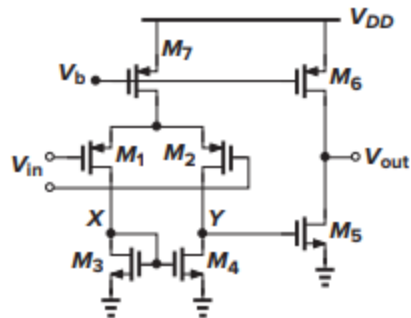



Figure 9.90

- Allocating a current of 1 mA to the output stage and roughly equal overdrive voltages to M_5 and M_6 , determine $(W/L)_5$ and $(W/L)_6$. Note that the gate-source capacitance of M_5 is in the signal path, whereas that of M_6 is not. Thus, M_6 can be quite a lot larger than M_5 .
- Calculate the small-signal gain of the output stage.
- With the remaining 1 mA flowing through M_7 , determine the aspect ratio of M_3 (and M_4) such that $V_{GS3} = V_{GS5}$. This is to guarantee that if $V_{in} = 0$ and hence $V_X = V_Y$, then M_5 carries the expected current.
- Calculate the aspect ratios of M_1 and M_2 such that the overall voltage gain of the op amp is equal to 500.

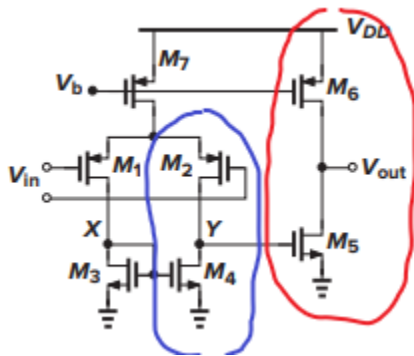

Stage 1: CS (pmos)

Stage 2: CS (nmos)

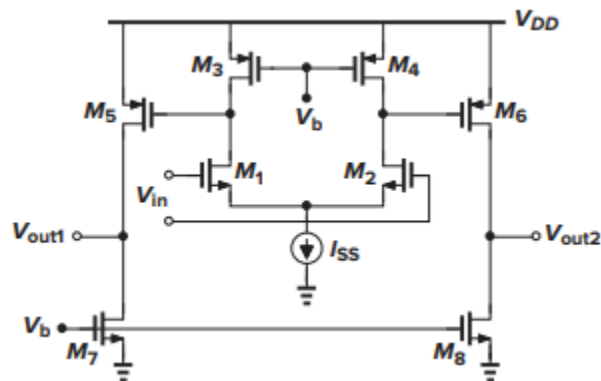

Compare to Differential Two-Stage Op Amp

9.18

Known

a.) Find $\left(\frac{W}{L}\right)_5$ and $\left(\frac{W}{L}\right)_6$

$$L_{eff} = 0.5 \text{ E-6}$$

$$V_{out, swing} = 2.5 \text{ V}$$

$$V_{DD} = 3 \text{ V}$$

$$V_{DS5} + V_{DS6} < V_{DD} - V_{out, swing}$$

$$V_{DS5} + V_{DS6} < 3 - 2.5$$

$$V_{DS5} + V_{DS6} < 0.5 \text{ V} \quad \text{and} \quad V_{DS5} \approx V_{DS6} \quad \text{so each get } 0.25 \text{ V}$$

[V_{DS5}]

$$0.25 \text{ V} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \quad | \quad I_D = 1 \text{ mA}$$

$$0.25^2 = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)} \quad | \quad L = L_{eff} = 0.5 \text{ E-6}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (0.25)^2}$$

$$W = \frac{2I_D \cdot L}{\mu_n C_{ox} (0.25)^2} = \frac{2(1 \text{ mA})(0.5 \text{ E-6})}{1.34 \text{ E-4} (0.25)^2}$$

$$W_5 = 119 \text{ E-6 m}$$

$$W_6 = \frac{2I_D \cdot L}{\mu_p C_{ox} (0.25)^2} = \frac{2(1 \text{ mA})(0.5 \text{ E-6})}{3.83 \text{ E-5} (0.25)^2}$$

$$W_6 = 418 \text{ E-6 m}$$

$$b) \quad A_{v2} = g_{m5} (r_{os} \parallel r_{o6})$$

$$\left(\frac{W}{L}\right)_5 = \frac{119}{0.5} = 238.8$$

$$g_{m5} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad | \quad I_D = 1 \text{ mA}$$

$$g_{m5} = \sqrt{2(1.34 \text{ E-4})(238.8)(1 \text{ mA})}$$

$$g_{m5} = 0.008$$

$$r_{os} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1(1 \text{ mA})} = 10,000$$

$$r_{o6} = \frac{1}{\lambda_p I_D} = \frac{1}{0.2(1 \text{ mA})} = 5,000$$

$$r_{os} \parallel r_{o6} = 3.33 \text{ k}$$

$$A_{v2} = (0.008)(3.33 \text{ k})$$

$$A_{v2} = 26.66 \text{ V/V}$$

$$c) \quad I_{D4} = \frac{I_{D7}}{2} = \frac{1 \text{ mA}}{2} = 0.5 \text{ mA}$$

$$\text{Find } \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_3$$

$$V_{GS3} = V_{GS5}$$

$$\sqrt{\frac{2I_D'}{\mu_n C_{ox} \left(\frac{W}{L}\right)_3}} + V_{thn} \quad | \quad I_D' = 0.5 \text{ mA} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5}} + V_{thn} \quad | \quad I_D = 1 \text{ mA}$$

$$\frac{2I_D'}{\mu_n C_{ox} \left(\frac{W}{L}\right)_3} = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5} \quad I_D' = \frac{I_D}{2}$$

$$\frac{I_D'}{\left(\frac{W}{L}\right)_3} = \frac{2I_D}{\left(\frac{W}{L}\right)_5} \rightarrow \left(\frac{W}{L}\right)_3 = \frac{\left(\frac{W}{L}\right)_5}{2}$$

$$d.) \quad A_V = A_{V1} \cdot A_{V2} = 500$$

$$A_V = g_{m2} (r_{o2} \parallel r_{o4}) \cdot 26.66 = 500$$

$$g_{m2} (r_{o2} \parallel r_{o4}) = \frac{500}{26.66} = 18.75$$

$$g_{m2} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_2 I_D} \quad | \quad I_D = 0.5 \text{ mA}$$

$$g_{m2} = \sqrt{2(3.83 \text{E-}5)(0.5 \text{ mA}) \left(\frac{W}{L}\right)_2}$$

$$g_{m2} = \sqrt{3.83 \text{E-}8 \left(\frac{W}{L}\right)_2}$$

$$r_{o2} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.2)(0.5 \text{ mA})} = 10,000$$

$$r_{o4} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1(0.5 \text{ mA})} = 20,000$$

$$r_{o2} \parallel r_{o4} = 6.67 \text{ k}$$

$$A_{V1} = \left(\sqrt{3.83 \text{E-}8 \left(\frac{W}{L}\right)_2} \right) (6.67 \text{ k}) = 18.75 \text{ V/V}$$

$$3.83 \text{E-}8 \left(\frac{W}{L}\right)_2 = \left(\frac{18.75}{6.67 \text{ k}} \right)^2$$

$$\left(\frac{W}{L}\right)_2 = \frac{(18.75/6.67 \text{ k})^2}{3.83 \text{E-}8}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \underline{206.56} \quad \rightarrow \quad W = 206.56 L_{\text{eff}} = 103 \text{E-}6 \text{ m}$$

Known:

$$L_{\text{eff}} = 0.5 \text{E-}6$$