

12.1. Derive an expression for  $I_{out}$  in Fig. 12.42.

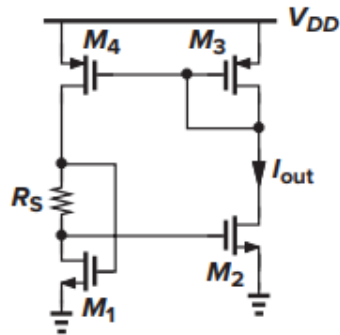


Figure 12.42

1. Given  $M_3 = M_4$ , then  $I_{ref} = I_{out}$

Proof: Current Mirror

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W_4}{L_4} \right) (V_{gs} - V_{th_4})^2 \quad I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W_3}{L_3} \right) (V_{gs} - V_{th_3})^2$$

$M_3$  and  $M_4$  are same device  $\rightarrow V_{th_4} = V_{th_3}$

KCL  $I_{out} - I_{ref} = 0$

$$I_{out} = \frac{(W_3/L_3)}{(W_4/L_4)} I_{ref} = I_{ref}$$

Also,  $M_1 = M_2$

KVL  $(I_{ref} R_S - V_{gs_1}) + V_{gs_2} = 0 \quad | \quad I_{D1} = I_{ref} \quad ; \quad I_{D2} = I_{out}$

$$I_{ref} R_S - \left( \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox} (W_1/L_1)}} + V_{th_1} \right) + \left( \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} (W_2/L_2)}} + V_{th_2} \right)$$

Known:  $I_{ref} = I_{out}$ ,  $V_{th_1} = V_{th_2}$

$$I_{out} R_S = \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} (W_1/L_1)}} - \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} (W_2/L_2)}} = \left( \sqrt{\frac{2 I_{out}}{\mu_n C_{ox}}} \right) \left( \sqrt{\frac{1}{(W_1/L_1)}} - \sqrt{\frac{1}{(W_2/L_2)}} \right)$$

$$I_{out}^2 R_S^2 = \left( \frac{2 I_{out}}{\mu_n C_{ox}} \right) \left( \sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right)^2$$

$$I_{out} = \left( \frac{2}{\mu_n C_{ox} R_S^2} \right) \left( \sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right)^2$$

- 12.2. Explain how the start-up circuit shown in Fig. 12.43 operates. Derive a relationship that guarantees that  $V_X < V_{TH}$  after the circuit turns on.

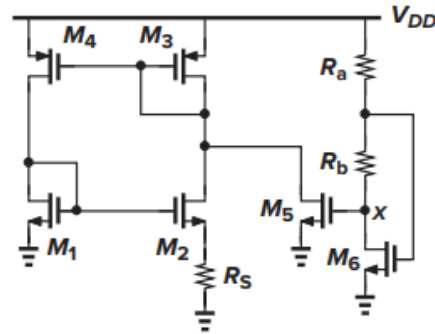


Figure 12.43

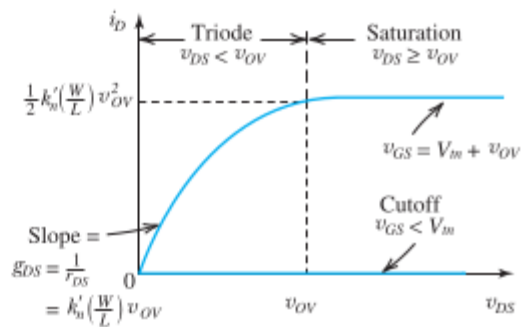


Figure: Sedra Smith Microelectronic Circuits

Define  $V_y$  at the point between  $R_a$  and  $R_b$ .

Initially, all channels are closed because  $V_{DS} = V_{GS} < V_{th}$  and no current runs through  $R_a$  and  $R_b$ .

$V_{DS}$  increases such that  $V_x = V_y = V_{GS} = V_{th}$ .

The channel is no longer pinched and allows current.

Both  $M_5$  and  $M_6$  turn on and the drain current through  $M_5$  turns on the remaining circuit.

Now the channel is induced and  $V_{DS}$  keeps increasing, allowing more drain current through  $M_6$ .

The voltages at  $V_y$  and  $V_x$  are defined as

$$V_y = V_{DD} - I_{D6} R_a \text{ and } V_x = V_{DD} - I_{D6} (R_a + R_b) = V_y - I_{D6} R_b.$$

As  $I_{D6}$  continues to grow,  $V_y$  decreases and also  $V_x$  decreases.

It is guaranteed that  $V_x < V_{th}$  when

$$V_{DD} - I_{D6} (R_a + R_b) < V_{th} \text{ where}$$

$$I_{D6} = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs} - V_{th})^2 \bigg|_{V_{gs} = V_{DD} - I_{D6} R_a}$$

- 12.5. In the circuit of Fig. 12.15, assume that  $Q_2$  and  $Q_4$  have a finite current gain  $\beta$ . Calculate the error in the output voltage.

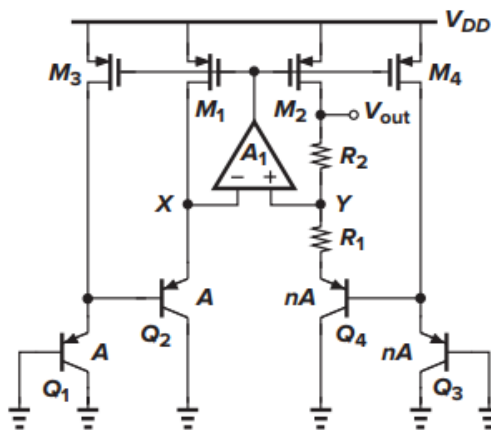


Figure 12.15 Reference generator incorporating two series base-emitter voltages.

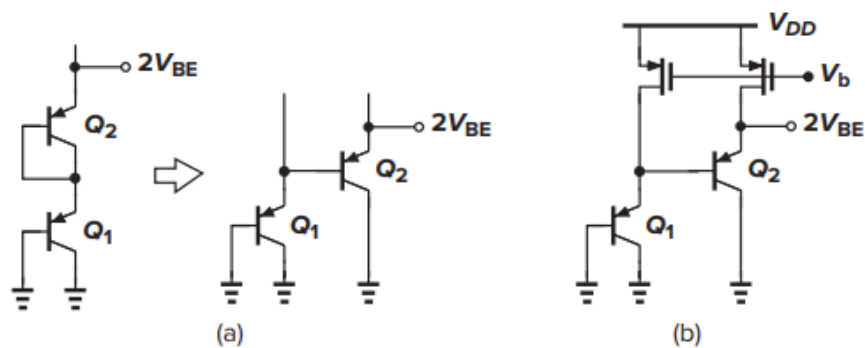


Figure 12.14 (a) Conversion of series diodes to a topology with grounded collectors; (b) circuit of part (a) biased by PMOS current sources.

5.

$$I_C = I_S e^{-V_{BE}/V_T}$$

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right)$$

$$I_E = \alpha I_C = \frac{\beta+1}{\beta} I_C$$

$$\Delta V_{BE} = 2V_T \ln \left( \frac{I_0}{I_S} \right) - 2V_T \ln \left( \frac{I_0}{n I_S} \right)$$

Assume all devices are same size

$$\Delta V_{BE} = 2V_T \ln n$$

$$I_{C4} = \frac{\Delta V_{BE}}{R_1} \rightarrow I_{E4} = \left( \frac{\beta+1}{\beta} \right) \frac{\Delta V_{BE}}{R_1}$$

$$V_{out} = V_{BE4} + V_{BE3} + (R_2 + R_1) I_{E4}$$

$$V_{out} = 2V_{BE} + (R_2 + R_1) \frac{2V_T \ln n}{R_1} \left( \frac{\beta+1}{\beta} \right)$$

$$V_{out} = 2V_{BE} + (R_2 + R_1) \frac{2V_T \ln n}{R_1} \left( 1 + \frac{1}{\beta} \right)$$

( $V_{out}$  without error has no  $\frac{1}{\beta}$  term)

$$V_{out, error} = (R_2 + R_1) \frac{2V_T \ln n}{R_1} \left( \frac{1}{\beta} \right)$$

$$= \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{\beta} \right) \frac{2V_T \ln n}{1}$$