

Figure1: Inverter Schematic


 


Figure2: Inverter Layout

Summary

Lab 3 emphasizes real world layout vs schematic simulations. In figure7, the layout waveform OUT_EX is slightly more damped, i.e. has a slower response, than the OUT waveform. The layout response takes ~50ps (0.05ns) longer to reach the steady state value than the schematic response. Other noticeable differences are seen in the input currents. The layout waveform VEX_PLUS is more damped and its peak current doesn't obtain the same values compared to the schematic. The layout current is several μA smaller at peak draw than VSCHM_PLUS.

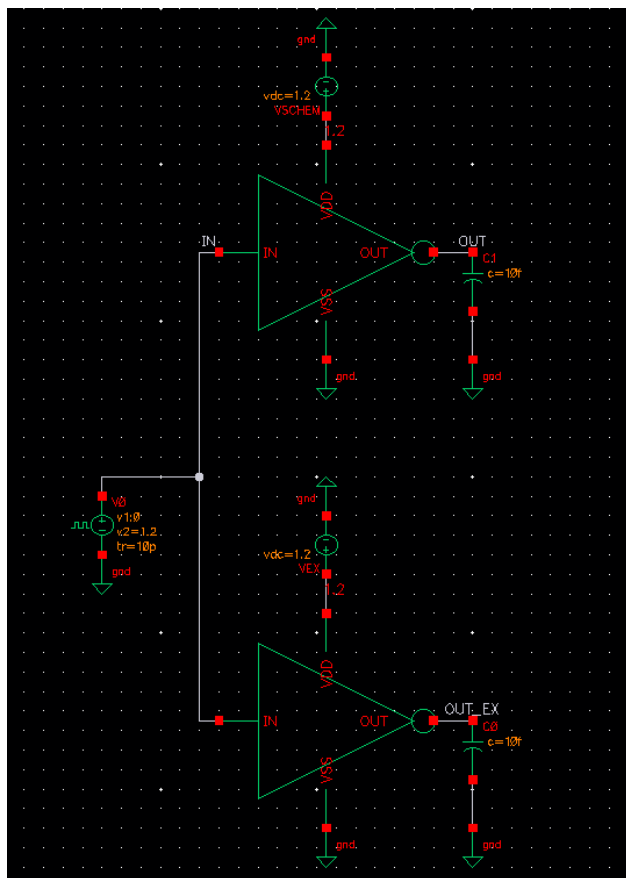

Check / Cell	Results
Check OD, DN, 1L	1
Check DOD, R, 1	1
Check PO, DN, 1L	1
Check PO, R, 8	2
Check DPO, R, 1	1
Check M9, DN, 1L	1
Check CSR, R, 1, NWi	1
Check CSR, R, 1, PPi	2
Check CSR, R, 1, NPi	2
Check CSR, R, 1, COi	12
Check CSR, R, 1, M1i	4
Check CSR, R, 1, M1_real	4
Check CSR, R, 1, ODi	4
Check CSR, R, 1, POi	1
Check DM1, R, 1	1
Check DM2, R, 1	1
Check DM3, R, 1	1
Check DM4, R, 1	1
Check DM5, R, 1	1
Check DM6, R, 1	1
Check DM7, R, 1	1
Check DM8, R, 1	1
Check DM9, R, 1	1
Check ESD, WARN, 1	1
Check DENSITY_PRINT_FILES	0

Figure3: Testbench Schematic

Figure4: DCR Clean Report

Fixed: PO.EX.1 & CO.EN3 CO.EN.4

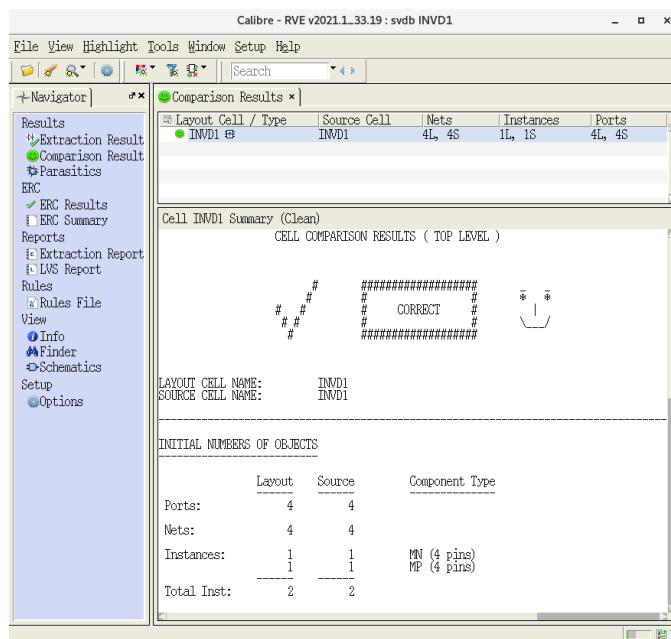


Figure5: LVS Clean Report

 


Figure6: Schematic and Layout Waveforms