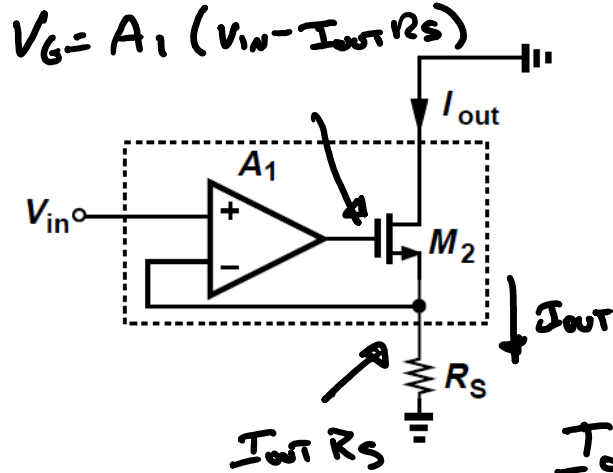


Lecture #18, Feb 18th, 2022

- We will bounce between chapters 8 (Feedback) and 9 (Op Amp design).
- Homework #3 Assigned.
- Project 2 will be assigned immediately.
- Monday we'll start Feedback
- Today
 - Regulated Cascode
 - Common-Mode Feedback.

Gain Boosting Techniques: Effective Gm



$$V_{GS} = A_1(V_{in} - I_{TOT} R_S) - I_{TOT} R_S$$

$$I_{TOT} = g_m \cdot V_{GS}$$

$$I_{TOT} = g_m [A_1(V_{in} - I_{TOT} R_S) - I_{TOT} R_S]$$

$$= g_m \cdot A_1 \cdot V_{in} - g_m A_1 I_{TOT} R_S - g_m I_{TOT} R_S$$

$$I_{TOT} (1 + g_m A_1 R_S + g_m R_S) = g_m \cdot A_1 \cdot V_{in}$$


FOR $1 \ll A_1$

$$G_m \approx \frac{I_{TOT}}{V_{in}} = \frac{g_m \cdot A_1}{(1 + g_m R_S (1 + A_1))}$$

$$G_m \approx \frac{1}{R_S},$$

SAME RESULT
w/o A_1 .

Output Resistance of Gain Boosting Stage

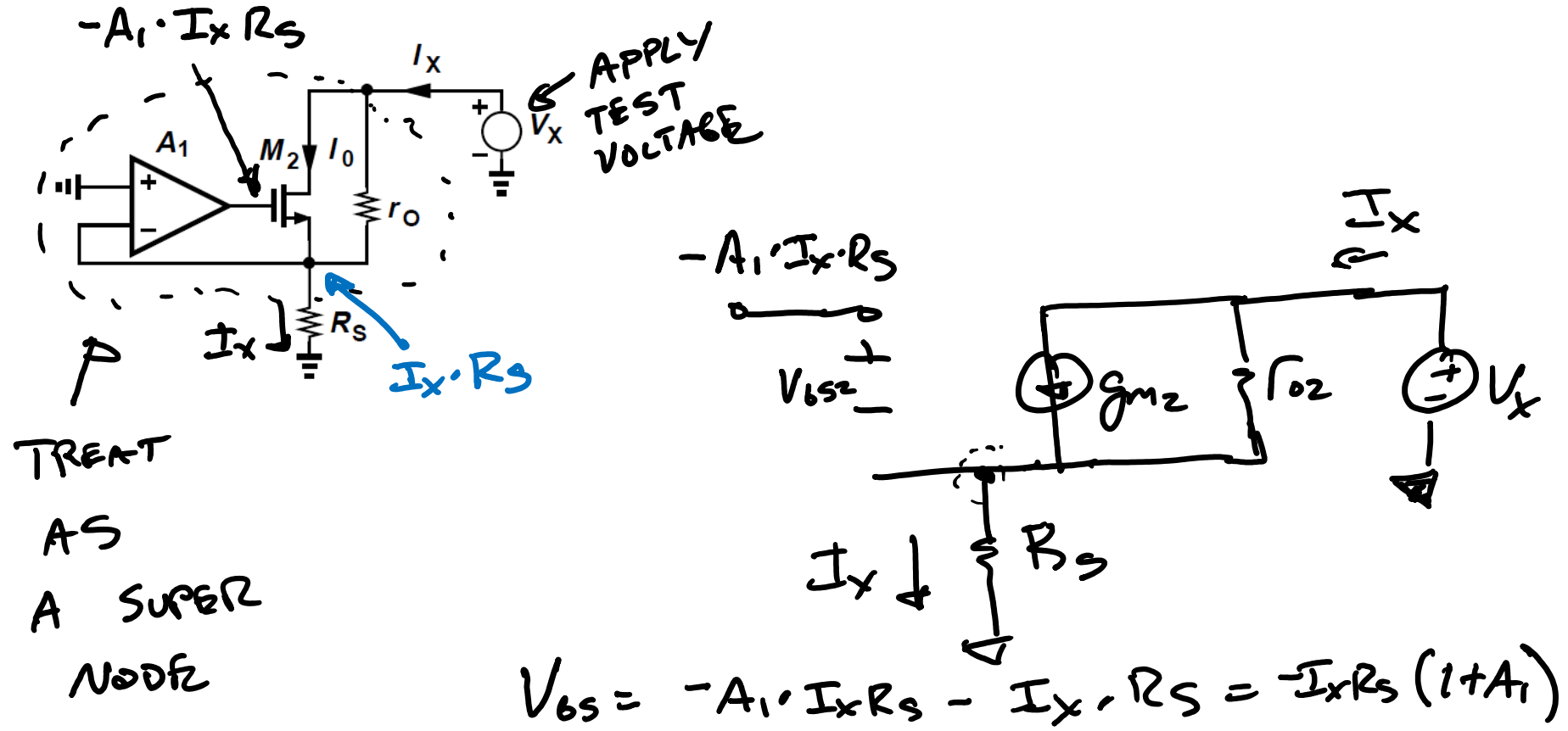

TREAT
AS
A SUPER
NODE

$$V_{bs} = -A_1 I_x R_s - I_x R_s = -I_x R_s (1 + A_1)$$


KCL @ SOURCE

$$I_x - g_{m2} V_{bs} - (V_x - V_s) g_{o2} = 0$$

$$V_s = I_x R_s$$

$$I_x + g_{m2} I_x R_s (1 + A_1) - V_x g_{o2} + I_x R_s g_{o2} = 0$$

Output Resistance of Gain-Boosted Stage

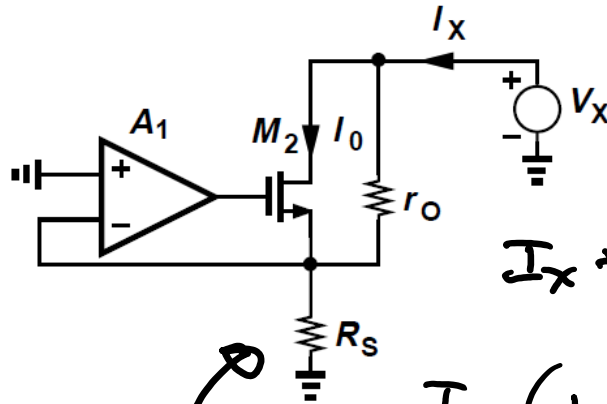

$$I_x + g_{m2} I_x R_s (1 + A_1) - V_x g_{o2} + I_x R_s g_{o2} = 0$$

$$I_x (1 + g_{m2} R_s (1 + A_1) + R_s g_{o2}) = V_x g_{o2}$$

REPLACE
w/ EQUIV.


$$\frac{V_x}{I_x} = \frac{(1 + g_{m2} R_s (1 + A_1) + R_s / r_{o2})}{1 / r_{o2}}$$

$$= \overset{\vee}{r_{o2}} + \underset{\cdot}{g_{m2}} R_s \underset{\cdot}{r_{o2}} (1 + A_1) + R_s$$

$$r_{o2}, R_s \ll g_{m2} R_s r_{o2} (1 + A_1)$$

$$R_o \approx g_{m2} R_s r_{o2} (1 + A_1) \approx g_{m2} R_s r_{o2} A_1$$

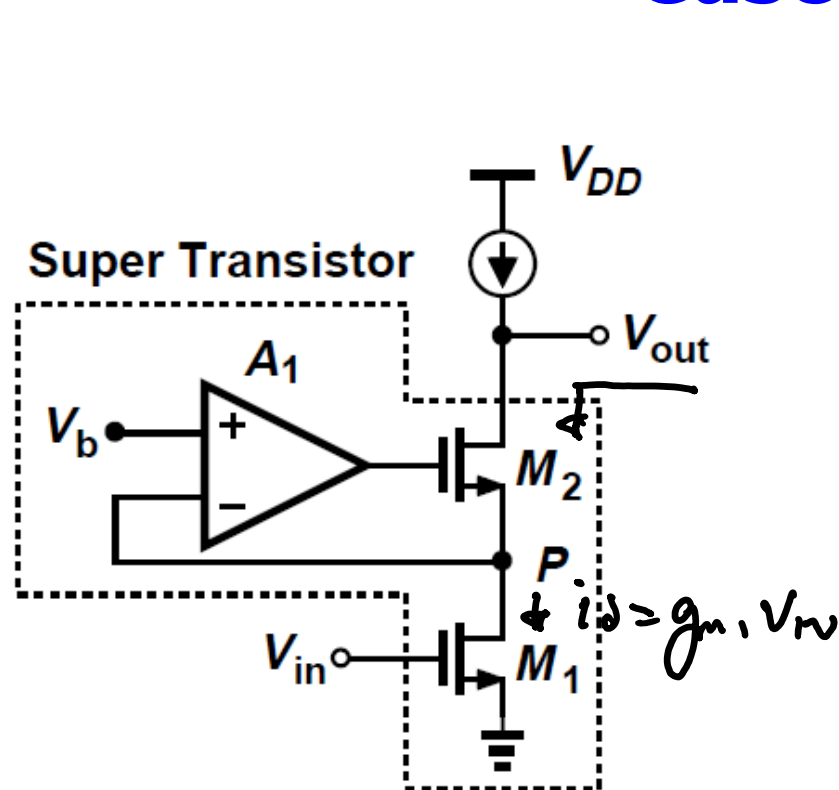Gain-boosting with Active/Regulated Cascode



$$R_o \approx g_{m2} (r_{o1}) r_{o2} \cdot A_1$$

$$G_m \approx g_{m1}$$


$$A_v \approx -g_{m1} \cdot (g_{m2}) r_{o1} r_{o2} \cdot A_1$$

$$\approx -g_m^2 r_{on}^2 \cdot A_2$$

$$10_5 < A_1 < \sim 100,000_3$$

• POTENTIALLY BLAST THE R_o & A_v !

Example Implementations

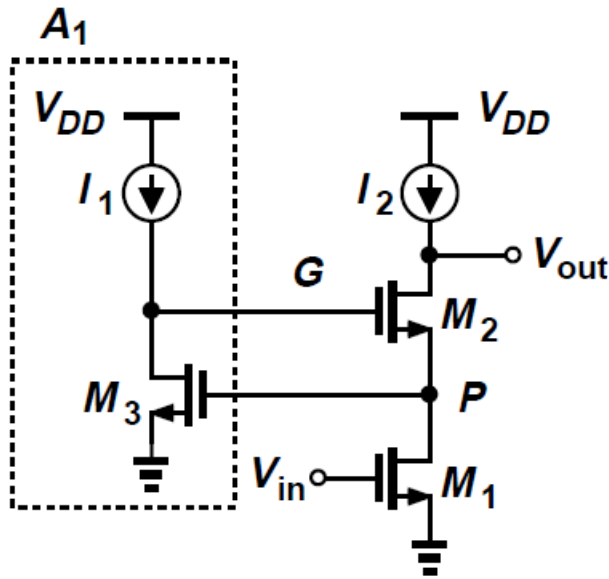

POPULAR IMPLEMENTATION.

$$A_1 \approx \underbrace{g_{m3} \cdot r_{o3}}$$

INTRINSIC GAIN OF M_3


$$\begin{aligned} A_v &\approx -g_{m1}^2 r_{o1}^2 \cdot A_1 \\ &= -g_{m3}^3 r_{o3}^3 \end{aligned}$$

Gain Boosting Circuit Implementation


- Simplest a common-source stage

$$|V_{out}/V_{in}| \approx g_{m1}r_{O1}g_{m2}r_{O2}(g_{m3}r_{O3} + 1)$$

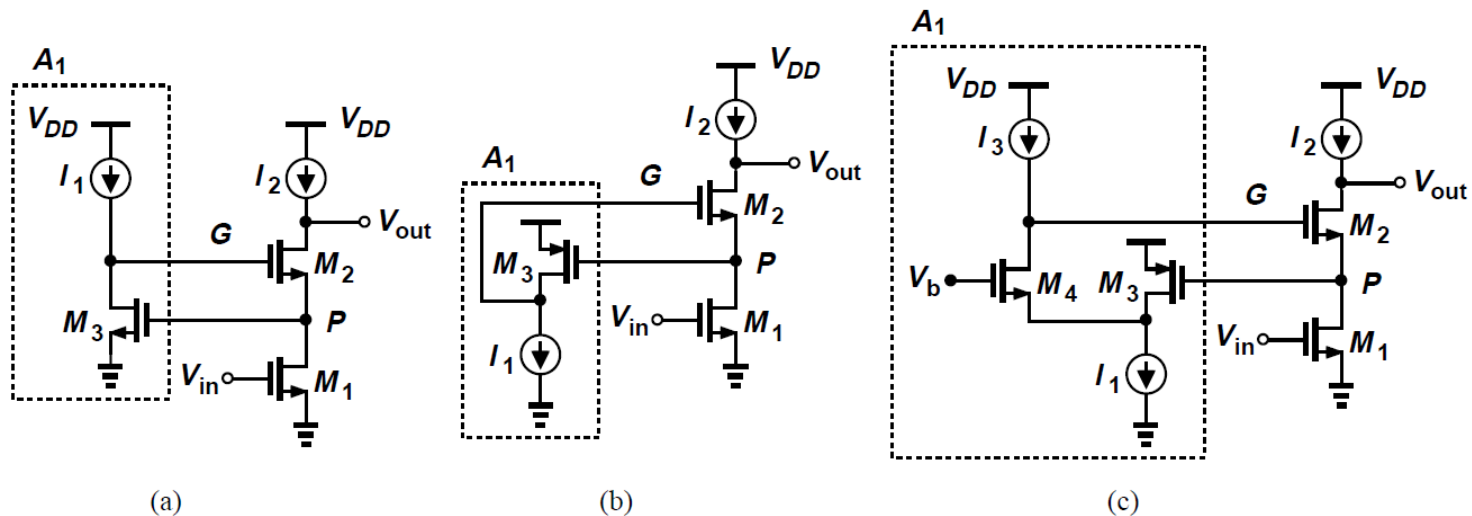- Avoid headroom limitation, PMOS common-source stage is better, but M3 could go in triode
- Folded-cascode inserts one more stage



Common-Mode Feedback

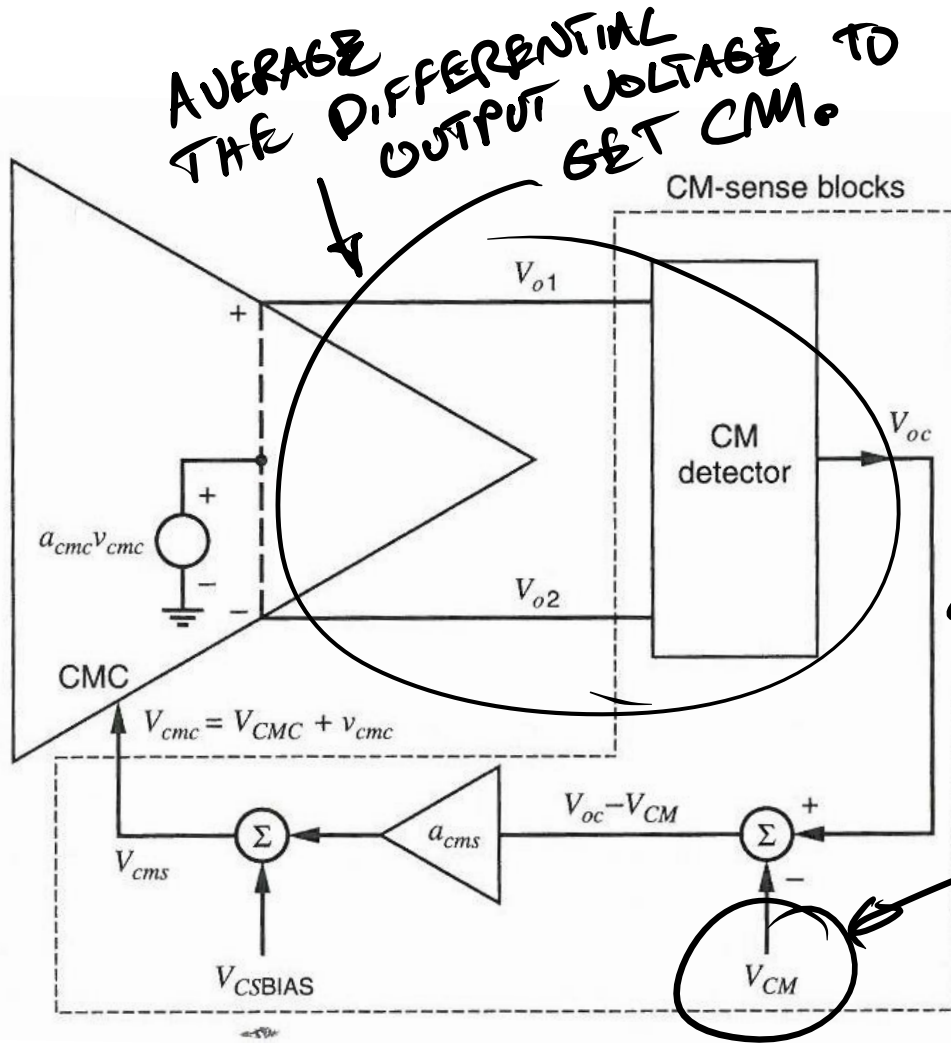


• IN DIFFERENTIAL AMPS,
NEED TO SET OUTPUT
COMMON MODE VOLTAGE.

← MEASURED COMMON
MODE VOLTAGE.


← COMPARE TO
THE DESIRED
COMMON MODE
VOLTAGE,

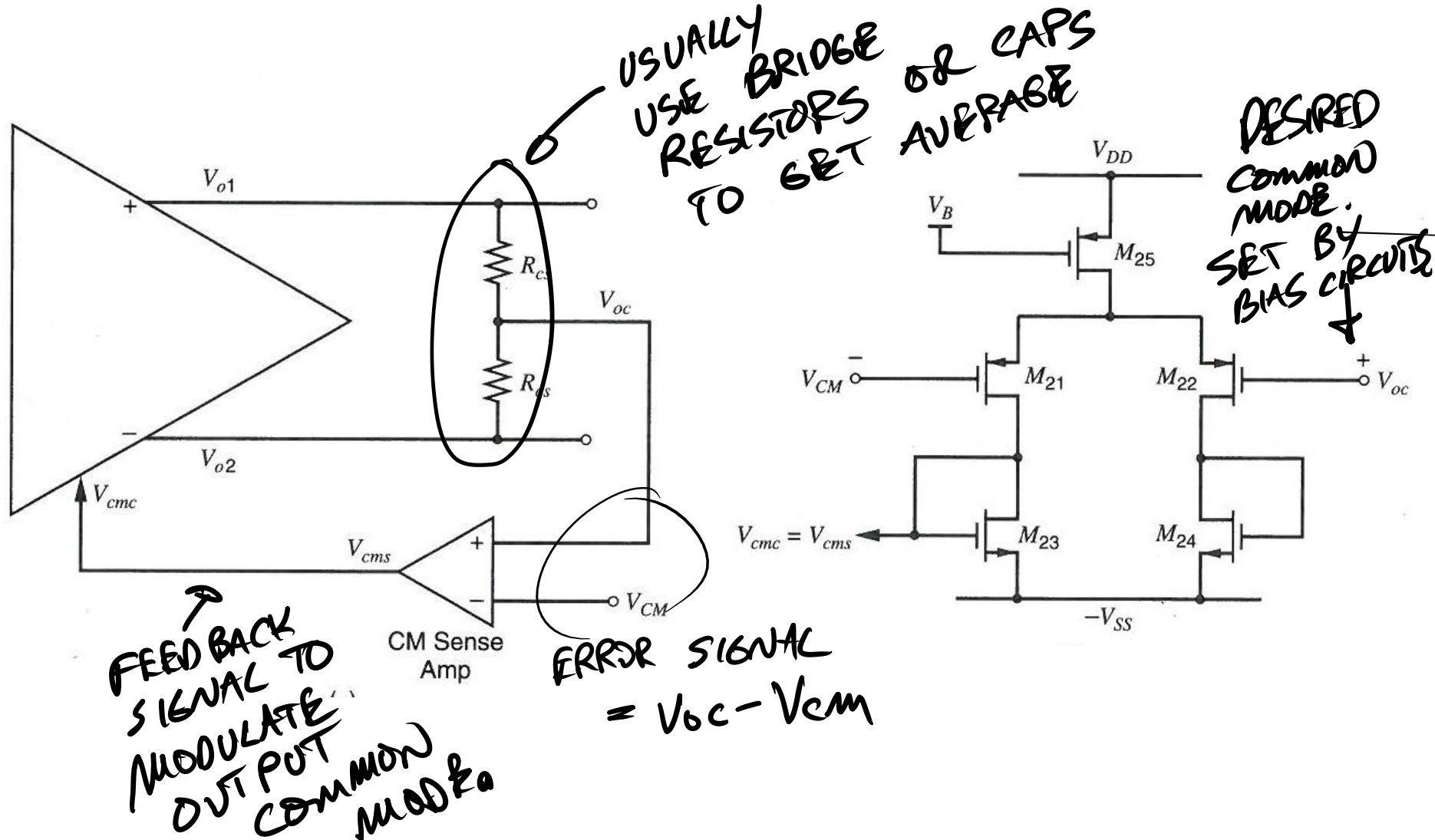Methods to Measure and Compare Common-Mode Voltage




Feeding back the Common Signal to the Amp.

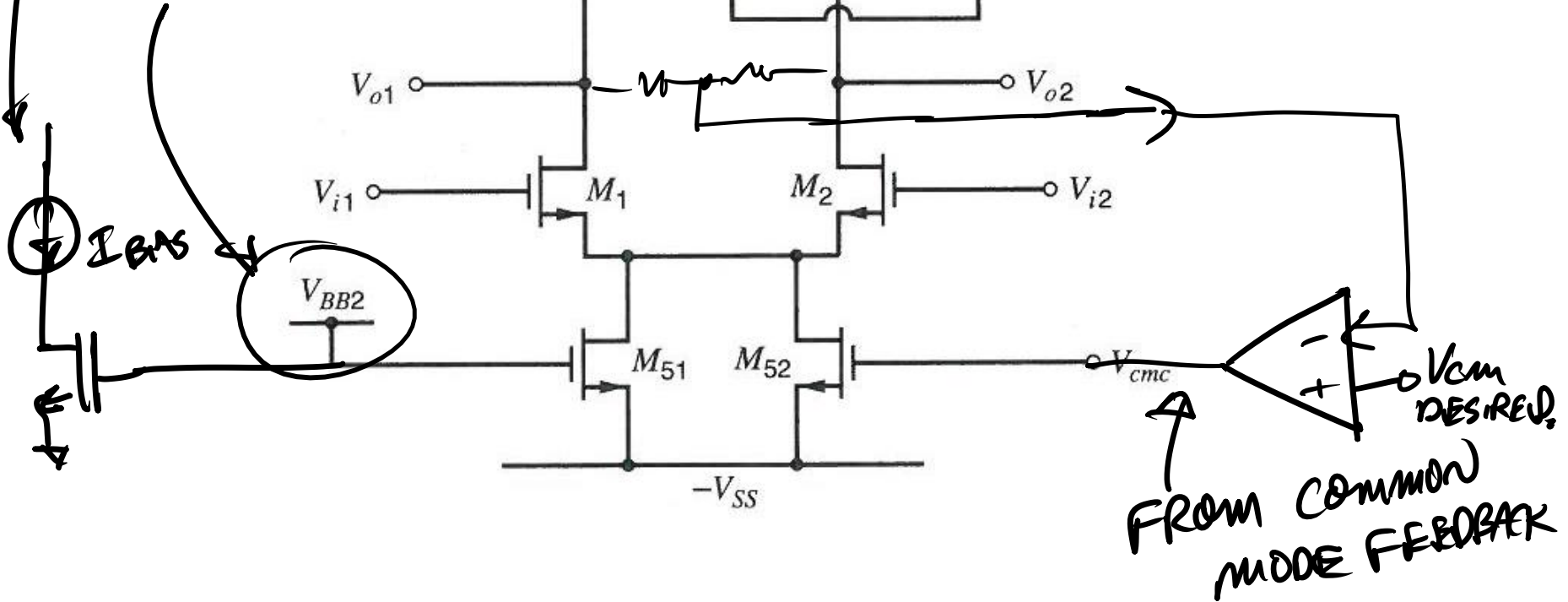- FROM CURRENT SOURCE / MIRROR
- FIXED / STATIC




Folded Cascode and Common-Mode Feedback

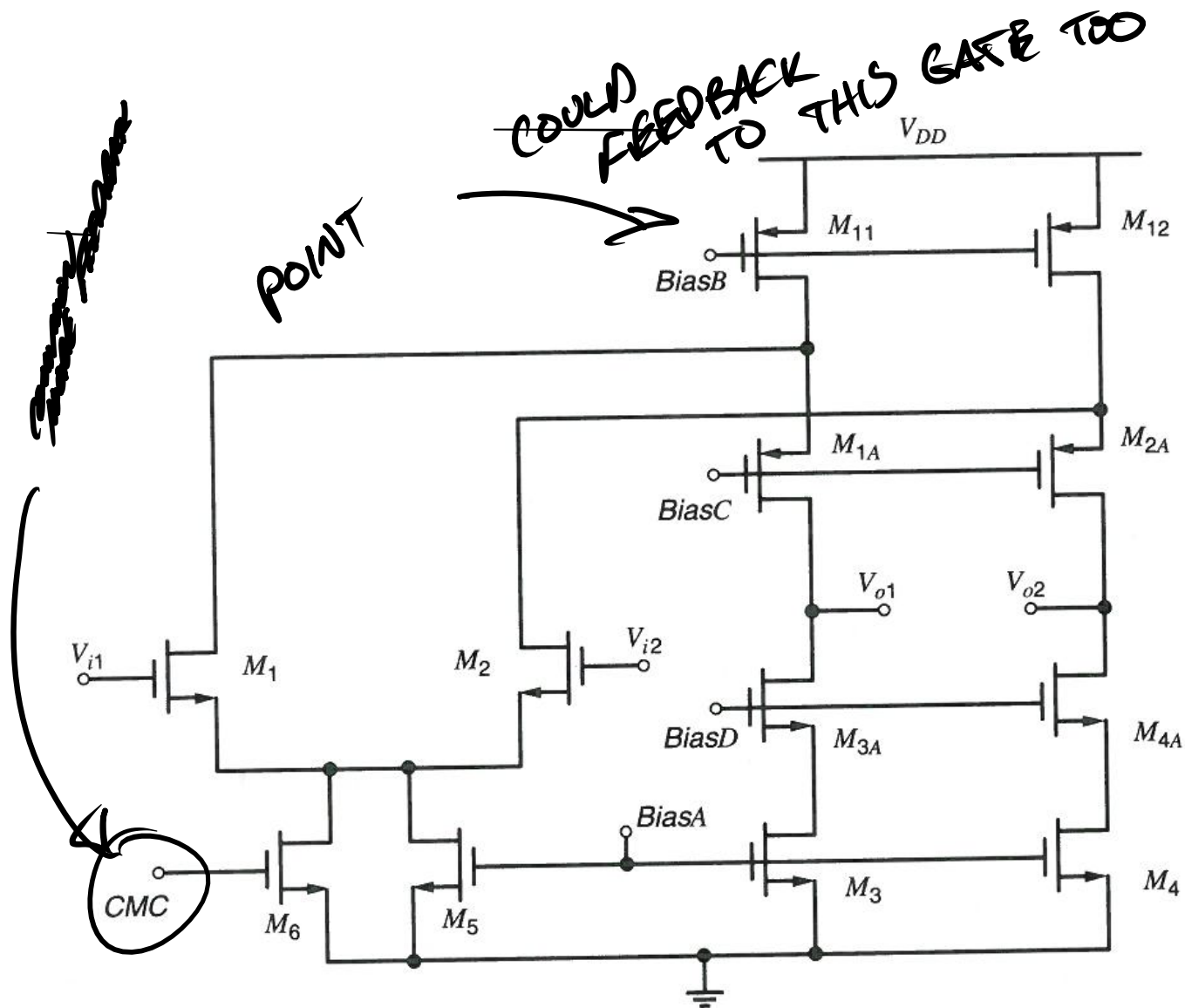


CM Sensing Techniques

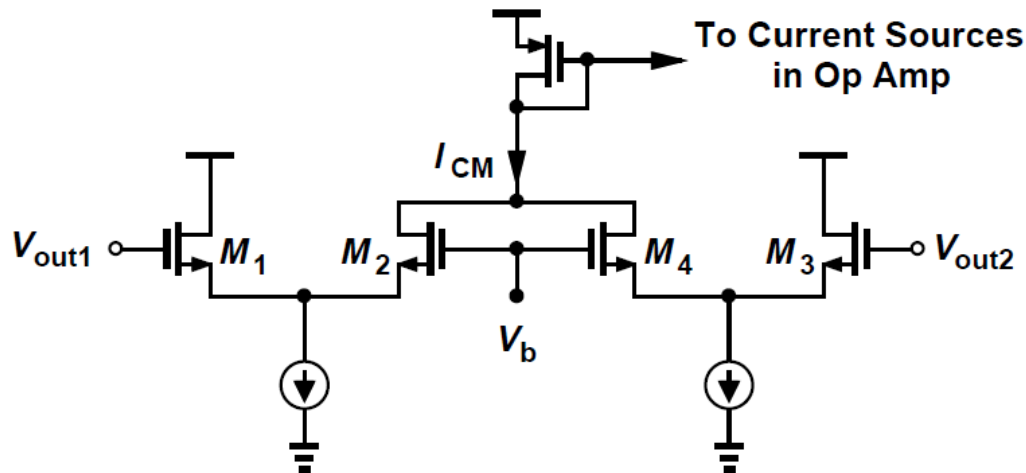
- Differential pair sensing
 - $I_{CM} \propto V_{out1} + V_{out2}$ by small signal analysis
 - Under Large swings situation, sensing is not valid due to large non-linearity.




- **Control cascade current source**

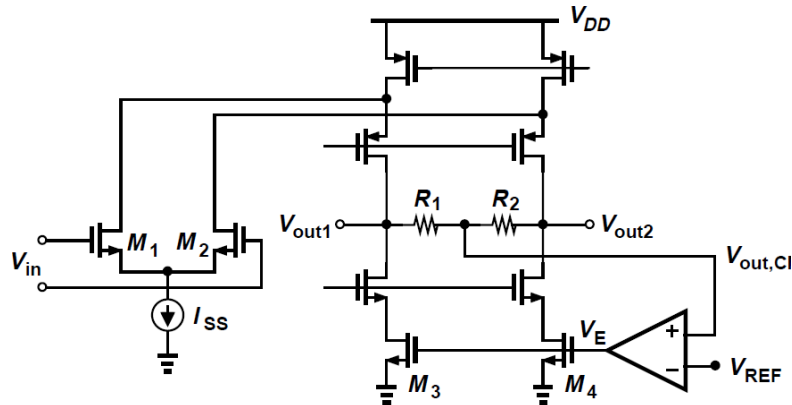


- **Control tail current source**

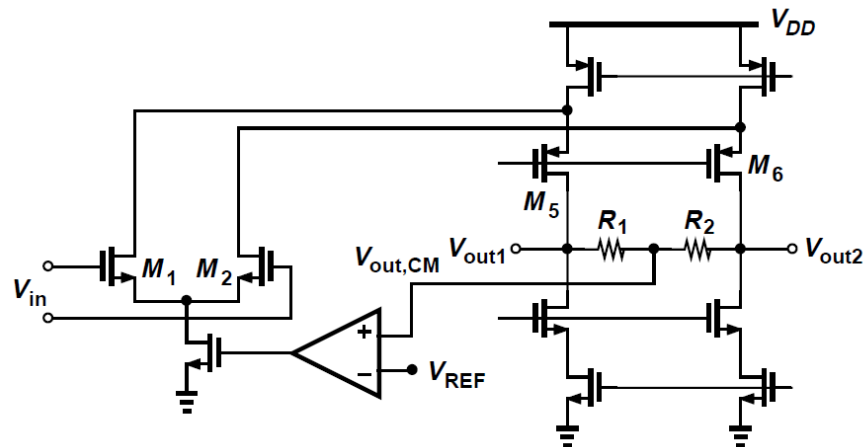

Detection w/o Bridge R or C

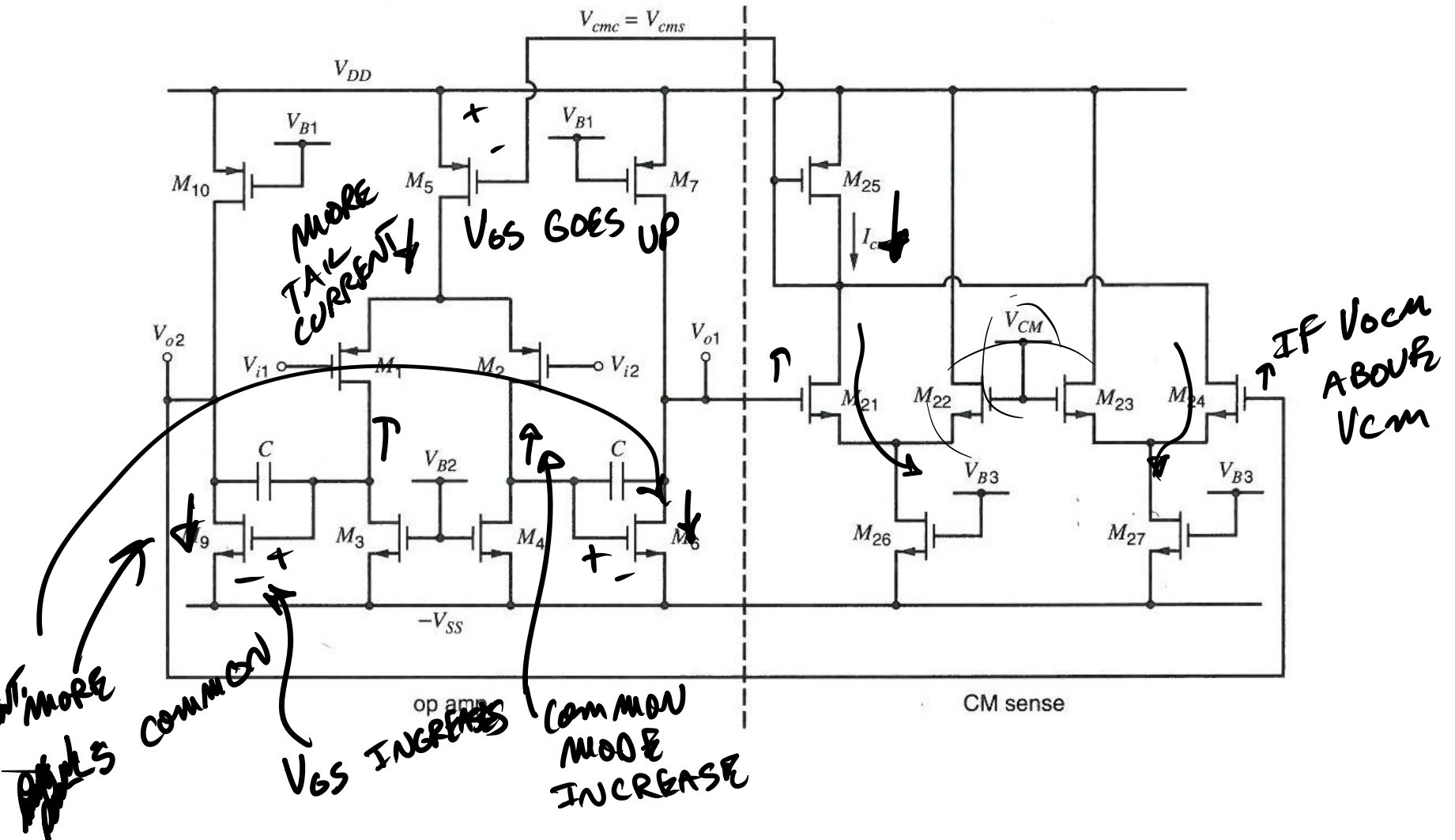



Project: Ideal Common-Mode Feedback

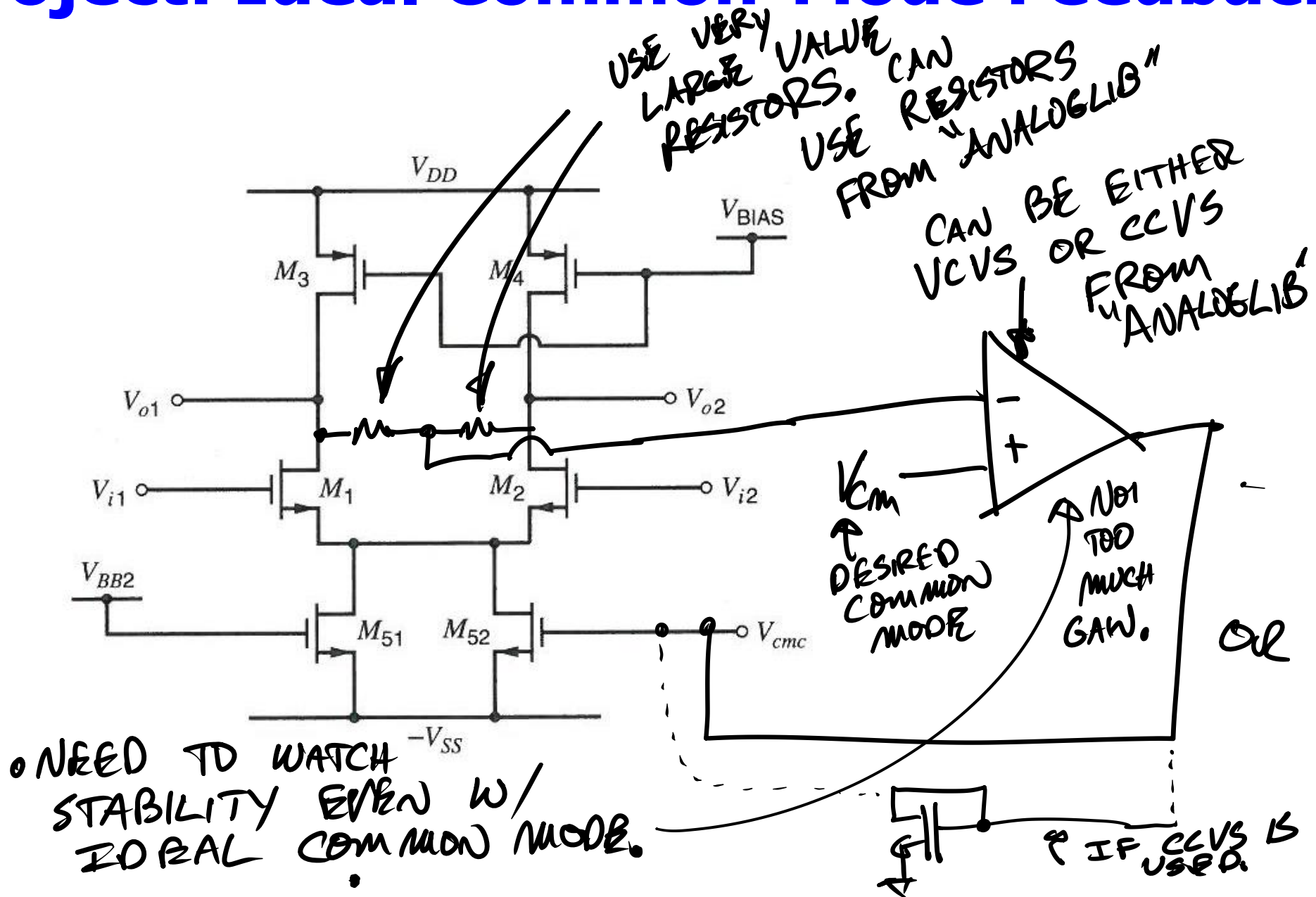

CM Feedback Techniques

- Deep triode sensing feedback
 - Limited headroom
 - Large C
 - Device variation
- Deep triode folded-cascade sensing feedback
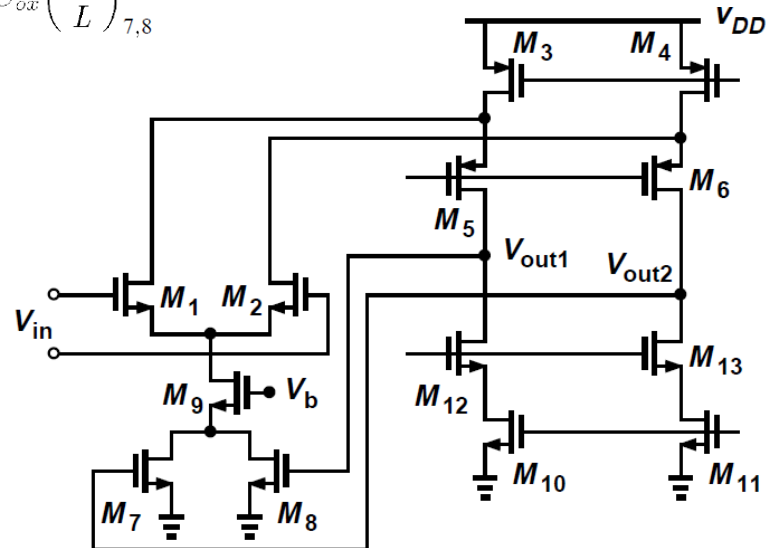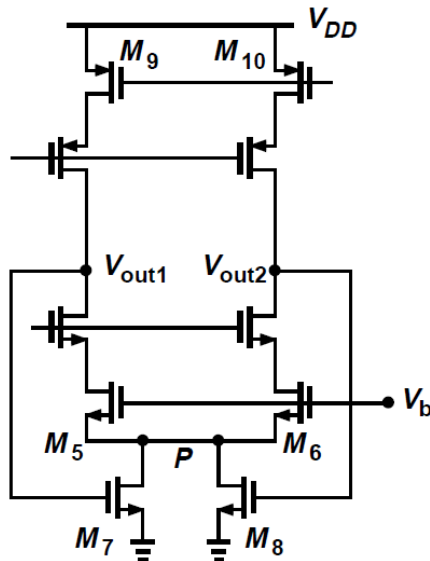
$$V_{out1} + V_{out2} = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)_{7,8}} \frac{1}{V_b - V_{GS5}} + 2V_{TH}$$




CM Feedback Techniques

- **Modification of deep triode sensing feedback**

$$(W/L)_{15} = (W/L)_9 \qquad (W/L)_{16} = (W/L)_7 + (W/L)_8$$

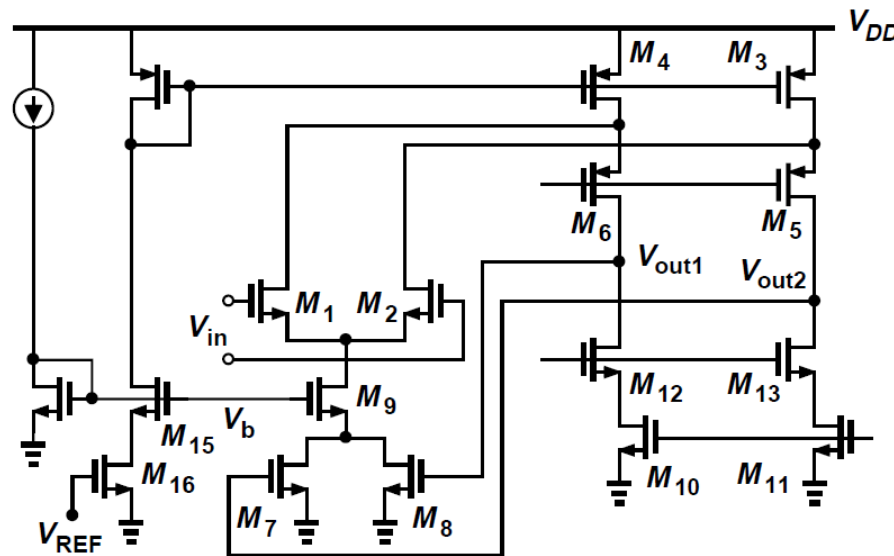- **The output level is relatively independent of device parameters and lowers sensitivity of V_b**




CM Feedback Techniques

- **Modification of deep triode sensing feedback**


$$(W/L)_{15} = (W/L)_9 \quad (W/L)_{16} = (W/L)_7 + (W/L)_8$$

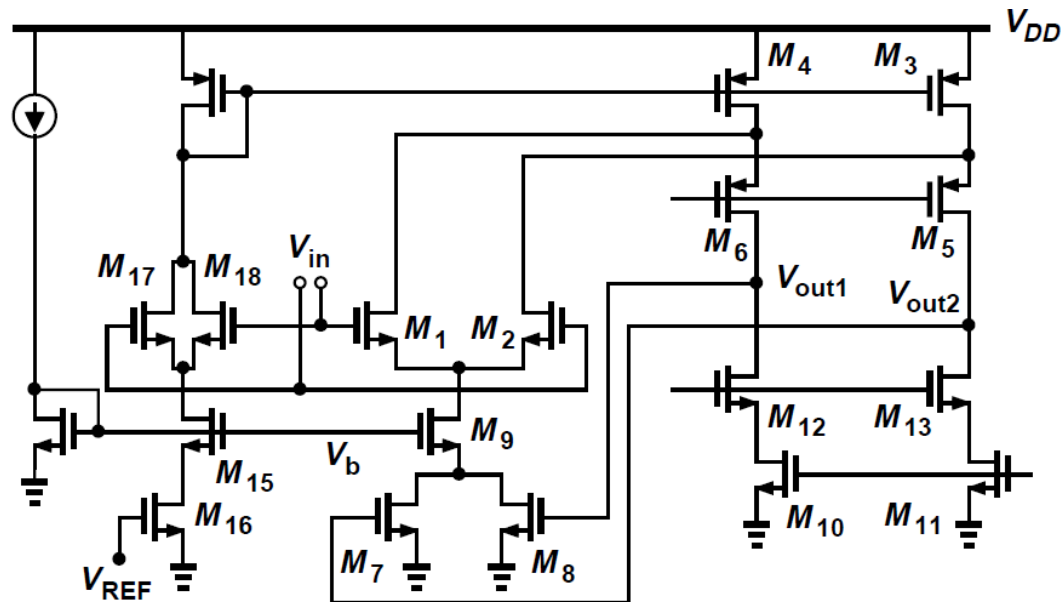- **M17, M18 reproduces the drain of M15 a voltage equal to the source voltage of M1 and M2**




CM Feedback Techniques


- Another type of CM feedback topology
- Diode-connected loads' output CM level is well-defined
- Differential small signal gain $g_{m1,2}(r_{O1,2} \parallel r_{O3,4} \parallel R_F)$
- Common-mode work as a diode-connected $R_F \gg r_{O1,2} \parallel r_{O3,4}$
- Low supply voltage design $I_1 R_F / 2 = |V_{TH3,4}|$

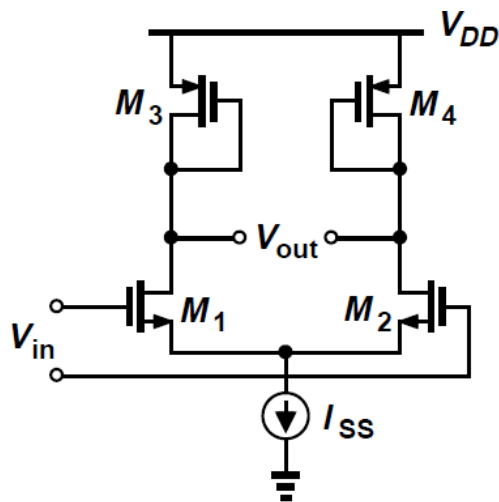

(a)

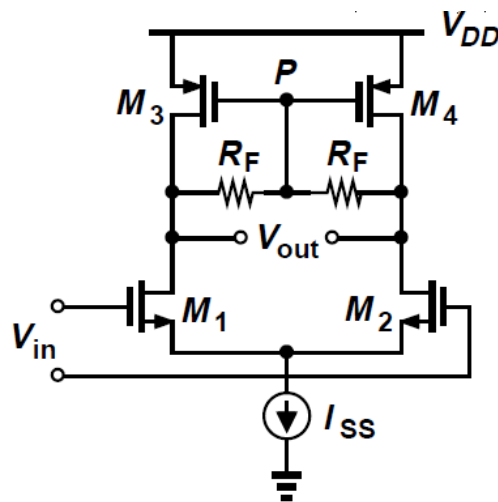



(b)

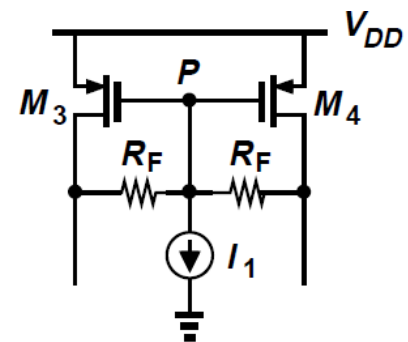

(c)



CMFB in Two-Stage Op Amps

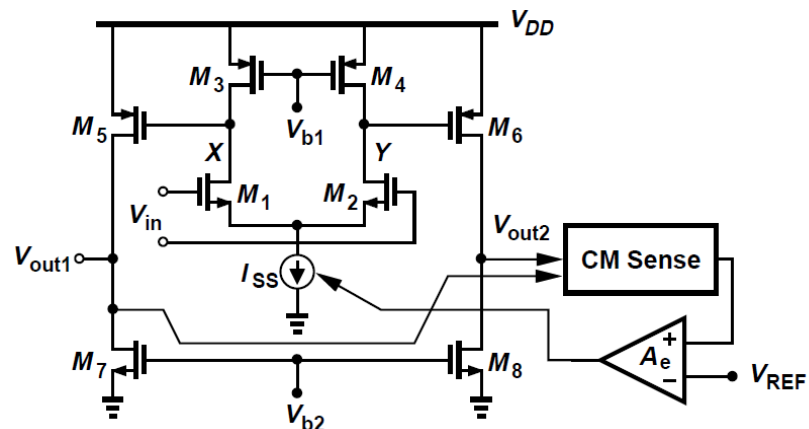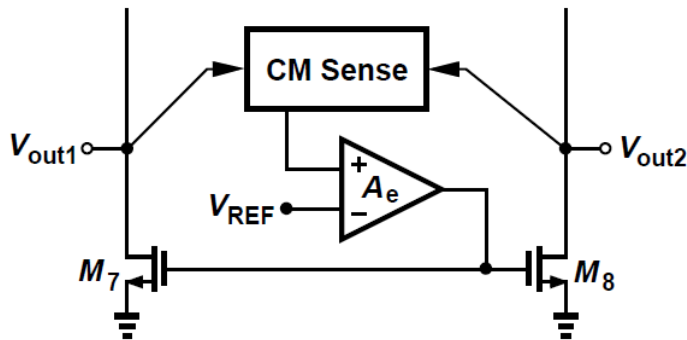- CMFB around second stage (not good)
 - May establish a current beyond nominal value
- CMFB from second stage to first stage
 - Global loop control of both stages



CMFB from Second to First Stage

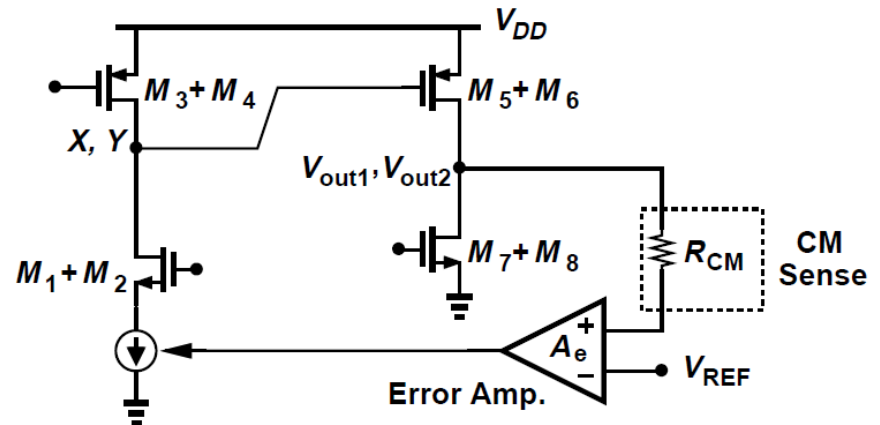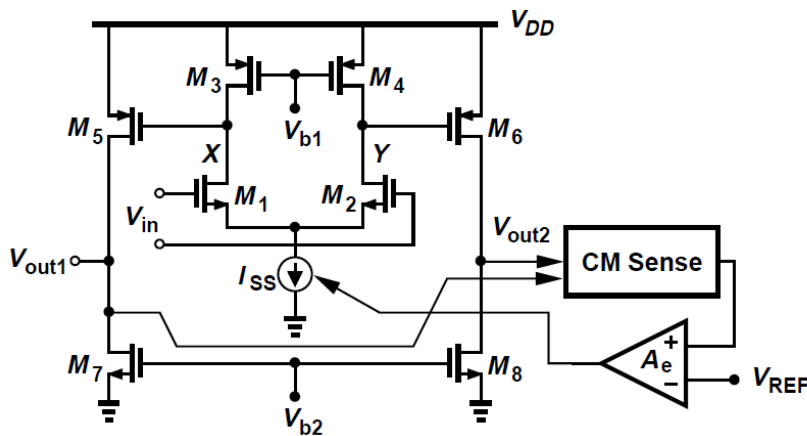
- CMFB from second stage to first stage limitation
 - 3 or 4 poles, which makes it difficult for the loop stable



CMFB at both Stages

- All the drain currents are copied from I_{SS}
- The differential voltage gain is equal to

$$g_{m1}(r_{O1}||r_{O3}||R_1)g_{m5}(r_{O5}||r_{O7}||R_3).$$


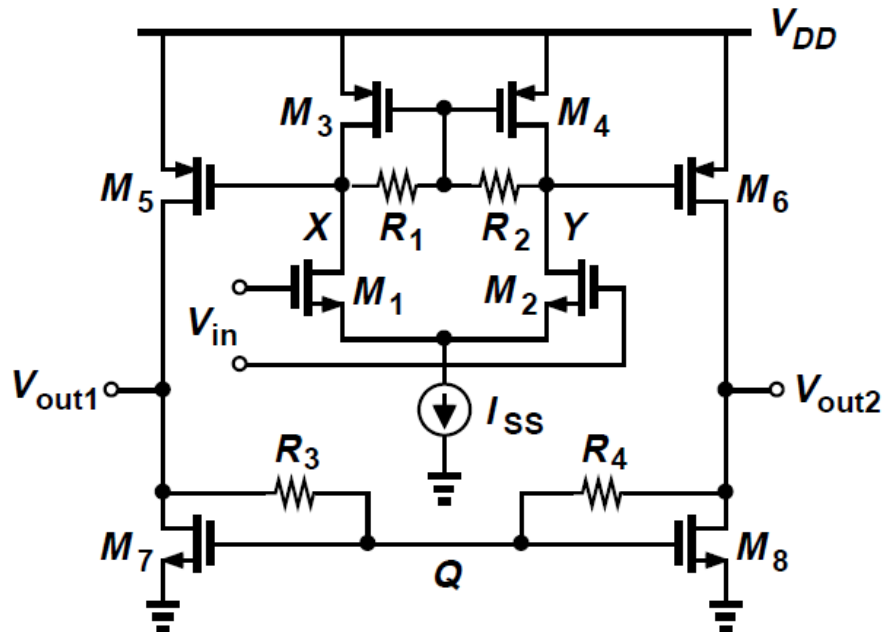


Example 9.21

For the below design explain why the output CM level is inevitably well below $V_{DD}/2$ and hence the output swings are limited. Devise a solution.

Solution:

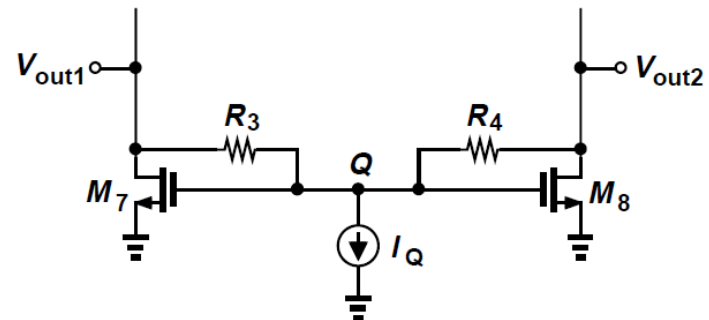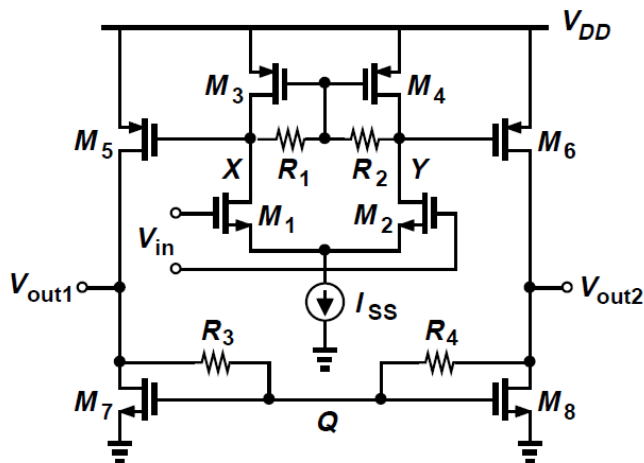The output CM is equal to VG7,8, which is only slightly greater than one threshold. The issue can be resolved by drawing a small current from node Q. It can be upwards to desired output and the device is still in saturation.



CMFB for Cascode First Stage

- First stage use deep triode feedback loop to avoid loading.
- Achieving high gain while not precise

