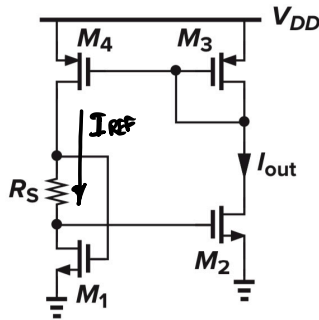


12.1. Derive an expression for  $I_{out}$  in Fig. 12.42.



THE PROBLEM STATEMENT IS NOT COMPLETE, MORE INFORMATION IS NEEDED.

ASSUME  $(W/L)_4 = (W/L)_3 \neq (W/L)_1 \neq (W/L)_2$   
FURTHER ASSUME  
 $\lambda = 0$  FOR ALL DEVICES.

Figure 12.42

$$\begin{aligned}
 I_{REF} &= I_{OUT} \\
 V_{GS1} &= V_{GS2} + I_{REF} R_S \\
 \text{USE SQUARE LAW EQNS. \& SOLVE FOR } V_{GS} \\
 \sqrt{\frac{2I_{OUT}}{\mu_n C_{ox} (W/L)_1}} + V_{TH1} &= \sqrt{\frac{2I_{OUT}}{\mu_n C_{ox} (W/L)_2}} + V_{TH2} + I_{OUT} R_S \\
 \text{ASSUME } V_{TH1} &= V_{TH2} \text{ \& SOLVE FOR } I_{OUT} \\
 \sqrt{\frac{2I_{OUT}}{\mu_n C_{ox}}} \left( \frac{1}{\sqrt{W/L_1}} - \frac{1}{\sqrt{W/L_2}} \right) &= I_{OUT} R_S \\
 \sqrt{I_{OUT}} &= \frac{1}{R_S} \sqrt{\frac{2}{\mu_n C_{ox}}} \left( \frac{1}{\sqrt{W/L_1}} - \frac{1}{\sqrt{W/L_2}} \right) \\
 \boxed{I_{OUT} = \frac{1}{R_S^2} \frac{2}{\mu_n C_{ox}} \left( \sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right)^2}
 \end{aligned}$$

12.2. Explain how the start-up circuit shown in Fig. 12.43 operates. Derive a relationship that guarantees that  $V_X < V_{TH}$  after the circuit turns on.


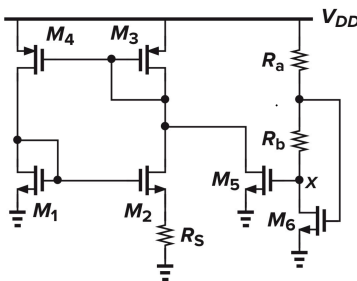


Figure 12.43

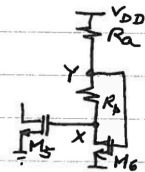12.2 When the circuit turns on, initially both  $M_5$  and  $M_6$  are off and  $V_X$  and  $V_Y$  rise together, i.e.,  $V_X = V_Y$ . When  $V_Y$  reaches  $V_{TH6}$ ,  $V_X$  is also near  $V_{TH5}$ . Thus,  $M_6$  and  $M_5$  turn on almost simultaneously. The surge in the drain current of  $M_5$  turns the rest of the circuit on. As  $V_Y$  increases further,  $V_X$  begins to drop if  $M_6$  is turned on sufficiently because the voltage gain of  $M_6$  and  $R_b$  exceeds unity. For high values of  $V_Y$ ,  $V_X$  can be lower than  $V_{TH5}$ .



Since  $(V_{DD} - I_{D6} R_a - V_{TH})^2 \mu_n C_{ox} (W/L)_6 = I_{D6}$ , we solve the quadratic equation:


$$\begin{aligned}
 R_a^2 I_{D6}^2 - I_{D6} (2 R_a + \frac{C_{VDD-V_{TH}}}{\mu_n C_{ox} (W/L)_6}) + (V_{DD} - V_{TH})^2 &= 0 \\
 \Rightarrow I_{D6} = \frac{2 R_a (V_{DD} - V_{TH}) + \frac{1}{\mu_n C_{ox} (W/L)_6} + \sqrt{[2 R_a (V_{DD} - V_{TH}) + \frac{1}{\mu_n C_{ox} (W/L)_6}]^2 - 4 R_a^2 (V_{DD} - V_{TH})^2}}{2 R_a^2}
 \end{aligned}$$

This value is substituted in the other condition:

$$V_{DD} - I_{D6} (R_a + R_b) \leq V_{TH5}$$

to give the condition for turning off  $M_5$ .

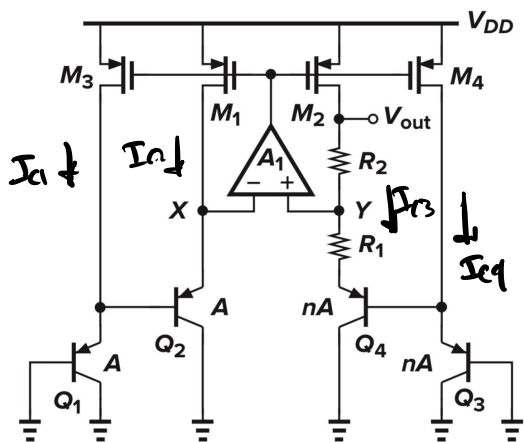**12.5.** In the circuit of Fig. 12.15, assume that  $Q_2$  and  $Q_4$  have a finite current gain  $\beta$ . Calculate the error in the output voltage.



F16 12.15

$$I_C = \beta I_B$$

FIRST FIND  $V_{out}$  WHEN  $\beta = 0$ .

ASSUME  $\left(\frac{w}{L}\right)_3 = \left(\frac{w}{L}\right)_1 = \left(\frac{w}{L}\right)_2 = \left(\frac{w}{L}\right)_4$

\* ASSUME IDEAL OP AMP

$$V_x = V_y \quad \& \quad I_{S,1,2,3,4} = I_S$$

BECAUSE ALL PMOS THE SAME SIZE.

$$I_1 = I_2 = I_3 = I_4 = I_c$$

$$V_X = V_{BE1} + V_{BE2} = \ln\left(\frac{I_C}{I_S}\right) + \ln\left(\frac{I_C}{I_S}\right)$$

$$V_y = V_{BE3} + V_{BE4} + I_C \cdot R_1$$

$$= \ln\left(\frac{I_C}{n I_S}\right) + \ln\left(\frac{I_C}{n I_S}\right) + I_C R_1$$

$$V_x = V_{x'}$$

$$\ln\left(\frac{I_C}{I_S}\right) + \ln\left(\frac{I_C}{I_S}\right) = \ln\left(\frac{I_C}{nI_S}\right) + \ln\left(\frac{I_C}{nI_S}\right) + I_C R_i$$

$$2 \ln(n) \approx I_C R_1$$

$$I_c = \frac{2 \ln(n)}{R_1}$$


$$V_{out} = \frac{R_1}{R_2} 2 \ln(n) + V_{BE3} + V_{BE4}$$

WITH  $\beta$  ERROR

$$I_E = I_C - I_B$$

$$I_E = I_C - \frac{I_C}{\beta}$$
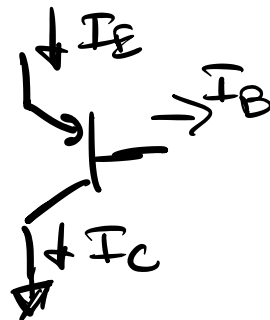
$$= I_C \left(1 - \frac{1}{\beta}\right)$$



$$I_C = I_E \frac{1}{(1 - 1/\beta)} = I_E \frac{(1 + 1/\beta)}{1 - (1/\beta)^2} \quad 1/\beta \ll 1$$

$$\approx I_E (\beta + 1/\beta)$$

$\therefore$  THE ERROR IN  $I_E$  IS

$$I_E = I_C \frac{\beta}{\beta + 1}$$

$\$$  THE ERROR VOLTAGE IS:

$$\Delta V_{out} = \frac{R_2}{R_1} \alpha \ln \left( \frac{\beta}{\beta + 1} \right)$$