

EE473/538 Cadence Lab4

Due Thursday, Feb. 17th, 2022

Kevin Egedy

Lab 4 discusses the design of a single-stage, fully differential op-amp. The input signal is common mode 600mV and AC signal 10uV. The opamp output sits on top of 673.7mV with approximately 150uV AC signal.


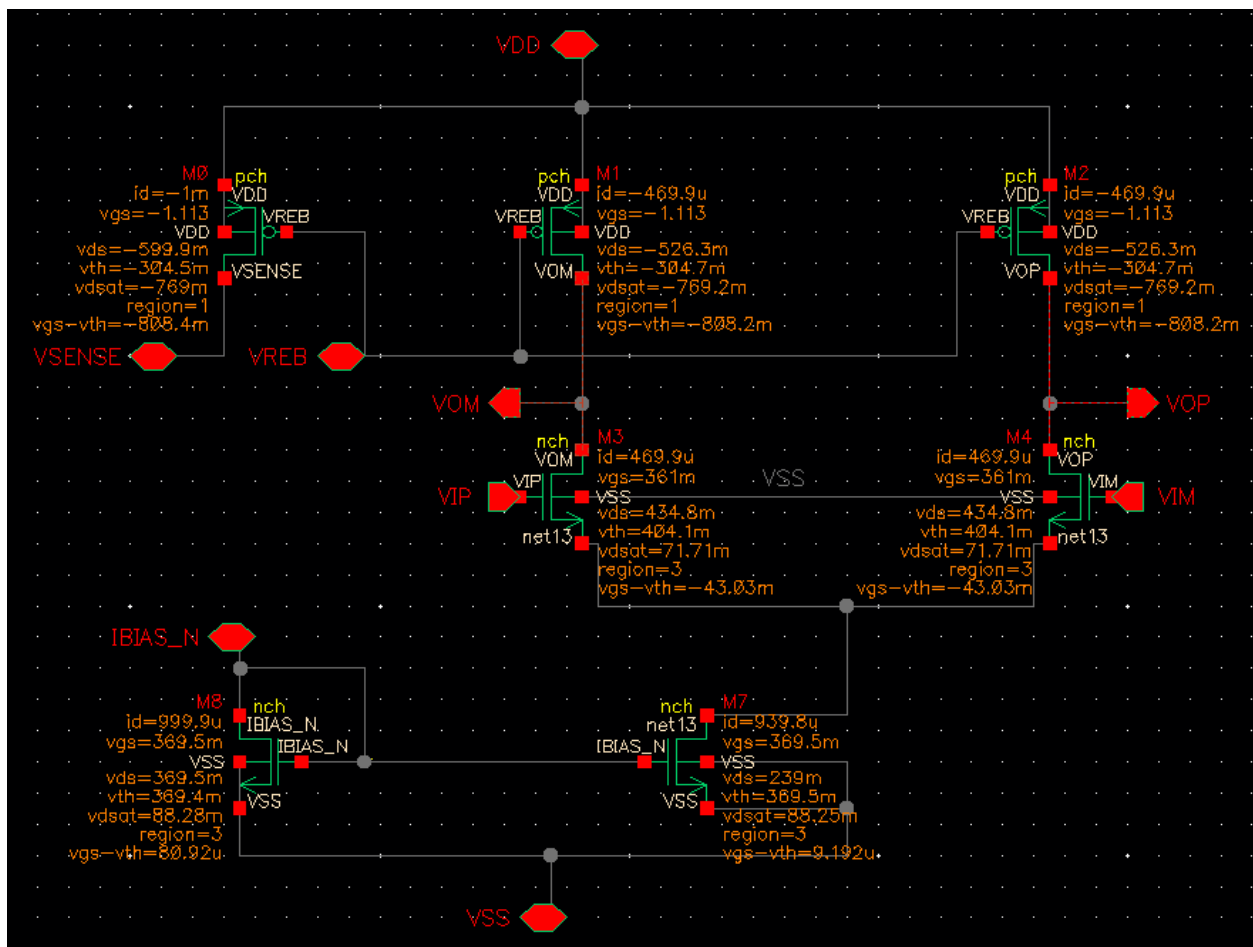
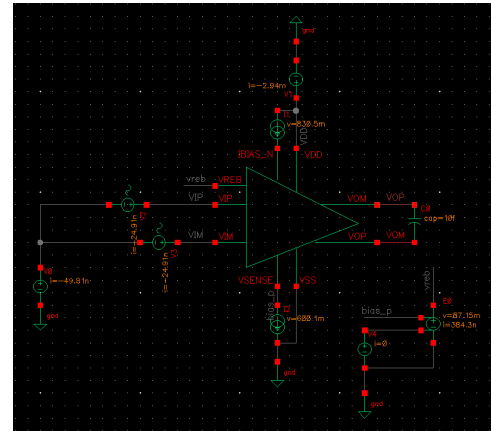
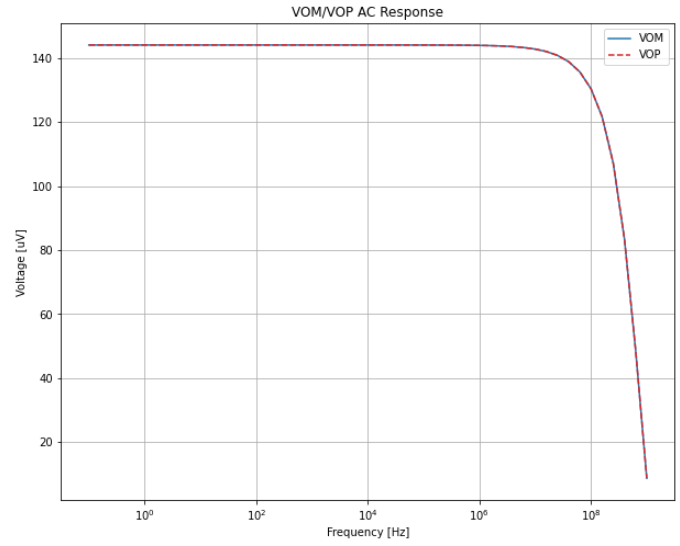


Figure: Amplifier Internal Circuit. PMOS in Triode, NMOS in Saturation

Regions	Device	W	L	Device	$ id $	$ vds $	$ vgs - vth $
0 Cutoff	M0	2u	500n	M0	1m	599.9m	808.4m
	M1	2u	500n	M1	469.9u	526.3m	808.2m
1 Triode	M2	2u	500n	M2	469.9u	526.3m	808.2m
2 Saturation	M3	8u	200n	M3	469.9u	434.8m	43.03m
	M4	8u	200n	M4	469.9u	434.8m	43.03m
3 Subthreshold	M7	8u	200n	M7	939.8u	239m	9.192u
4 Breakdown	M8	8u	200n	M8	999.9u	369.5m	80.92u

 

Given 10uV AC signal, the amplifier small signal gain is approximately 15 V/V from the frequency response. The expected output signal now has an amplitude of 150uV and is evident on the transient response. Note, the amplifier has a small amount of common mode gain because it is no longer sitting at the 600mV input. The AC signal is riding on top of 673.7mV such that the common mode gain is $(673.7\text{mV})/(600\text{mV}) = 1.12$ V/V. The output waveform is from [673.57mv, 673.87mV].