

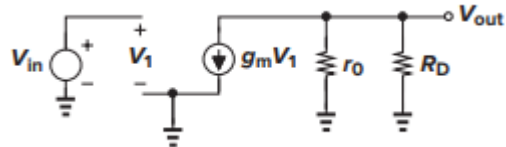


Common Source

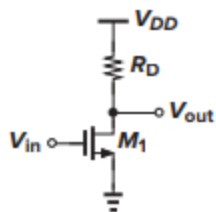

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \frac{V_{RD}}{I_D}$$


Diode Connected Load

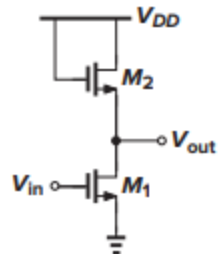

$$A_v = -g_{m1} \frac{1}{g_{m2} + g_{mb2}}$$




$$= -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$
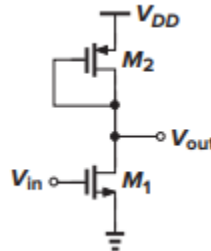
$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$







$$A_v = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}}$$

CS with current-source load

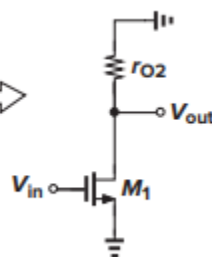
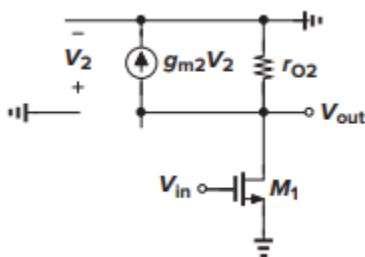
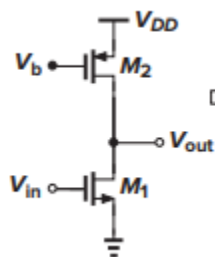


$$A_v = -g_{m1}(r_{O1} \parallel r_{O2})$$

Voltage Swing

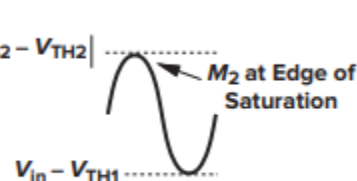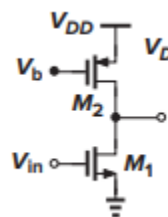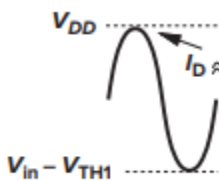
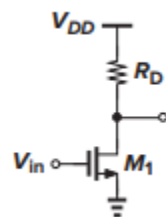


CS with Active Load

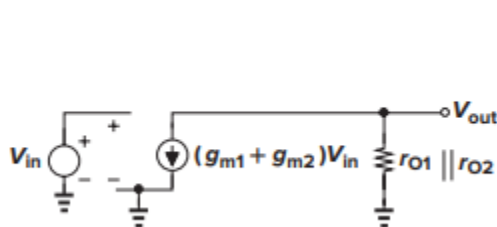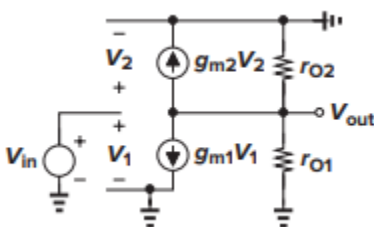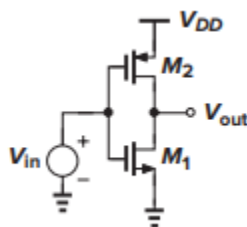

$$A_v = -(g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})$$

CS with Source Degeneration

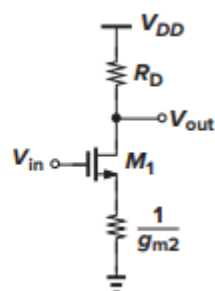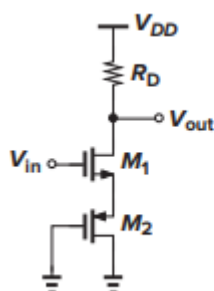

$$G_m = \frac{g_m}{1 + g_m R_S}$$



$$A_v = -G_m R_D$$

$$= \frac{-g_m R_D}{1 + g_m R_S}$$

$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$


$$A_v = -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

Source Follower

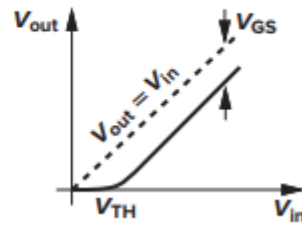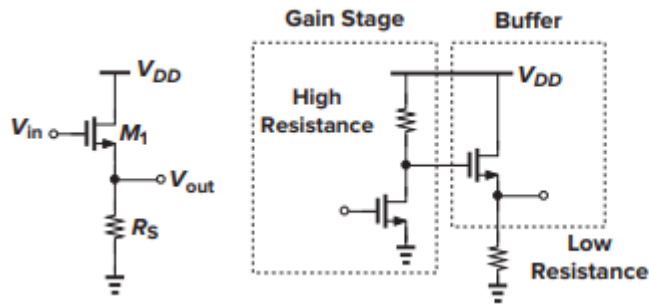

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

Cascode

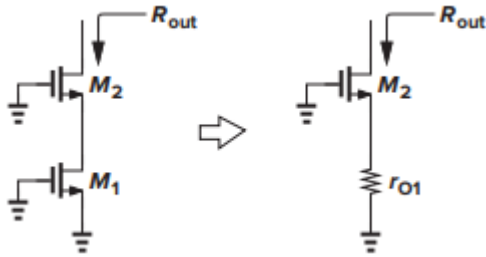

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2}$$

Assuming $g_m r_O \gg 1$, we have $R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$.

A. Negative-TC Voltage (CTAT)

For a bipolar device, the forward voltage of a pn -junction diode exhibits a negative TC.

$$I_C = I_s \exp(V_{BE}/V_T) \text{ where } V_T = \frac{kT}{q}$$

$$I_s = bT^{4+m} \exp(-\frac{E_g}{kT})$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_s}\right)$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln\left(\frac{I_C}{I_s}\right) - \frac{V_T}{I_s} \frac{\partial I_s}{\partial T}$$

$$\frac{V_T}{I_s} \frac{\partial I_s}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T$$

$$\begin{aligned} \frac{\partial V_{BE}}{\partial T} &= \frac{V_T}{T} \ln\left(\frac{I_C}{I_s}\right) - (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T \\ &= \frac{V_{BE} - (4+m)V_T - E_g/q}{T} \end{aligned}$$

Thus, at $T = 300K$ and $V_{BE} \approx 750mV$, the change in TC voltage with respect to temperature is $\partial V_{BE}/\partial T \approx -1.5mV$.

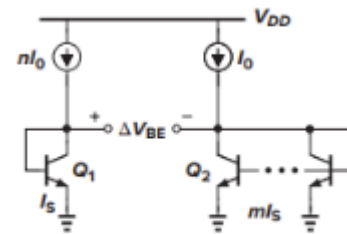


Fig. 1. PTAT Circuit

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln\left(\frac{nI_0}{I_s}\right) - V_T \ln\left(\frac{I_0}{mI_s}\right)$$

$$= V_T \ln(nm)$$

$$= \frac{kT}{q} \ln(nm)$$

$$\frac{\partial}{\partial T} \Delta V_{BE} = \frac{\partial}{\partial T} \frac{kT}{q} \ln(nm)$$

$$= \frac{k}{q} \ln(nm)$$

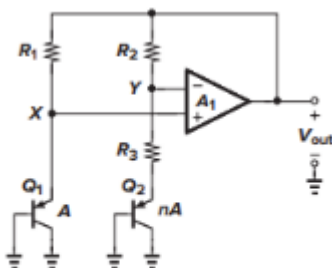


Fig. 2. Practical Bandgap Implementation

$$V_{REF} = \alpha_1 V_{BE} + \alpha_2 V_T \ln(nm)$$

For simplicity, α_1 is chosen to be 1. Then V_{REF} is

$$V_{REF} = V_{BE} + \alpha_2 V_T \ln(m)$$



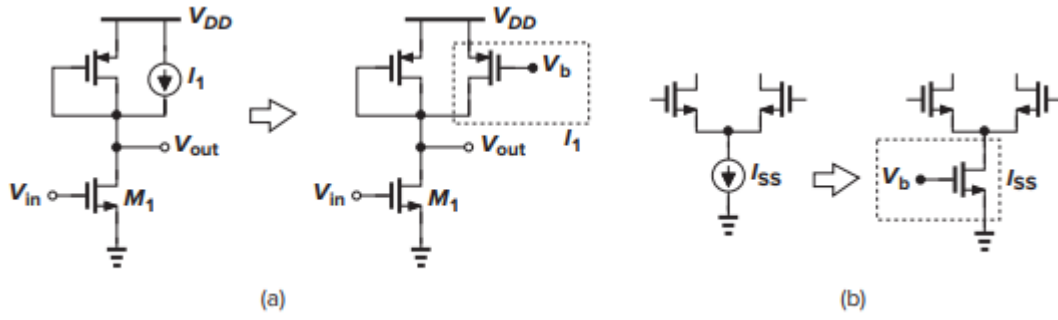


Figure 5.1 Applications of current sources.

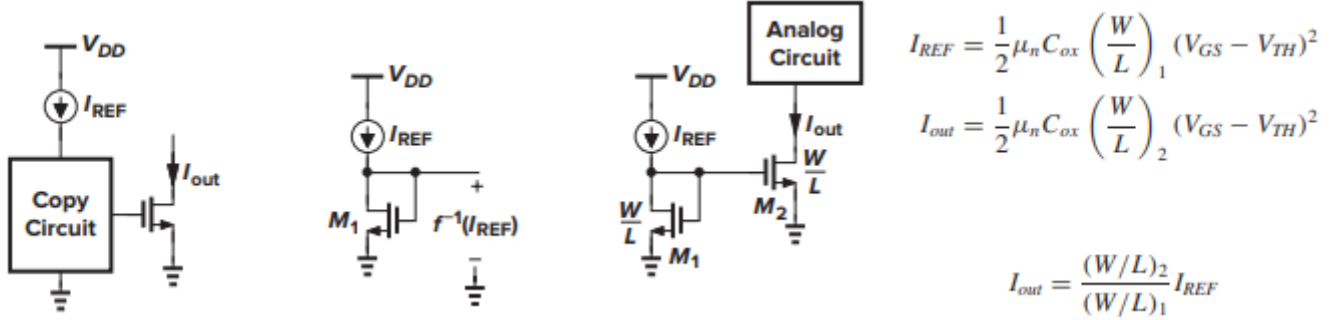

It is important to appreciate the cause-and-effect relationships stipulated by $V_{GS} = f^{-1}(I_{REF})$ and $f[f^{-1}(I_{REF})] = I_{REF}$. The former suggests that we must *generate* a V_{GS} from I_{REF} ; i.e., I_{REF} is the cause and V_{GS} is the effect. A MOSFET can perform this function only if it is configured as a diode while carrying a current of I_{REF} [M_1 in Fig. 5.5(b)]. Similarly, the latter equation indicates that a transistor must sense $f^{-1}(I_{REF}) (= V_{GS})$ and generate $f[f^{-1}(I_{REF})]$. In this case, the cause is V_{GS} and the effect is the output current, $f[f^{-1}(I_{REF})]$ [as provided by M_2 in Fig. 5.5(b)].

$$|I_{D4}| = \alpha \beta I_{REF}, \alpha = \frac{(W/L)_2}{(W/L)_1}, \beta = \frac{(W/L)_4}{(W/L)_3}$$

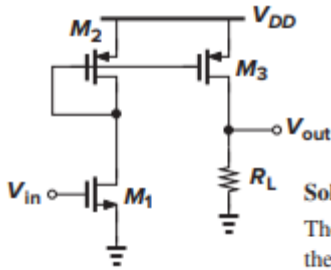

Solution

The small-signal drain current of M_1 is equal to $g_{m1} V_{in}$. Since $I_{D2} = I_{D1}$ and $I_{D3} = I_{D2} (W/L)_3 / (W/L)_2$, the small-signal drain current of M_3 is equal to $g_{m1} V_{in} (W/L)_3 / (W/L)_2$, yielding a voltage gain of $g_{m1} R_L (W/L)_3 / (W/L)_2$.

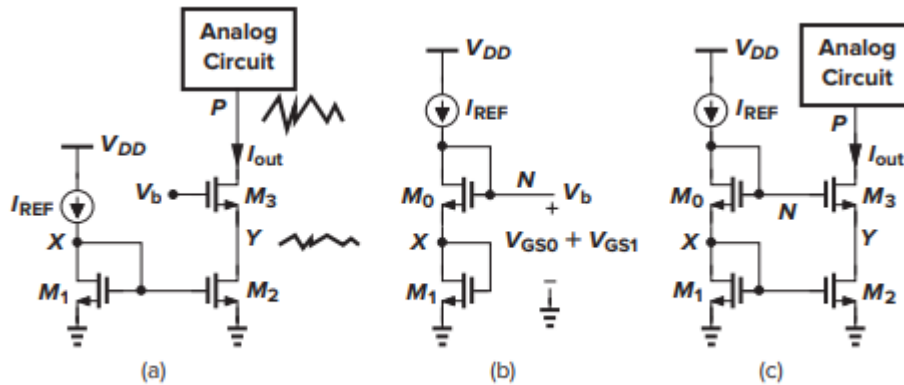
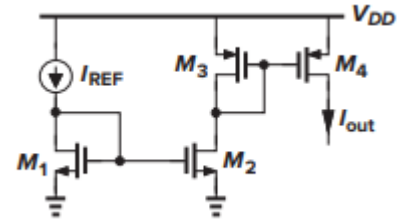


Figure 5.12 (a) Cascode current source, (b) modification of mirror circuit to generate the cascode bias voltage, and (c) cascode current mirror.

$$V_N = V_{GS0} + V_{GS1}$$

$$= \sqrt{\frac{2I_{REF}}{\mu_n C_{ox}}} \left[\sqrt{\left(\frac{L}{W} \right)_0} + \sqrt{\left(\frac{L}{W} \right)_1} \right] + V_{TH0} + V_{TH1}$$


$$V_Y = V_X \approx \sqrt{2I_{REF} / [\mu_n C_{ox} (W/L)_1]} +$$

Table 7.4 Characteristics of MOSFET Amplifiers


Amplifier type	Characteristics ^a				
	R_{in}	A_{v_o}	R_o	A_v	G_v
Common source (Fig. 7.35)	∞	$-g_m R_D$	R_D	$-g_m(R_D \parallel R_L)$	$-g_m(R_D \parallel R_L)$
Common source with R_s (Fig. 7.37)	∞	$-\frac{g_m R_D}{1 + g_m R_s}$	R_D	$\frac{-g_m(R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$	$-\frac{g_m(R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$
Common gate (Fig. 7.39)	$\frac{1}{g_m}$	$g_m R_D$	R_D	$g_m(R_D \parallel R_L)$	$\frac{R_D \parallel R_L}{R_{sig} + 1/g_m}$
Source follower (Fig. 7.42)	∞	1	$\frac{1}{g_m}$	$\frac{R_L}{R_L + 1/g_m}$	$\frac{R_L}{R_L + 1/g_m}$

^a For the interpretation of R_{in} , A_{v_o} , and R_o , refer to Fig. 7.34(b).


Common Emitter

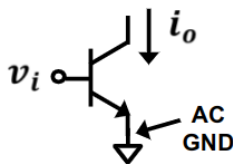


Common Base

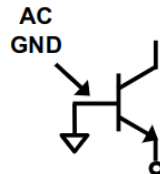


Common Collector or "Emitter Follower"

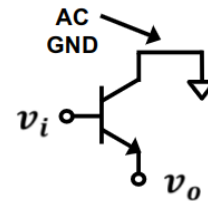

Common Source

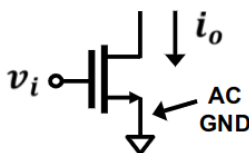

Common Gate

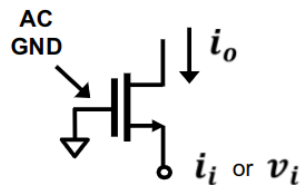

Common Drain or "Source Follower"

