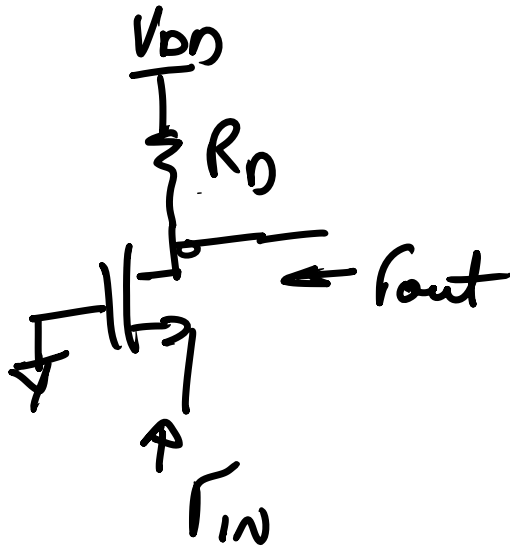


Lecture #7, Jan 21st, 2022


- Review Chapter 1 and 2 of Razavi book as needed. Course will start with Chapter 3.
- Moving to Chapter 12 next – Bandgap References.
- CAD 2 due next Tuesday, Jan 25th.
- Homework 1 out, due today.
- Homework 2 and Project 1 coming shortly.
- Class will be virtual next week.
- Discuss Single-Transistor Amplifier Configurations
 - Common-Gate Amplifier.
 - Common-Drain Amplifier.
 - Example problem.

Common-Gate Amplifier



$$r_{out} = (g_{ds} // g_D)^{-1}$$

$$= r_{ds} // R_D \approx R_D$$

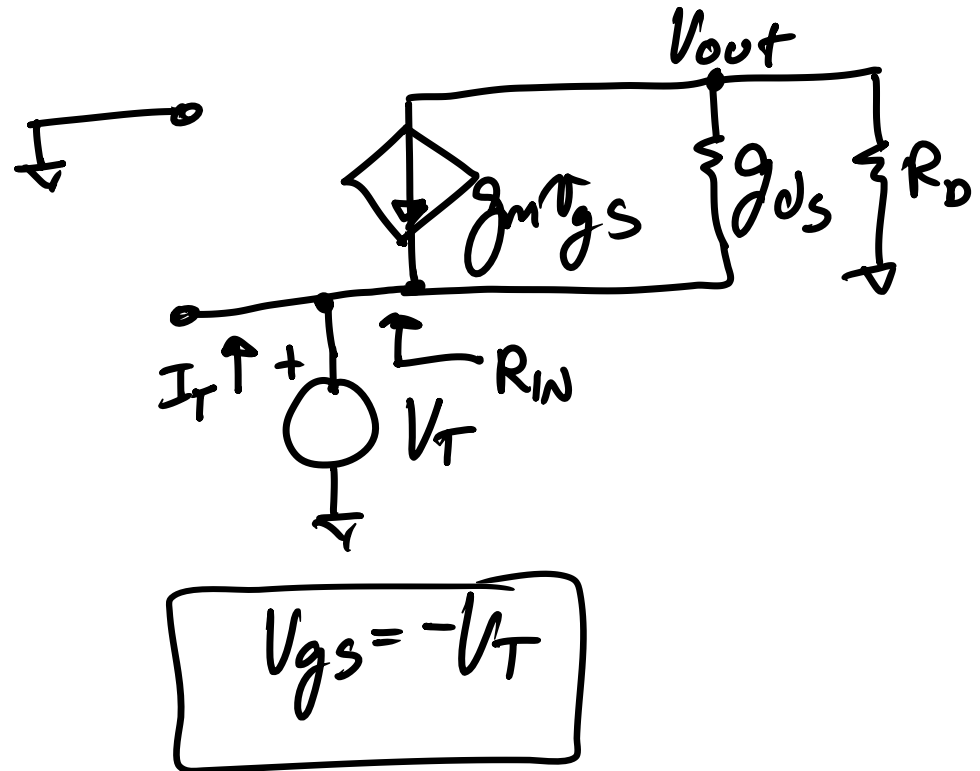

R_{IN} : APPLY TEST SOURCE .

KCL @ V_{IN}

ON NEXT PAGE.

KCL @ V_{out} Common-Gate Amplifier

$$\dot{I}_T + g_m V_{gs} + (V_{out} - V_T) g_{ds} = 0$$

$$\dot{I}_T - g_m V_T + \underbrace{V_{out} g_{ds} - V_T g_{ds}}_{\text{CAN WRITE IN TERMS OF } V_T} = 0$$

$$\dot{I}_T - g_m V_T + \underbrace{V_T \frac{g_m + g_{ds}}{g_{ds} + g_o}}_{\text{VOLTAGE GAIN OF CG}} \cdot g_{ds} = 0$$

$$\dot{I}_T = V_T \left(g_m + g_{ds} + \frac{g_m + g_{ds}}{g_{ds} + g_o} \right) V_T$$

$$\begin{aligned} r_{\pi} = \frac{V_T}{\dot{I}_T} &= \frac{g_{ds} + g_o}{(g_m + g_{ds})(g_{ds} + g_o) + g_m + g_{ds}} \\ &= \frac{g_{ds} + g_o}{g_o(g_m + g_{ds})} \end{aligned}$$

Common-Gate Amplifier

$$g_m \gg g_{ds}$$

if $g_{ds} \ll g_D$ ($R_{DS} \gg R_D$, e.g. RESISTIVE LOAD)



$$\text{THEN } r_{in} \approx \frac{g_D}{g_D g_m} = \frac{1}{g_m}$$

SAME AS BJT, EXCEPT ~~THAT~~ FOR SAME CURRENT

$$g_{m_{mos}} < g_{m_{BJT}} \quad \checkmark$$

$$r_{in_{mos}} > r_{in_{BJT}}$$

Common-Gate Amplifier

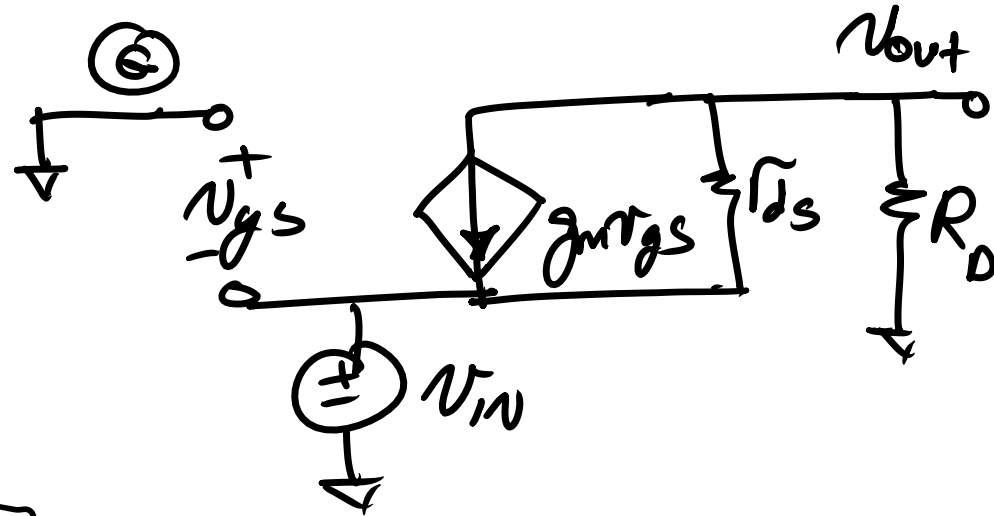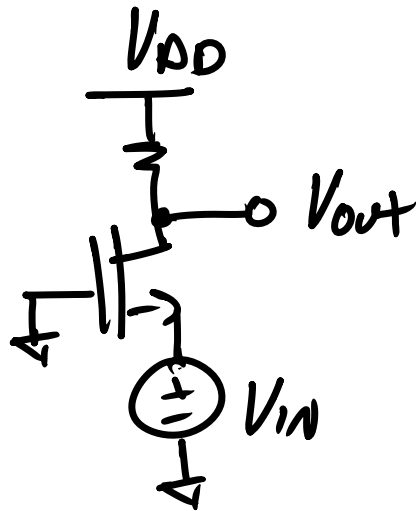

NOTICE $V_{gs} = -V_{in}$

KCL @ V_{out}


$$g_m V_{gs} + g_{ds} (V_{out} - V_{in}) + g_o V_{out} = 0$$

$$-g_m V_{in} + g_{ds} V_{out} - g_{ds} V_{in} + g_o V_{out} = 0$$

$$A_v = \frac{+(g_m + g_{ds})}{g_{ds} + g_o}$$

$$g_m \neq g_o \ll g_{ds} \therefore A_v \approx g_m / g_o$$

Common-Drain Amplifier

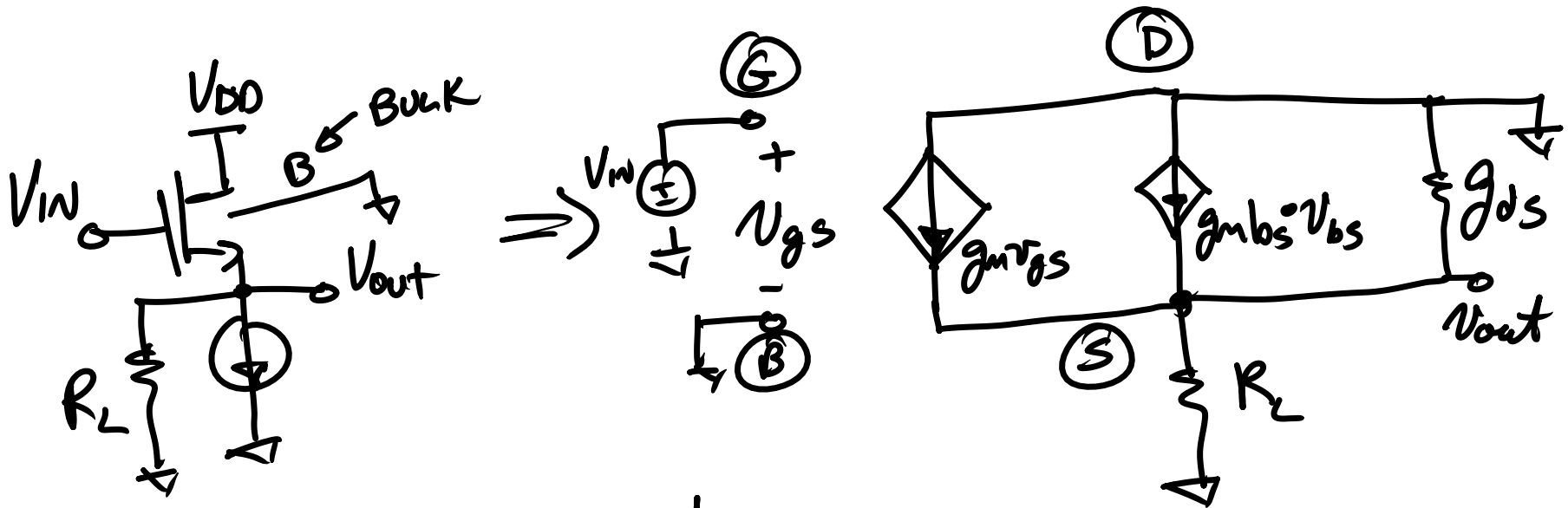

$$V_{gs} = V_m - V_{out}; \quad V_{bs} = V_b - V_s = 0 - V_{out}$$

KCL @ V_{out} :

$$g_m V_{gs} + g_{mbs} V_{bs} = g_L V_{out} + g_{ds} V_{out}$$

$$g_m (V_m - V_{out}) + g_{mbs} (0 - V_{out}) = (g_L + g_{ds}) V_{out}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m}{g_m + g_{mbs} + g_{ds} + g_L} \quad \text{av.}$$

Common-Drain Amplifier Output Resistance

$$A_v \approx 1$$
$$g_m \gg g_{mbs} \gg g_{ds} \quad \text{or} \quad g_{ds} = 1/r_{ds}$$

BY INSPECTION =

$$g_{out} = g_m + g_{mbs} + g_{ds} + g_L$$

\Rightarrow LOW OUTPUT RESISTANCE.