

Lecture #3, Jan 10th, 2022


- Review Chapter 1 and 2 of Razavi book as needed. Course will start with Chapter 3. Read and Review Chapter 3.1 – 3.5
- Homework #1 & CAD 1 coming.
- Discuss Single-Transistor Amplifier Configurations
 - Common-Source Amplifier
 - Common-Source w/ Active Load
 - Common-Source w/ Degeneration
 - Common-Gate Amplifier
 - Common-Drain Amplifier

Chapter 3: Single-Transistor Amps

Three Basic Amplifier Configurations

Assume devices are properly biased in saturation Region


Common Source

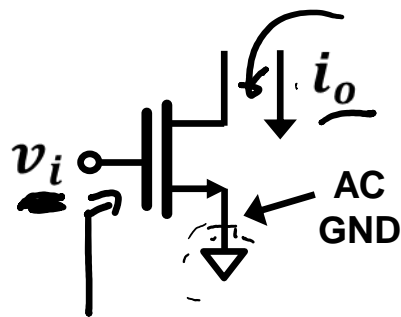

R_i

- WANT R_i LARGE
- WANT R_o LARGE

Common Gate

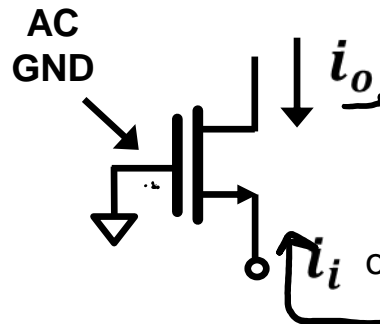


- IF I WANT R_i LOW

- IF I WANT R_o HIGH

$$R_i \approx \frac{1}{g_m} \approx \frac{(V_{GS} - V_{th})}{2I_D}$$

$$R_i = 50\Omega = \frac{(V_{GS} - V_{th})}{2I_D}$$


Common Drain or "Source Follower"

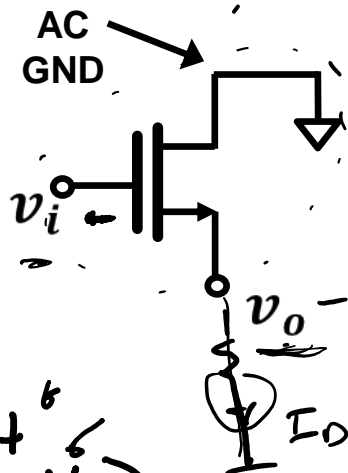

$$a_v = \frac{v_o}{v_i} = 1$$

Common-Source amplifier w/ Resistive load


A Large-Signal Perspective

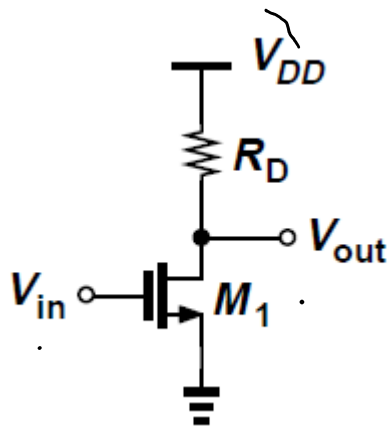


- Very high input impedance at low frequencies
- For $V_{in} < V_{TH}$, M_1 is off and $V_{out} = V_{DD}$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

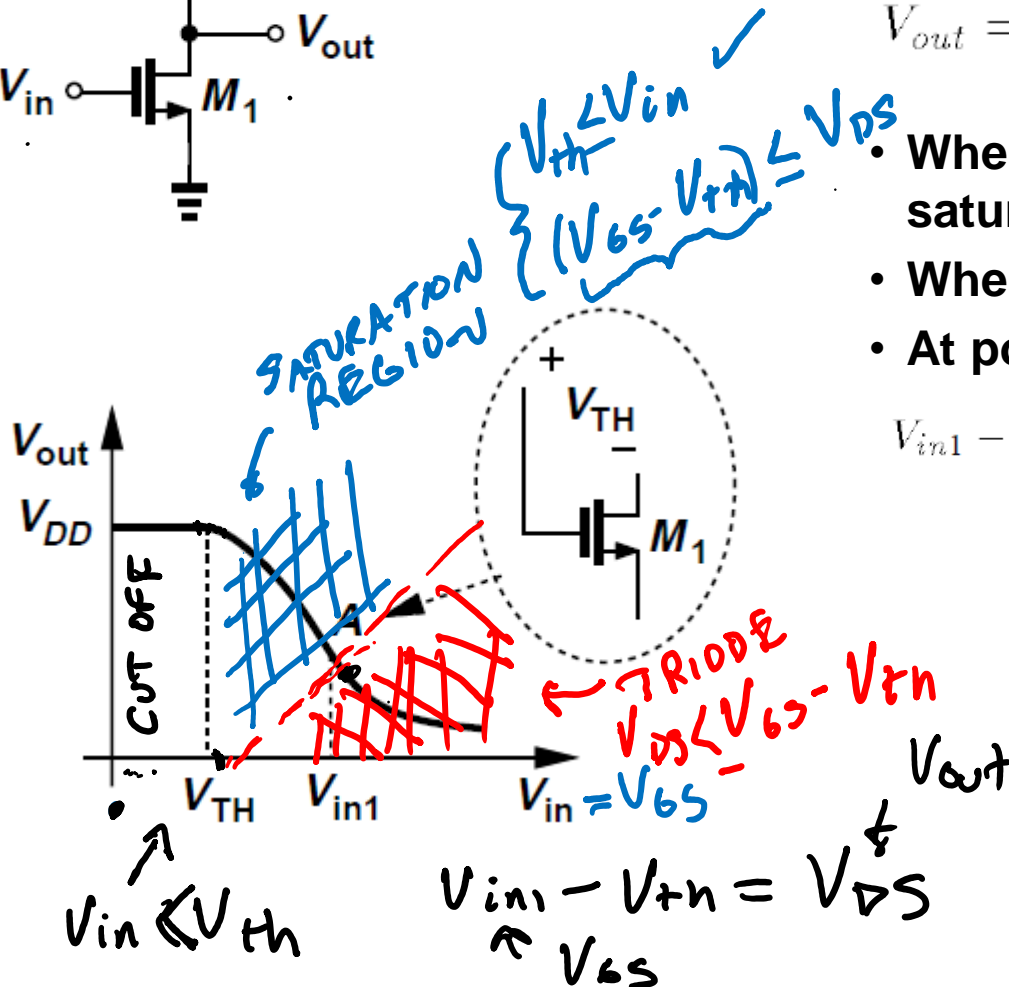- When $V_{in} > V_{TH}$, M_1 turns on in saturation region, V_{out} falls
- When $V_{in} > V_{in1}$, M_1 enters triode region
- At point A, $V_{out} = V_{in1} - V_{TH}$




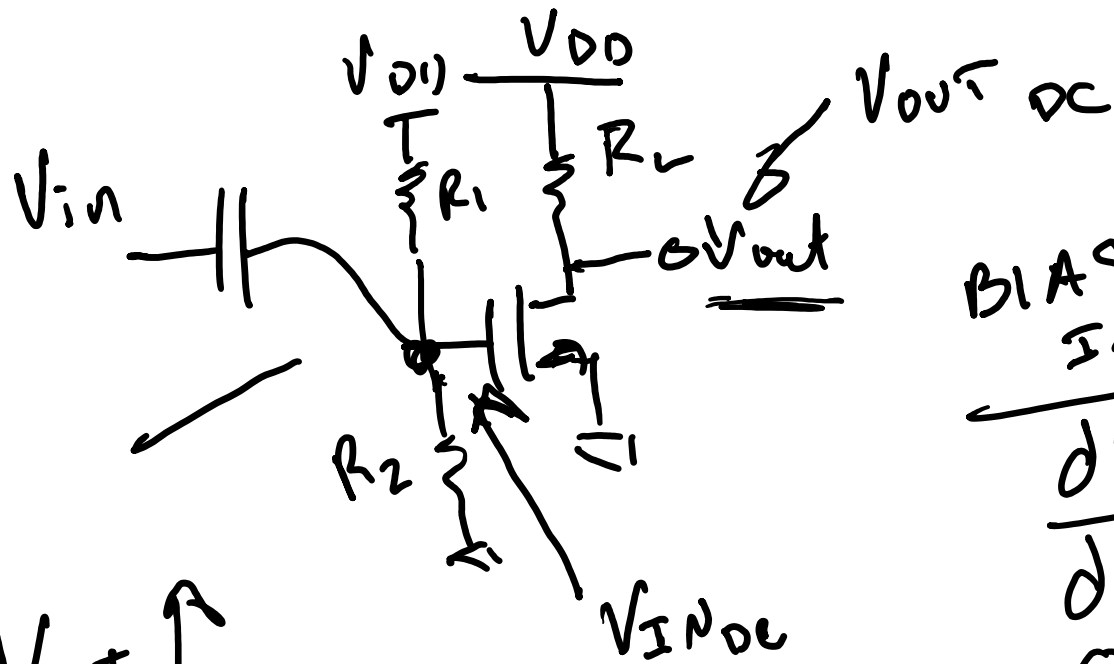

BIAS POINT INFLUENCES



$$\frac{dV_{out}}{dV_{in}} = \underline{A_v}$$

- ① HIGH GAIN
- ② HIGH OUTPUT SWING.

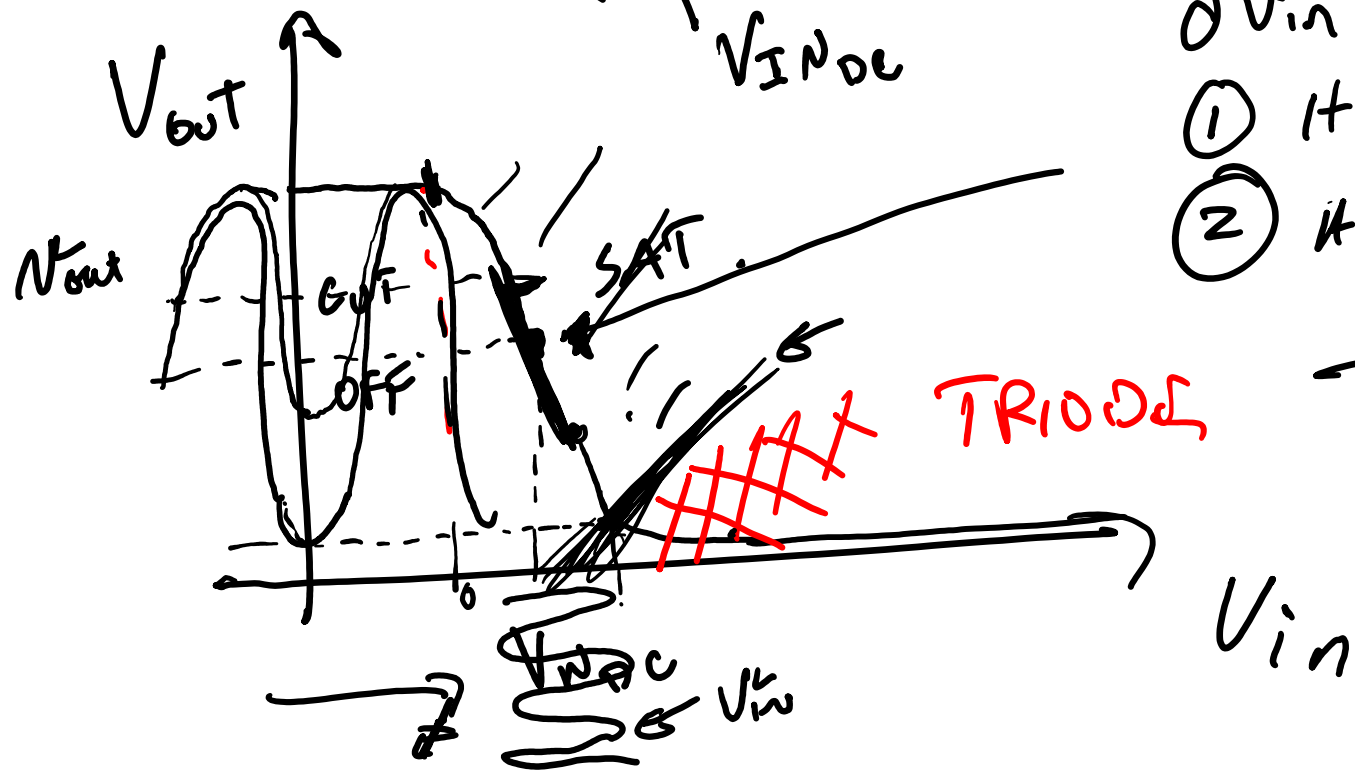

Common-Source amplifier w/ Resistive load

A Large-Signal Perspective

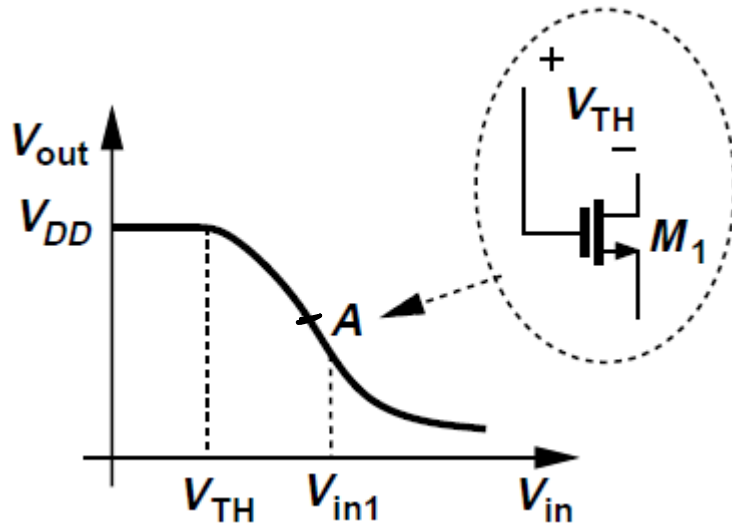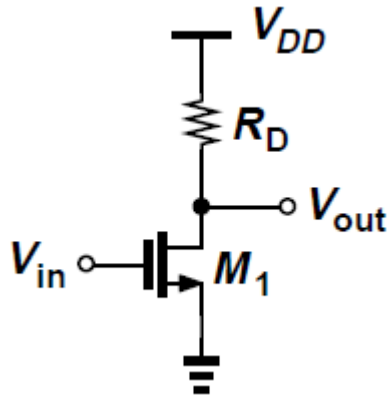


- Very high input impedance at low frequencies
- For $V_{in} < V_{TH}$, M_1 is off and $V_{out} = V_{DD}$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$
- When $V_{in} > V_{TH}$, M_1 turns on in saturation region, V_{out} falls
- When $V_{in} > V_{in1}$, M_1 enters triode region
- At point A, $V_{out} = V_{in1} - V_{TH}$


$$V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$$
- Note: The VTC defines the output voltage range or the “Output Swing” of the amplifier. In this example, the amplifier output can swing from $V_{OUT(min)} = V_{dsat}$ to $V_{OUT(max)} = V_{DD}$ & M_1 will remain in saturation.

Common-Source Small-Signal Gain, R_i and R_o


AC + DC Circuit

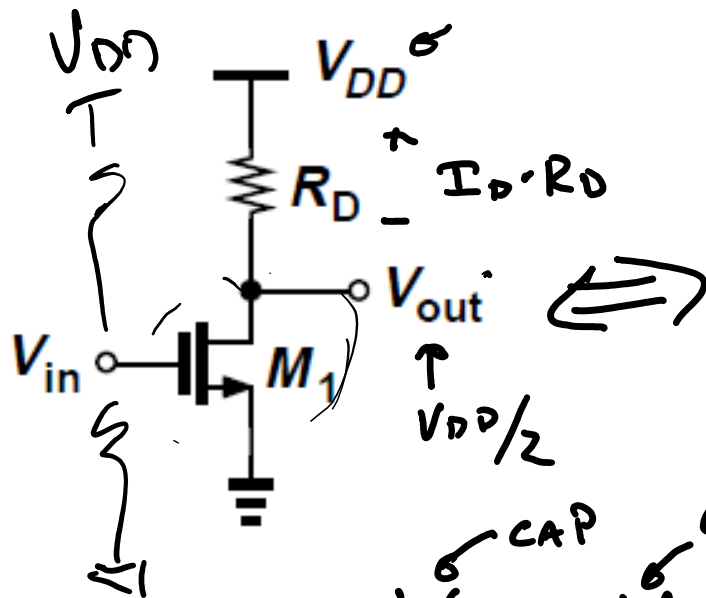

DC Circuit

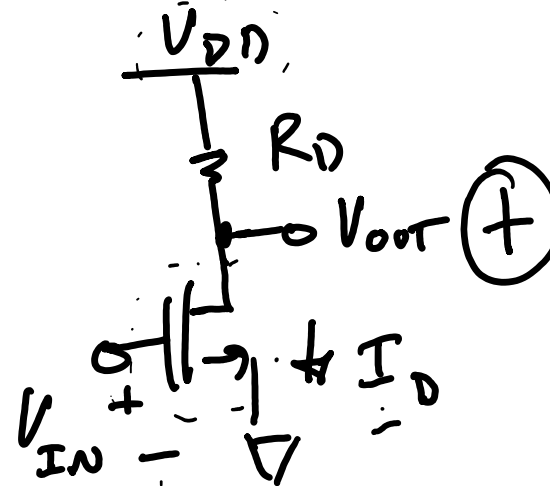

AC Circuit - SS

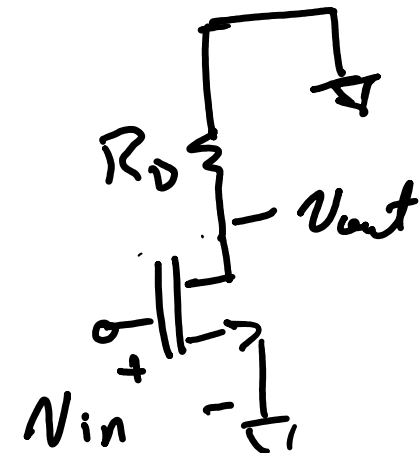

$$V_{in} = V_{IN} + v_{in}$$


Labels: V_{IN} is the DC bias voltage, v_{in} is the small-signal input voltage. The input is labeled as a capacitor C_{AP} and a low-pass filter (LWPF).

Step 1) DC Analysis to find DC I_D , $V_{GS} - V_{TH}$, V_{DS} , DC values used to find small-signal values such as g_m , r_o , g_{mb} , etc.

Common-Source Small-Signal Signal Analysis

Step 1) DC Analysis to find DC I_D , $V_{GS} - V_{TH}$, V_{DS} , DC values used to find small-signal values such as g_m , r_o , g_{mb} , etc.

SMALL-SIGNAL

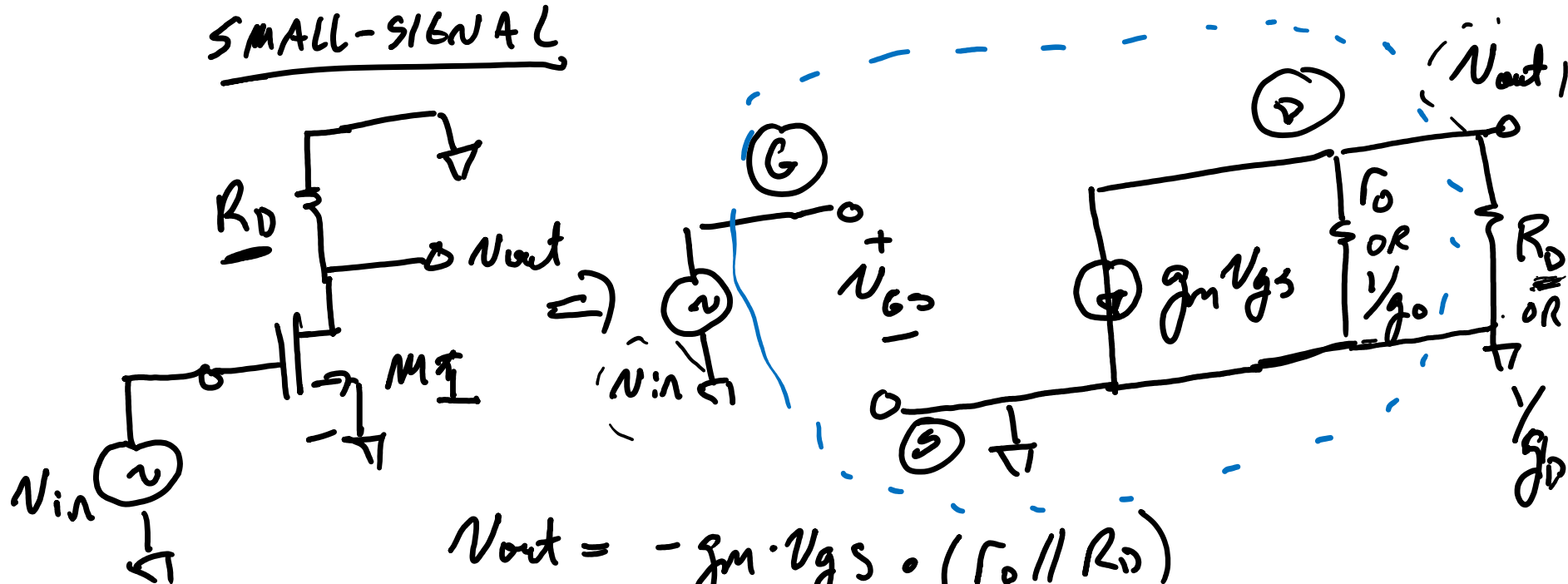

$$v_{out} = -g_m \cdot v_{gs} \cdot (r_o \parallel R_D)$$

$$v_{out} = -g_m \cdot v_{in} \cdot \left(\frac{1}{r_o} + \frac{1}{R_D} \right) \quad \text{EX: } R_D \ll r_o$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot \left(\frac{1}{r_o} + \frac{1}{R_D} \right) = -g_m \cdot \frac{r_o R_D}{r_o + R_D} \approx -g_m \cdot R_D$$

$$a_v \approx -g_m \cdot R_D \approx -\frac{2I_D}{(V_{GS} - V_{th})} \cdot R_D$$

$$\approx -\frac{2}{(V_{GS} - V_{th})} \cdot \underbrace{(I_D \cdot R_D)}_{\substack{\text{VOLTAGE DROP} \\ \text{ACROSS } R_D}}$$


$$V_{out} \approx \frac{V_{DD}}{2} \\ = V_{DD} - \underbrace{I_D \cdot R_D}$$

$$\approx -\frac{V_{DD}}{(V_{GS} - V_{th})} \approx -10 \text{ V/V}$$

$I_D \cdot R_D = V_{DD}/2$
 \uparrow 200 mV

TECH. SCALING
 $V_{DD} \downarrow \dots 1 \text{ V} \downarrow \} \Rightarrow \approx -5 \text{ V/V}$

• COMPARISON TO BJT.

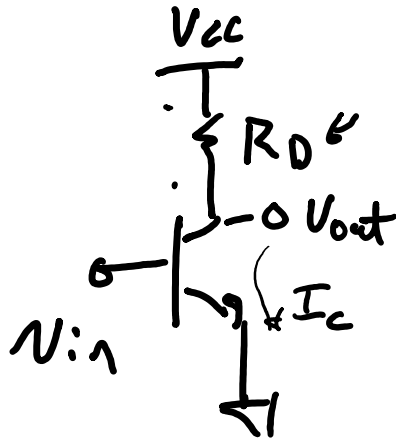


$$\frac{a_v(\text{BJT})}{a_v(\text{MOS})} = \frac{-V_{CC}/2V_T}{-\frac{V_{DD}}{(V_{GS} - V_{th})}} \approx \frac{(V_{GS} - V_{th})}{2V_T}$$

$V_T \approx 25 \text{ mV}$
 50 mV

\therefore BJT GAIN IS TYPICALLY 4x-5x

CMOS Intrinsic Gain

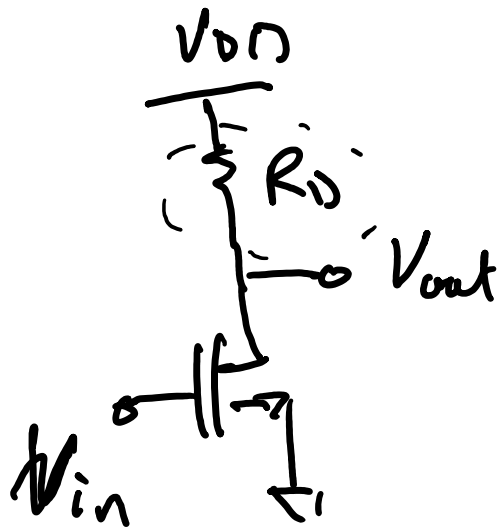



\Rightarrow

LOOK AT

IDEAL CASE

$$R_D \rightarrow \infty$$

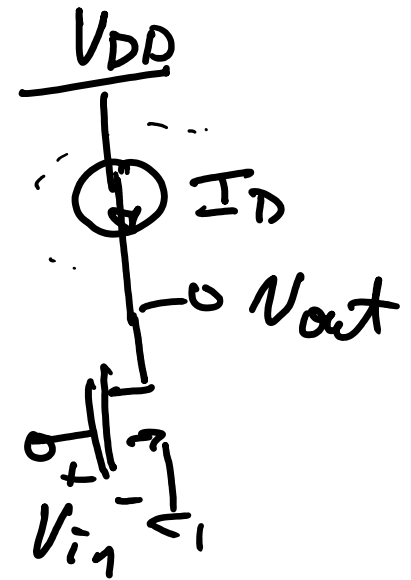

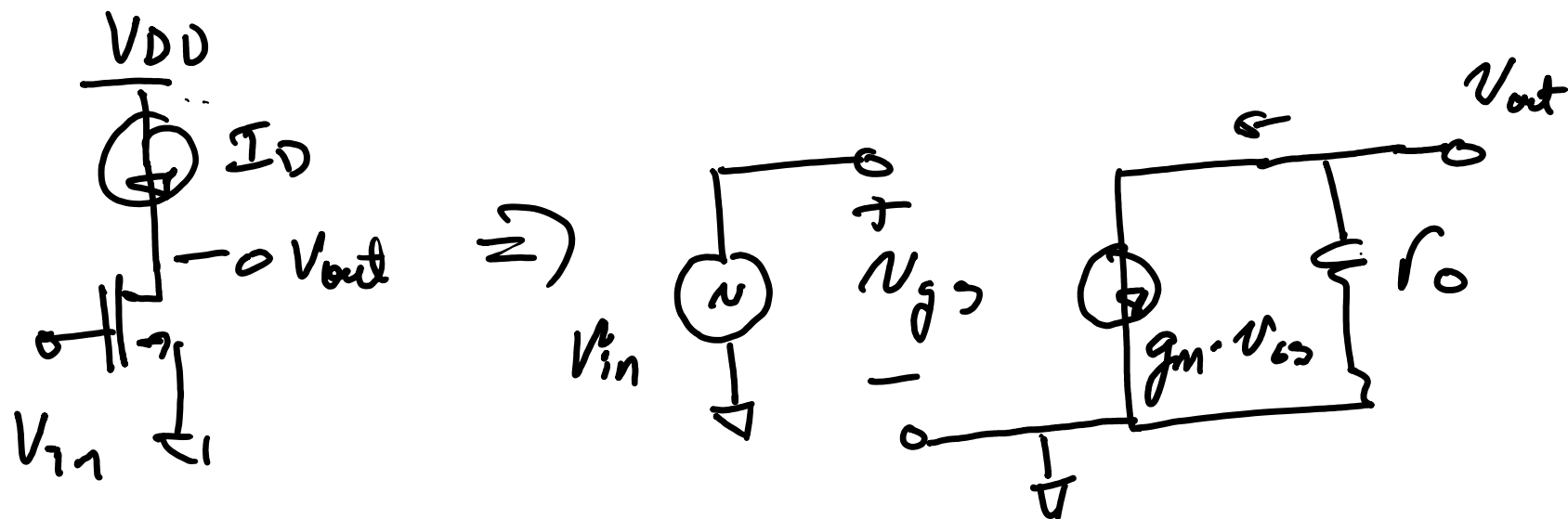


$$V_{out} = -g_m \cdot \underbrace{v_{gs}}_{V_{in}} \cdot r_o \quad V_{gs} = V_{in}$$

$$A_v = -g_m \cdot r_o$$

← DEVICE
INTRINSIC
GAIN

MOSFET Gain Limitations

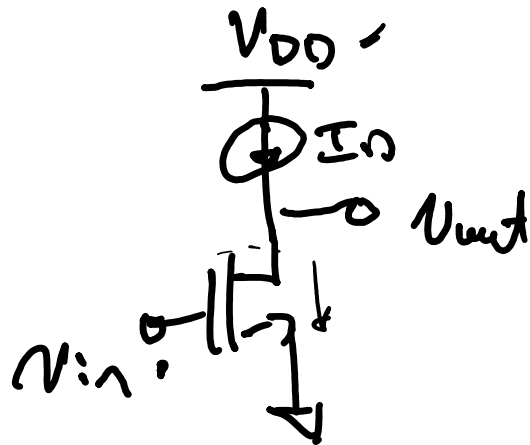

$$A_v = -g_m \cdot r_o$$

$$A_v = - \frac{g_m}{\lambda I_D}$$

$$g_m = \sqrt{2K_n' (W/L) I_D}$$


$$r_o = \frac{1}{\lambda I_D}$$

λ : TECH DEP.

SUBTHRESHOLD HOLD
OR WEAK INVERSION

$$A_v \propto \frac{1}{\sqrt{I_D}}$$

$\log A_v$

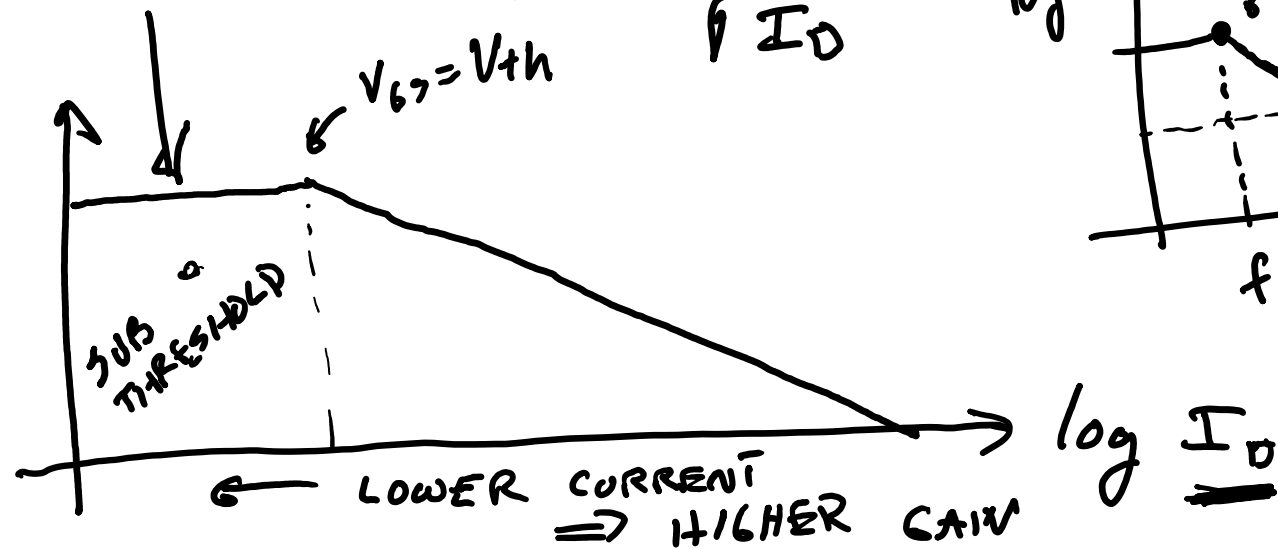

GBWP

