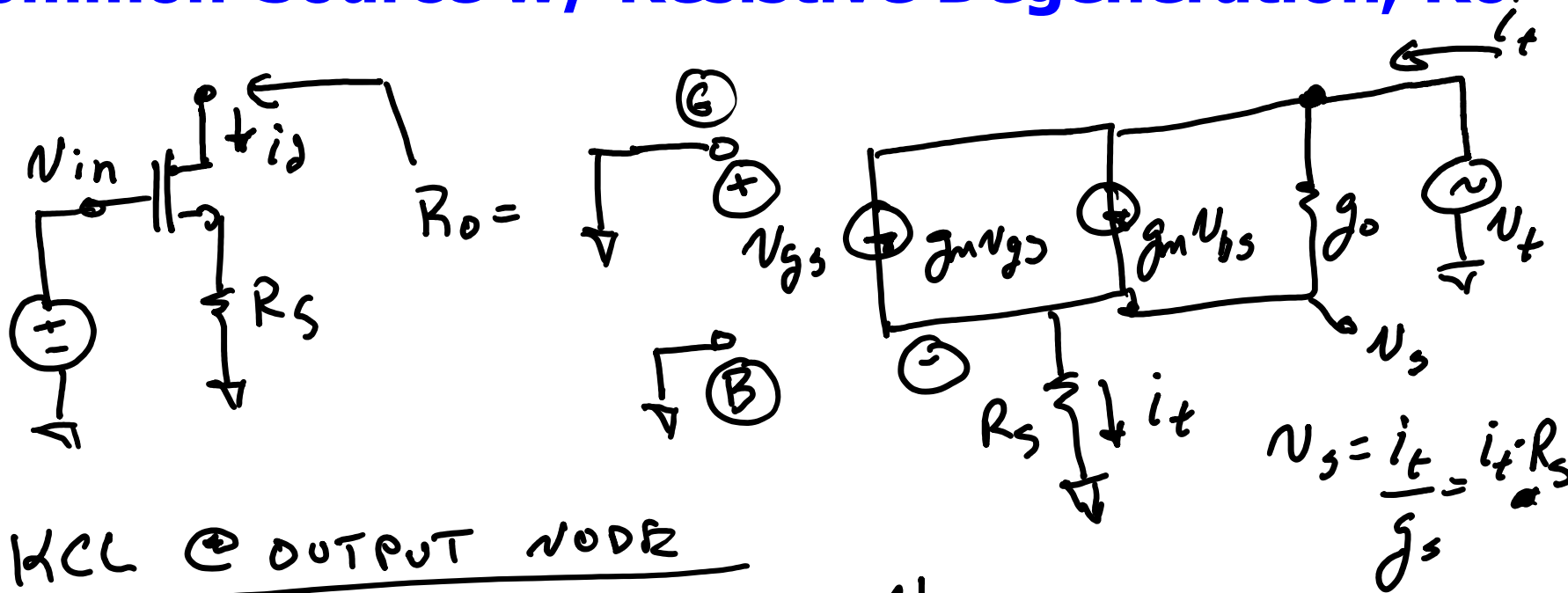


Lecture #5, Jan 14th, 2022

- Review Chapter 1 and 2 of Razavi book as needed. Course will start with Chapter 3.
- CAD 1 out, CAD 2 coming very soon – hopefully today.
- Homework 1 out, due 1 week from today.
- NDAs coming out with New CAD.
- Monday is MLK day.
- Class will be on campus next week w/ virtual option.
- Quiz 1 on Monday 1/24
- Discuss Single-Transistor Amplifier Configurations
 - Common-Source Amplifier
 - Common-Source w/ Active Load
 - Common-Source w/ Degeneration
 - Common-Gate Amplifier
 - Example problem.

Common-Source w/ Resistive Degeneration, R_o



KCL @ OUTPUT NODE

$$i_t = g_m \left(\overbrace{0 - \frac{i_t}{g_s}}^{V_{gs}} \right) + g_{mb} \left(\overbrace{0 - \frac{i_t}{g_s}}^{V_{bs}} \right) + g_o \left(V_t - \frac{i_t}{g_s} \right)$$

$$V_g = 0$$

$$V_b = 0$$

$$R_o = \frac{V_t}{i_t} \Rightarrow i_t \cdot \left[1 + \frac{(g_m + g_{mb} + g_o)}{g_s} \right] = g_o \cdot V_t$$

~~R_o~~

$$i_t \cdot \left[1 + \frac{(g_m + g_{mbs} + g_o)}{g_s} \right] = g_o \cdot V_t$$

$$R_o = \frac{V_t}{i_t}$$

$$\frac{V_t}{i_t} = \frac{\left[1 + \frac{(g_m + g_{mbs} + g_o)}{g_s} \right]}{g_o} \quad g_o = \frac{1}{r_o}$$

$$= r_o \left[1 + (g_m + g_{mbs} + g_o) R_s \right]$$

$$R_o \approx r_o \left[1 + g_m \cdot R_s \right]$$




BORN INTO MEMORY!

$$R_o \approx g_m \cdot R_s \cdot r_o$$


TYPICALLY/
 $g_{mbs} \ll g_m$

$g_o \ll g_m$
 ASSUME
 $1 \ll g_m \cdot R_s$

Cascode Gain

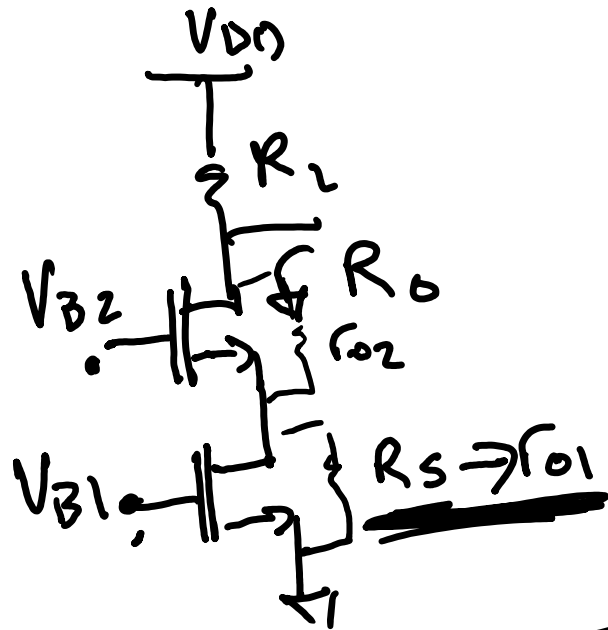
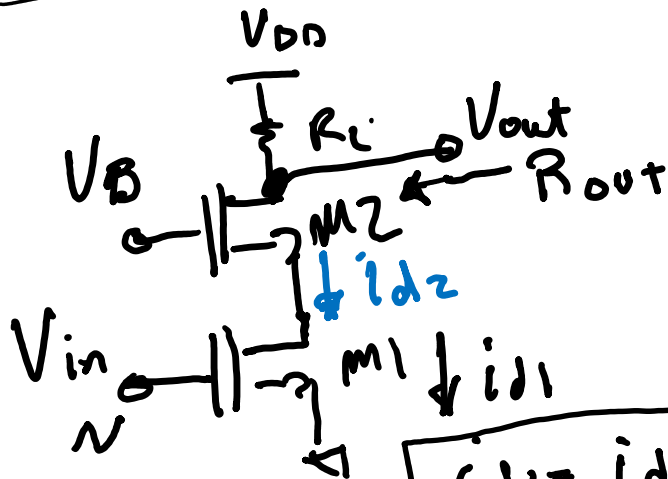
$$\underline{R_O} \approx \underbrace{g_{m2} \cdot r_{o1}}_{\text{cascode}} \cdot \underbrace{r_{o2}}_{\text{load}} \quad \leftarrow \underline{1\text{K}\Omega - 5\text{K}\Omega}$$



• BY INSPECTION $G_m = g_{m1}$

$$R_{out} = R_L // R_O$$

$$= R_L // g_{m2} \cdot r_{o1} \cdot r_{o2}$$

$$A_v = -G_m \cdot R_{out}$$

$$= \frac{-g_{m1} \cdot r_{o1} \cdot g_{m2} \cdot r_{o2} \cdot R_L}{g_{m2} \cdot r_{o2} \cdot r_{o1} + R_L}$$

$$\boxed{i_{d1} = i_{d2} = g_{m1} \cdot V_{in}}$$

Ideal Cascode Gain, $R_L \rightarrow \infty$

$$A_v = \frac{-g_{m1} r_{o1} \cdot g_{m2} \cdot r_{o2} \cdot R_L}{g_{m2} \cdot r_{o2} \cdot r_{o1} + R_L}$$
$$= \frac{-g_{m1} r_{o1} g_{m2} \cdot r_{o2}}{1 + (g_{m2} r_{o2} r_{o1}) / R_L}$$


INTRINSIC GAIN OF CASCODE.

$$\Rightarrow R_L \rightarrow \infty$$

$$A_v \approx -\underbrace{g_{m1} r_{o1}}_{\substack{\uparrow \\ \text{INTRINSIC GAIN OF CS Amp.}}} \underbrace{g_{m2} r_{o2}}_{\substack{\uparrow \\ \text{INTRINSIC GAIN OF CS Amp.}}}$$

← BURN IN MEMORY.

CASCADED CS Amps

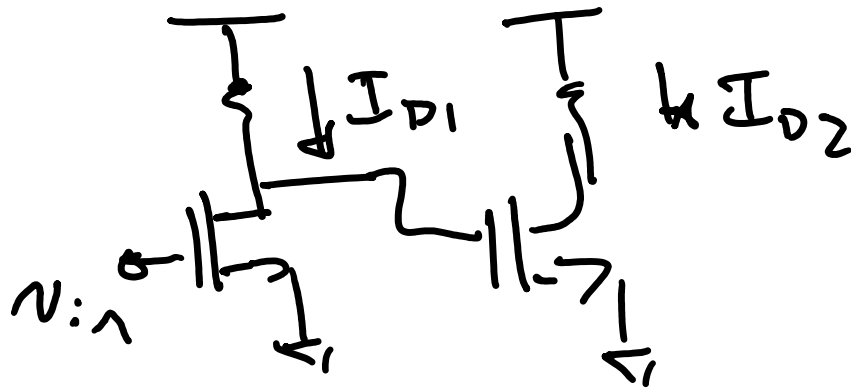

$$A_v = g_{m1} r_{o1} \cdot g_{m2} r_{o2}$$




CASCODE

- HAS CURRENT REUSE.
- VERY HIGH GAIN.
- LIMITED OUTPUT VOLTAGE SWING.

\Rightarrow LOW-END OF $\frac{g_{m1} r_{o1} \cdot g_{m2} r_{o2}}{1 + g_{m2} r_{o2}}$

" V_{out} " LIMITED TO $\frac{2V_{DD}}{3} - \frac{g_{m2} r_{o2} \cdot V_{out}}{1 + g_{m2} r_{o2}}$

FOR $M1 \neq M2$

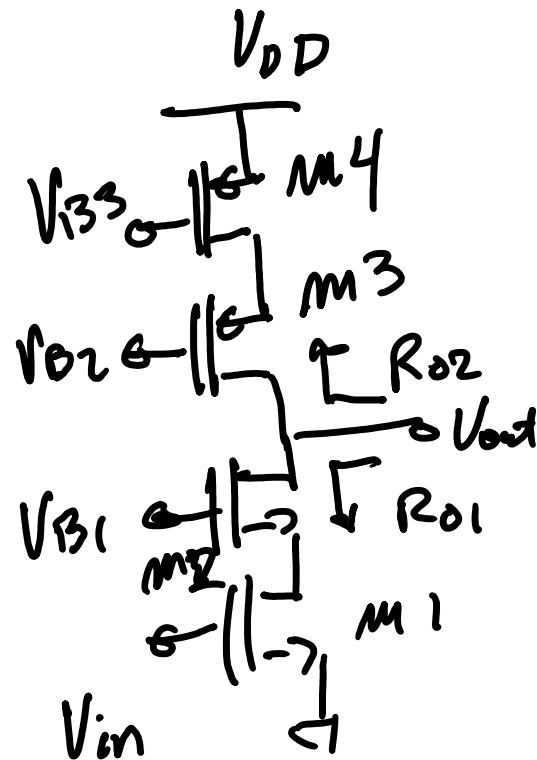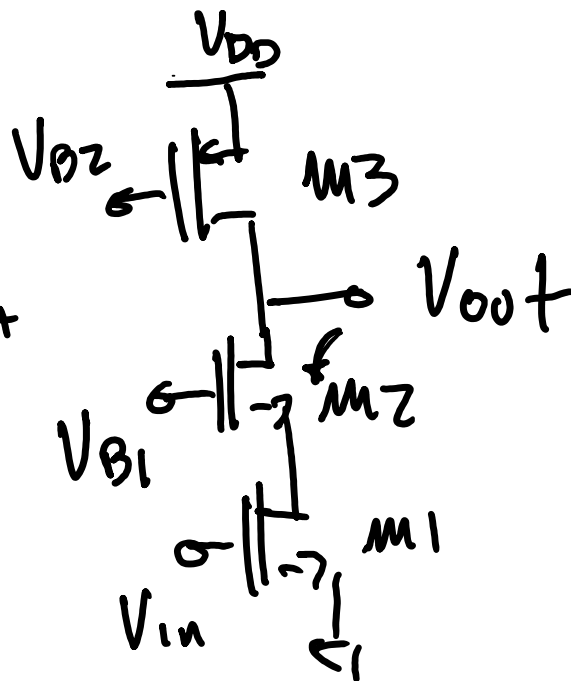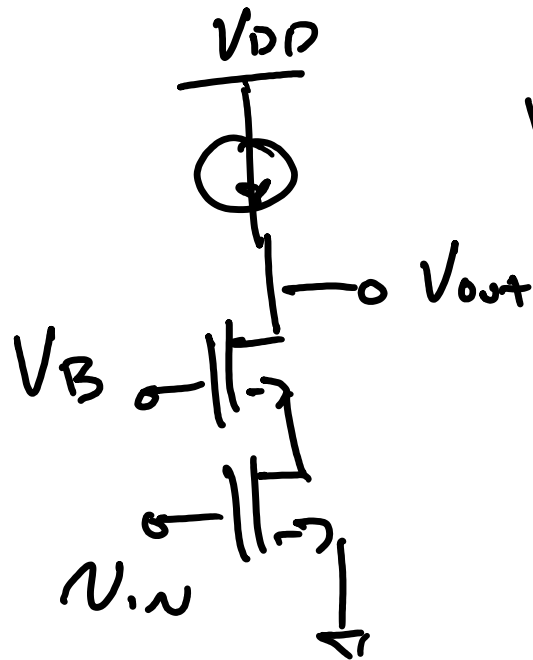

$$A_v \approx -g_{m1} \cdot r_{o3}$$

$$R_{o2} \approx g_{m3} \cdot r_{o2} \cdot r_{o3}$$

$$R_{o1} \approx g_{m2} \cdot r_{o1} \cdot r_{o2}$$

$$A_v \approx -g_{m1} \cdot (R_{o2} \parallel R_{o1})$$

$$A_v \approx -g_{m1} \cdot \left(\frac{g_m \cdot r_o \cdot r_o}{2} \right)$$

$$\left\{ \begin{array}{l} \text{ASSUME} \\ R_{o1} = R_{o2} \end{array} \right.$$

Example Problem 3.4

- 3.4. Suppose the common-source stage of Fig. 3.4(a) is to provide an output swing from 1 V to 2.5 V. Assume that $(W/L)_1 = 50/0.5$, $R_D = 2 \text{ k}\Omega$, and $\lambda = 0$.
- Calculate the input voltages that yield $V_{out} = 1 \text{ V}$ and $V_{out} = 2.5 \text{ V}$.
 - Calculate the drain current and the transconductance of M_1 for both cases.
 - How much does the small-signal gain, $g_m R_D$, vary as the output goes from 1 V to 2.5 V? (Variation of small-signal gain can be viewed as nonlinearity.)


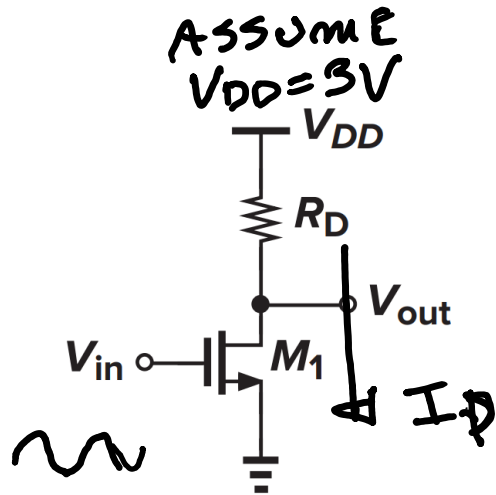


Fig 3.4 a

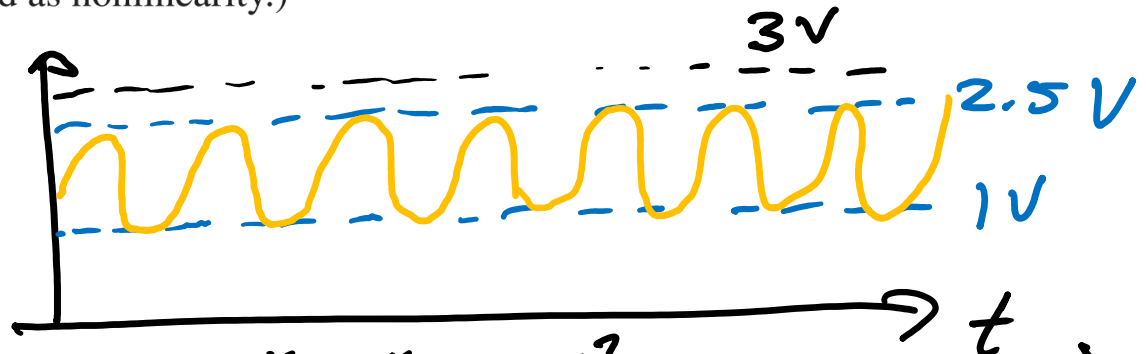

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$\lambda = 0$

1st FND $V_{in} = V_{GS} \big|_{V_{out} = 2.5\text{V}}$

$$I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{3\text{V} - 2.5\text{V}}{2\text{k}\Omega}$$

$$I_D \big|_{V_{out} = 1\text{V}} = \frac{3\text{V} - 1\text{V}}{2\text{k}\Omega} = 1\text{mA} = 0.25\text{mA}$$

$$V_{IN} = V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{th}$$

$$V_{out} = 2.5V$$

$$= \sqrt{\frac{2 \cdot 0.25 \text{ mA}}{1.34 \times 10^{-4} \left(\frac{50}{6.5}\right)}} + 0.7V = \underline{\underline{0.89V}}$$

$$V_{out} = 1V.$$

$$= \sqrt{\frac{2 \cdot 1 \text{ mA}}{1.34 \times 10^{-4} \left(\frac{50}{0.4}\right)}} + 0.7V = \underline{\underline{1.086V}}$$