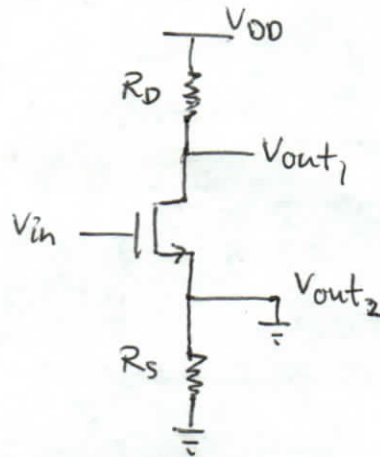


3.32 Prove $\frac{V_{out1}}{V_{out2}} = -\frac{R_D}{R_S} \rightarrow$ use superposition!

Find V_{out1} :

[V_{out2} is grounded]




V_{out1} sees common-source with resistive load

$$V_{out1} = -G_m R_D$$

$$V_{out2} = 0$$

Find V_{out2} :

[V_{out1} is grounded]

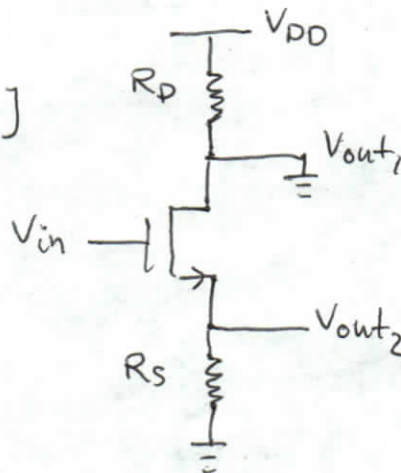

V_{out1} sees common-source with source degeneration

V_{out2} sees common-drain (source-follower)

$$V_{out1} = G_M = \frac{g_m}{1 + g_m R_S} \approx \frac{1}{R_S}$$

$$V_{out2} = 1$$

Combine equations:

$$V_{out1} = -\frac{R_D}{R_S}, \quad V_{out2} = 1$$

$$\text{Thus } \frac{V_{out1}}{V_{out2}} = \frac{-R_D/R_S}{1} = -\frac{R_D}{R_S}$$