

Name: SOLUTIONS

50 points total

EE 473


Quiz 2

Winter 2022

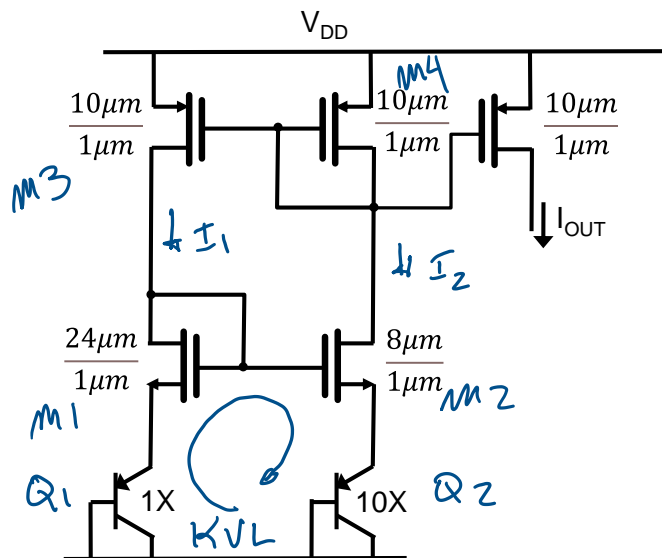1) a) For the below circuit, assume all MOS devices are in the saturation region.

Derive a closed-form expression for the value of the output current, I_{OUT} , then compute the value. The following parameters may, or may not be needed,

$\mu_n C_{ox} = 20 \text{ mA/V}^2$, $\mu_p C_{ox} = 10 \text{ mA/V}^2$, $V_{TH(NMOS)} = 0.7 \text{ V}$ and $V_{TH(PMOS)} = 0.8 \text{ V}$, $\lambda_n = 0$, and $\lambda_p = 0$. Ignore the body effect ($\gamma = 0$). (25 points)



$$\lambda = 0 \Rightarrow r_o \rightarrow \infty$$

$\Rightarrow I_1 = I_2 = I_{OUT}$ IF ALL DEVICES IN SATURATION.

KVL AROUND ABOVE LOOP:

$$V_{BE1} + V_{GS1} - V_{GS2} - V_{BE2} = 0$$

$$V_T \ln \left(\frac{I_1}{I_{S1}} \right) + (V_{DSAT} + V_{th})_{M1} - (V_{DSAT} + V_{th})_{M2} - V_T \ln \left(\frac{I_2}{n I_{S1}} \right) = 0$$

ASSUME $V_{th1} = V_{th2}$

$$V_T \ln \left(\frac{I_1}{I_2} \cdot \frac{n \cdot I_{S1}}{I_{S1}} \right) + (V_{DSATM1} - V_{DSATM2}) = 0$$

$$V_T \ln(n) = (V_{DSATM2} - V_{DSATM1})$$

$$V_T \ln(n) = \sqrt{\frac{2 \cdot I_{OUT}}{\mu_n C_{ox}}} \left(\sqrt{\left(\frac{L}{W} \right)_{M2}} - \sqrt{\left(\frac{L}{W} \right)_{M1}} \right)$$

SOLVE FOR I_{OUT}

$$\sqrt{\frac{2 \cdot I_{out}}{\mu_n C_{ox}}} = \frac{V_T \ln(n)}{\left(\sqrt{\frac{L}{W}}\right)_{m2} - \left(\sqrt{\frac{L}{W}}\right)_{m1}}$$

$$I_{out} = \frac{\mu_n C_{ox}}{2} \left(\frac{V_T \ln(n)}{\sqrt{\frac{L}{W}}_{m2} - \sqrt{\frac{L}{W}}_{m1}} \right)^2$$

$$= \frac{20 \mu A / 2}{2} \left(\frac{25 mV \ln(10)}{\sqrt{\frac{1}{8}} - \sqrt{\frac{1}{24}}} \right)^2$$

$$\boxed{I_{out} = 1.484 \mu A}$$


$$\approx 1.5 \mu A$$

b) For the circuit in part a), what is the minimum supply voltage (V_{DD}) that can be used for the current source to operate properly (10 points)

LOWEST VOLTAGE?

THE LOWEST VOLTAGE COULD BE DETERMINED BY THE LEFT LEG w/ I_1 , OR THE RIGHT LEG (I_2). SOLUTIONS WILL DO BOTH LEGS, BUT EITHER ANSW WILL BE ACCEPTED.

ASSUME $V_{BEQ_1} \approx 0.7V$

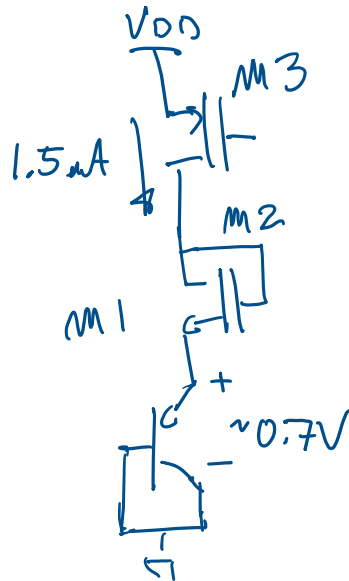

$$V_{DD, \min} = V_{BE1} + V_{GS M1} + V_{DSAT M3}$$

$$= V_{BE1} + V_{DSAT M1} + V_{thn} + V_{DSAT M3}$$

$$V_{BE} \approx 0.7V$$

$$V_{DSAT M1} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \approx \sqrt{\frac{2 \cdot 1.5mA}{20 \frac{\mu A}{V^2} \left(\frac{24}{1}\right)}} \approx 79mV$$

$$V_{DSAT M4} = \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}} \approx \sqrt{\frac{2 \cdot 1.5mA}{10 \frac{\mu A}{V^2} \left(\frac{10}{1}\right)}} \approx 173mV$$

$$V_{thn} = 0.7V \quad V_{thp} = 0.8V$$

$$\therefore V_{DD, \min, \text{LEFT}} = 0.7V + 0.08V + 0.7 + 0.175 + 0.8V = 2.455V$$

MIN V_{DD} DUE TO THE RIGHT LEG.

$$V_{DD, \min, \text{RIGHT}} = V_{BE2} + V_{DSAT M2} + V_{GS M4}$$

$$= V_{BE2} + V_{DSAT M2} + V_{DSAT M4} + V_{thp}$$

$$= 0.7V + 0.14 + 0.175 + 0.8$$

$$= 1.815$$

$$V_{BE2} \approx 0.7V$$

$$V_{DSAT M2} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}}$$

$$= \sqrt{\frac{2 \cdot 1.5mA}{20 \frac{\mu A}{V^2} \left(\frac{8}{1}\right)}}$$

$$\approx 140mV$$

$V_{DSAT M4}$: FROM ABOVE

$$V_{thn} = 0.7V$$

$$V_{thp} = 0.8V$$

LEFT LEG LIMITS LOW VOLTAGE!

c) Describe the relationship between the output current and temperature. This can be described as a proportionality if you want – e.g. $I_{OUT} \propto (T)$. (15 points)

$$I_{OUT} = \frac{\mu_n C_{ox}}{2} \left(\frac{V_T \ln(n)}{\sqrt{\left(\frac{L}{W}\right)_{m_2}} - \sqrt{\left(\frac{L}{W}\right)_{m_1}}} \right)^2$$

$$V_T = \frac{kT}{q} \quad \& \quad \mu_n \propto T^{-3/2}$$

ALL OTHER VARIABLES INDEPENDENT OF TEMP. \therefore

$$I_{OUT} \propto T^{-3/2} (T)^2$$

$$I_{OUT} \propto \sqrt{T}$$