

P8.7 – skip the part of the problem that deals with calculating the input referred noise.


P8.10

P10.1

P10.2

P10.3

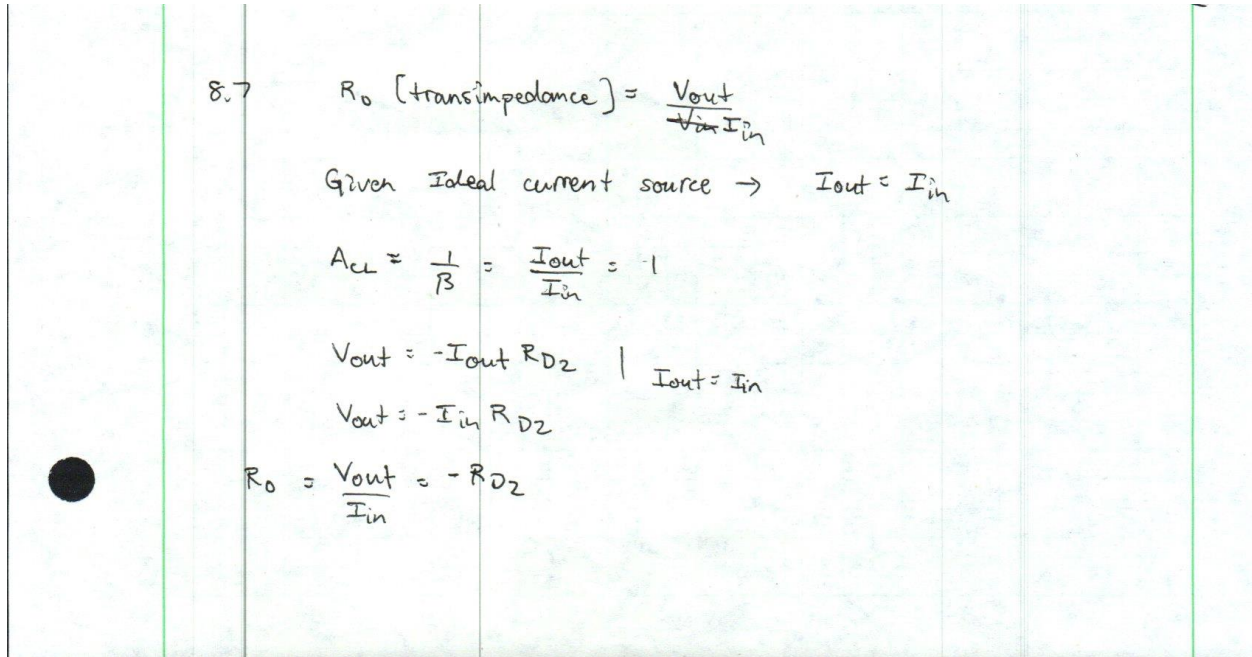P10.11 – please do parts a, b, c and d, but skip e.



8.7 R_o [transimpedance] = $\frac{V_{out}}{I_{in}}$

Given Ideal current source $\rightarrow I_{out} = I_{in}$


$A_{cl} \approx \frac{1}{\beta} = \frac{I_{out}}{I_{in}} = -1$

$V_{out} = -I_{out} R_{D2} \quad | \quad I_{out} = I_{in}$

$V_{out} = -I_{in} R_{D2}$


$R_o = \frac{V_{out}}{I_{in}} = -R_{D2}$

8.10

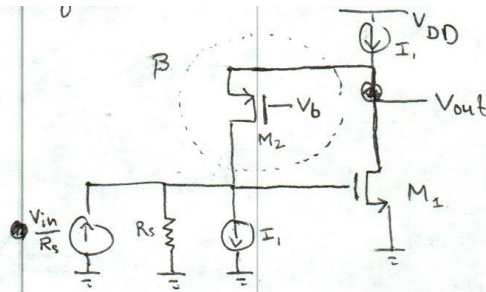

Break the loop and apply test voltage

Find the loop gain:

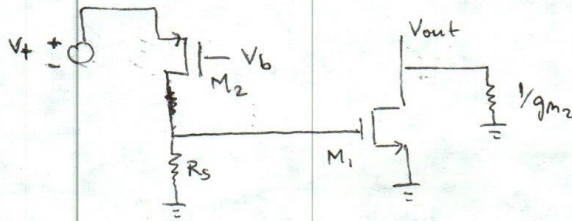

$$V_{out} = -g_{m2} \cdot (R_s \parallel r_{o2}) \cdot (-g_{m1} \cdot (\frac{1}{g_{m2}} \parallel r_{o1}))$$

$$V_{out} = (-g_{m2} R_s) (-g_{m1} \frac{1}{g_{m2}}) = -g_{m1} R_s \rightarrow A \cdot \beta = g_{m1} \cdot R_s$$

Find Open-Loop Forward Gain

$$V_{out} = -\left(\frac{V_{in}}{R_s}\right) \cdot (R_s \parallel r_{o2}) \cdot g_{m1} \cdot (\frac{1}{g_{m2}})$$

$$A_{closed} = \frac{-R_s \cdot g_{m1} / g_{m2}}{1 + g_{m1} R_s} = \frac{V_o}{V_{in} / R_s} \rightarrow \frac{V_{out}}{V_{in} / R_s} \Big|_{open} = -R_s \cdot \frac{g_{m1}}{g_{m2}}$$

$$A_{v, closed} = A_{v, closed} \cdot \frac{1}{R_s} = \frac{-1}{R_s} \cdot \frac{R_s g_{m1} / g_{m2}}{1 + g_{m1} R_s} = \frac{-g_{m1}}{g_{m2} (1 + g_{m1} R_s)}$$

Transresistance

Shunt-Shunt Feedback

$$R_{in, closed} = \frac{R_{in, open}}{1 + A\beta} \quad R_{in, open} \approx R_s$$



$$R_{in, closed} = \frac{R_s}{1 + \underbrace{g_{m1} R_s}_{\text{loop-gain}}}$$

$$R_{out, closed} = \frac{R_{out, open}}{(1 + A\beta)}$$

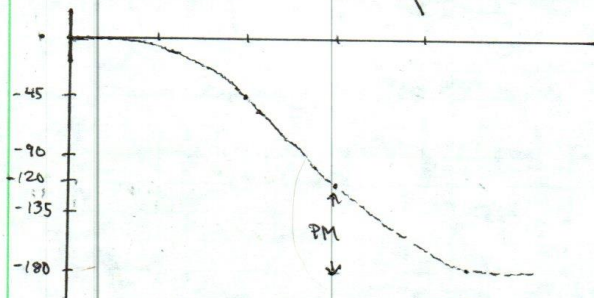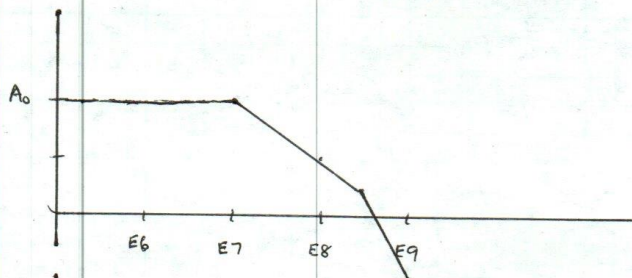10.1 $f_1 = 10 \text{ MHz}$, $f_2 = 500 \text{ MHz}$, $PM = 60^\circ$

Need $\angle \beta H = -120^\circ$

$$\frac{Y(s)}{X} = H(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) + \beta A_0}$$



gain crossover is after ω_{p1}

$$\angle \beta H = \underbrace{-\tan^{-1}\left(\frac{\omega}{\omega_1}\right)}_{-90^\circ} - \tan^{-1}\left(\frac{\omega}{\omega_2}\right) = -120^\circ$$

$$-\tan^{-1}\left(\frac{\omega}{\omega_2}\right) = -30^\circ$$

$$\tan^{-1}\left(\frac{\omega}{\omega_2}\right) = 30^\circ$$

$$\tan\left[\right] = \tan\left(30^\circ \cdot \frac{\pi}{180^\circ}\right)$$

$$\frac{\omega}{\omega_2} = \tan\left(\frac{\pi}{6}\right)$$

$$\frac{f}{f_2} = \tan\left(\frac{\pi}{6}\right) \rightarrow$$

$$f = f_2 \tan\left(\frac{\pi}{6}\right) = \overset{2.65}{2.89} \text{ E8 Hz}$$

$$f = 2.89 \text{ E8 Hz [gain crossover]}$$

Find A_0 :

$$A_0 - 20 \log_{10} \left(\frac{\omega}{\omega_c} \right) - 20 \log_{10} \left(\frac{\omega}{\omega_c} \right) = 0$$

$$A_0 - 20 \log_{10} \left(\frac{f}{f_1} \right) - 20 \log_{10} \left(\frac{f}{f_2} \right) = 0$$

$$A_0 - 20 \left[\log_{10} \left(\frac{f}{f_1} \right) + \log_{10} \left(\frac{f}{f_2} \right) \right] = 0 \quad \times$$

$$A_0 = 20 \left[\log_{10} \left(\frac{f}{f_1} \right) + \log_{10} \left(\frac{f}{f_2} \right) \right] \quad | \quad f = \overset{2.65}{\cancel{2.89 \text{ E8}}} \text{ Hz} \quad 2.89 \text{ E8 Hz}$$

$$A_0 = 20 \log_{10} \left(\frac{f}{f_1} \right) \quad \underbrace{\hspace{1cm}}_0$$

$$A_0 = 29.2 \text{ dB}$$

10.2

$$\beta = 1 \quad H(s) = \frac{A_0}{(1 + \frac{s}{\omega_p})(1 + \frac{s}{\omega_p}) + \beta A_0}$$

$$A_0 - 40 \log_{10} \left(\frac{\omega}{\omega_p} \right) = 0 \quad \omega_p = 1 \text{ MHz}$$

Need $\angle \beta H = -120^\circ$ for 60° phase margin

$$-2 \tan^{-1} \left(\frac{\omega}{\omega_p} \right) - \tan^{-1} \left(\frac{\omega}{\omega_p} \right) = -120^\circ$$

$$-2 \tan^{-1} \left(\frac{\omega}{\omega_p} \right) = -120^\circ$$

$$\tan^{-1} \left(\frac{\omega}{\omega_p} \right) = 60^\circ$$

$$\frac{f}{f_p} = \tan \left(\frac{\pi}{3} \right)$$

$$f = 1.73 \text{ MHz}$$

$$A_0 - 40 \log_{10} \left(\frac{1.73 \text{ MHz}}{1 \text{ MHz}} \right) = 0$$

$$\underline{A_0 = 9.52 \text{ dB}}$$

$$\frac{1}{\beta} = 4 \rightarrow A_0' = A_0 \cdot \left| \frac{1}{\beta} \right|$$

$$A_0' = A_0 [\text{dB}] + 20 \log_{10} \left(\frac{1}{\beta} \right)$$

$$A_0' = 9.52 \text{ dB} + 20 \log_{10} (4)$$

$$A_0' = 21.56 \text{ dB}$$

10.3

$$\omega_p = 1 \text{ MHz}$$

$$\omega_{p2} = 2\omega_{p1}$$

$$100 = 60 \text{ dB}$$

$$A_0 - 20 \log\left(\frac{\omega}{\omega_c}\right) - 20 \log\left(\frac{\omega}{\omega_{c2}}\right) = 0 \quad [\log = \log_{10}]$$

$$A_0 - 20 \log\left(\frac{f}{f_1}\right) - 20 \log\left(\frac{f}{2f_1}\right) = 0 \quad [\log = \log_{10}]$$

$$60 - 20 \left[\log\left(\frac{f}{f_1}\right) + \log\left(\frac{f}{2f_1}\right) \right] = 0 \quad [\log = \log_{10}]$$

$$60 - 20 \log_{10}\left(\frac{f^2}{2f_1^2}\right) = 0$$

$$60 - 40 \log_{10}\left(\frac{f}{\sqrt{2}f_1}\right) = 0$$

$$\log_{10}\left(\frac{f}{\sqrt{2}f_1}\right) = \frac{3}{2}$$

$$\frac{\log(f) - \log(f_1) - \log(2)}{\log(10)} = \frac{3}{2} \quad [\log = \ln]$$

$$\log(f) = \frac{3}{2} \log(10) + \log(f_1) + \frac{\log(2)}{2} \quad [\log = \ln]$$

$$\log(f) = 17.62$$

$$f = e^{17.62} = 44.7 \text{ MHz}$$

$$\phi = -\tan^{-1}\left(\frac{44.7 \text{ MHz}}{1 \text{ MHz}}\right) - \tan^{-1}\left(\frac{44.7 \text{ MHz}}{2 \text{ MHz}}\right)$$

$$= -3.07 \cdot \frac{180}{\pi}$$

$$= -176.16^\circ$$

$$\text{PM} = 180 - 176.16^\circ$$

$$= \underline{3.84^\circ}$$

$$\omega_{p2} = 4\omega_{p1}$$

$$\frac{\log(f) - \log(f_1) - \log(2)}{\log(10)} = \frac{3}{2}$$

$$\log(f) = \frac{3}{2} \log(10) + \log(f_1) + \log(2)$$

$$\log(f) = 17.96$$

$$f = 63.2 \text{ MHz}$$

$$\angle = -\tan^{-1}\left(\frac{63.2 \text{ MHz}}{1 \text{ MHz}}\right) - \tan^{-1}\left(\frac{63.2 \text{ MHz}}{4 \text{ MHz}}\right)$$

$$\angle = -3.06 \cdot \frac{180}{\pi} = -175.47^\circ$$

$$\text{PM} = 180 - 175.47 = \underline{4.53^\circ}$$