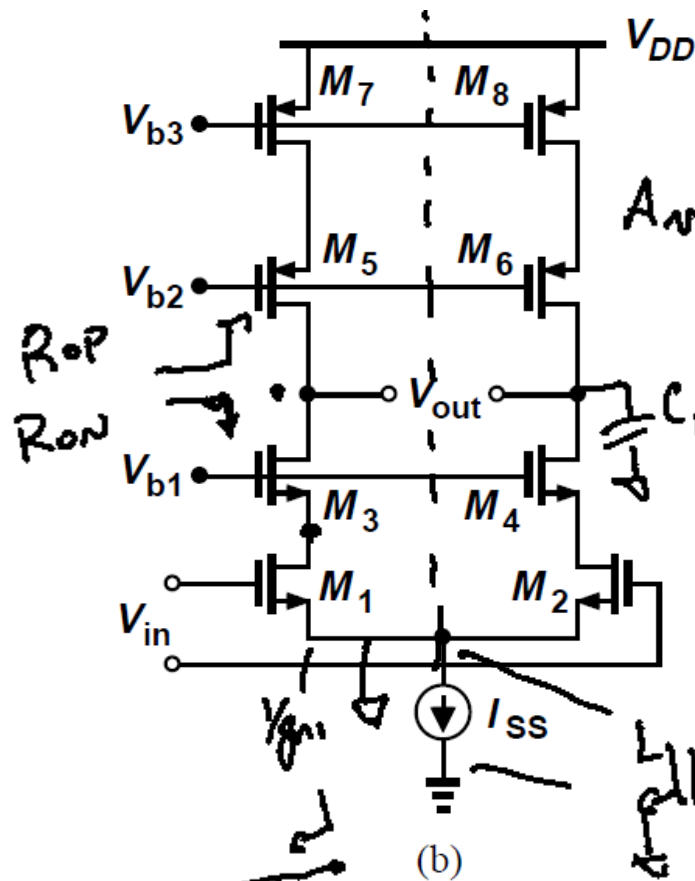


Lecture #16, Feb 14th, 2022

- We will bounce between chapters 8 (Feedback) and 9 (Op Amp design).
- CAD 4 now out, due Thursday.
- Quiz #2 postponed until Wednesday.
 - Results:
 - High = 3 x 50 Nice work!
 - Mean = 39
 - Standard Deviation = 11
- Project 1 due tomorrow!
- Project 2 coming very soon.
- Today:
 - Opamp Topologies
 - Common-Source
 - Telescopic
 - Folded-Cascode
 - Two-Stage Op Amp
 - Regulated Cascodes (Active Cascode)

Telescopic Cascode Op Amps



• VOLTAGE GAIN

$$A_v = -g_{m1} \cdot (\underbrace{g_{m3} \cdot r_{o3} \cdot r_{o1}}_{\text{INTERNAL (10-100)}} \parallel g_{m5} \cdot r_{o5} \cdot r_{o7})$$

C_L = OUTPUT SWING

$$V_{out, MAX} = V_{DD} - 5 V_{DSAT} \quad ; \quad \text{POOR OUTPUT SWING}$$

($\widehat{V_{b3} - V_{th}}$)

• BW


$$P = \frac{1}{2\pi (R_{on} \parallel R_{op}) \cdot C_L}$$

DOMINATE POLE
STABLE


Telescopic Cascode Op Amps

- Low-frequency gain: $g_{mN}[(g_{mN}r_{ON}^2) \parallel (g_{mP}r_{OP}^2)]$
- Speed: Additional poles
- Output Swing (single-side): $V_{DD} - 5 \times \text{Overdrive}$
- Mirror pole in single-ended
- Difficult to short telescopic op amp output to input
- Power and noise: good, input noise mainly has four devices contribution

DIFF IN SINGLE-ENDED OUT

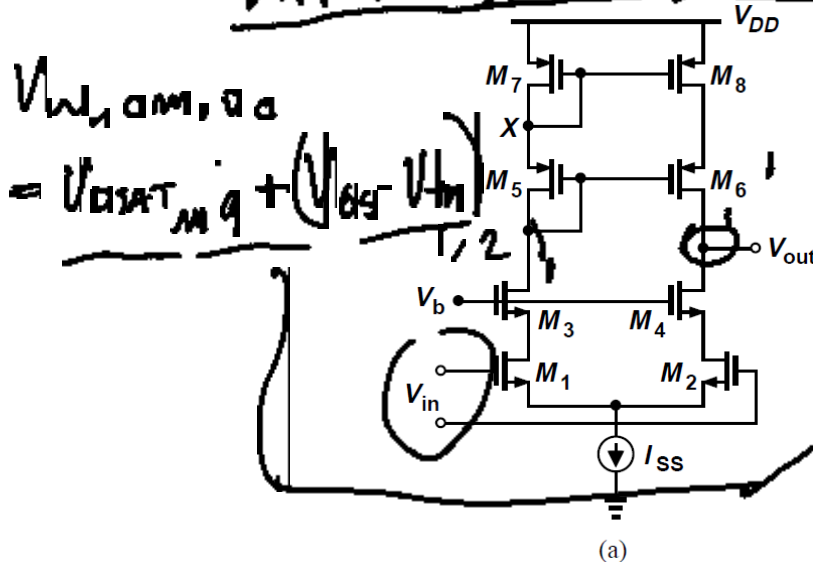


FULLY-DIFF

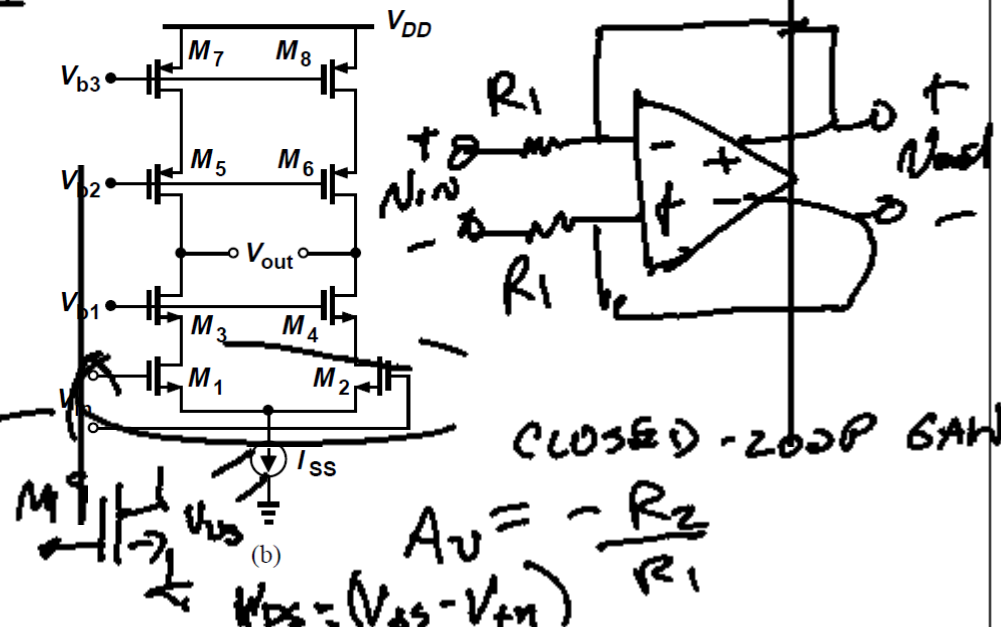

Gate Bias Voltage Generation

 - Ensure bias voltage to track the input CM level
- Choose Mb1 to be a narrow, long, “weak” device



KVL

$$V_{GS,b1} - V_{GS3} - V_{DS,M1} = 0 \quad \text{WANT}$$

$$V_{GS,b1} = V_{GS3} + V_{DS,M1} \quad \checkmark \quad V_{DS,M1} = (V_{GS} - V_{th})_{M1}$$


$$= (V_{GS} - V_{th})_1 + V_{GS3} \quad (V_{GS} - V_{th})_{M1}$$

$$V_{b1} = V_P + V_{GS,b1}$$



$$V_{GS,b1} = (V_{GS1,2} - V_{TH1,2}) + V_{GS3,4}$$

Removing the Diff Pair From the Stack

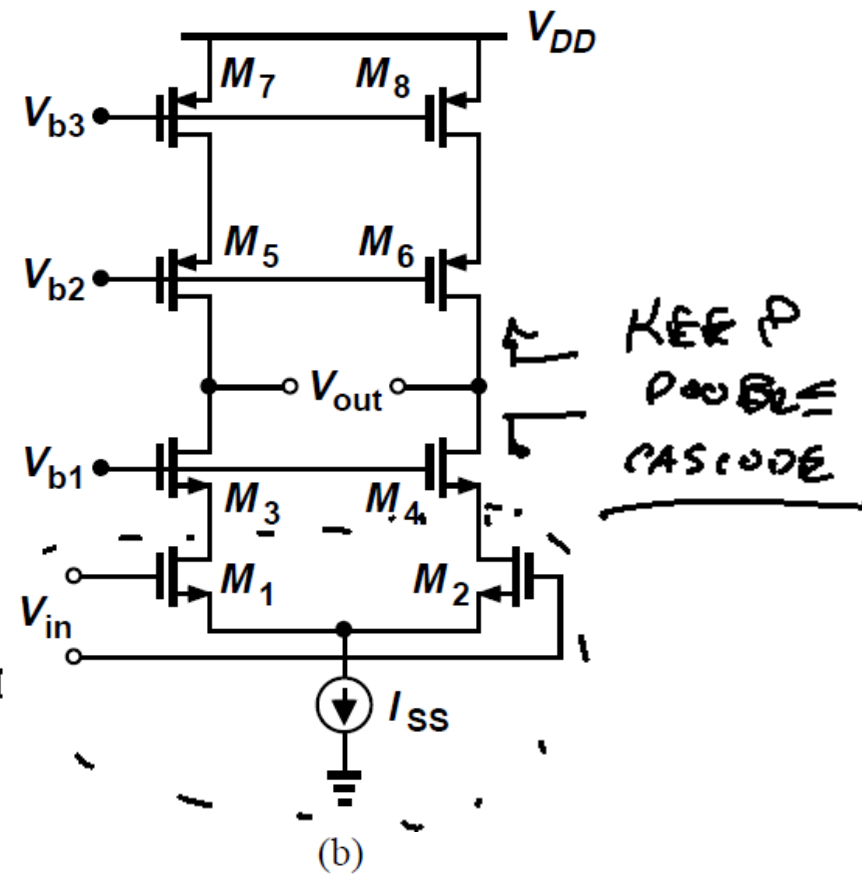
WHAT IF WE
POULLED THIS OUT
OF
THE
STACK.



Folded Cascode

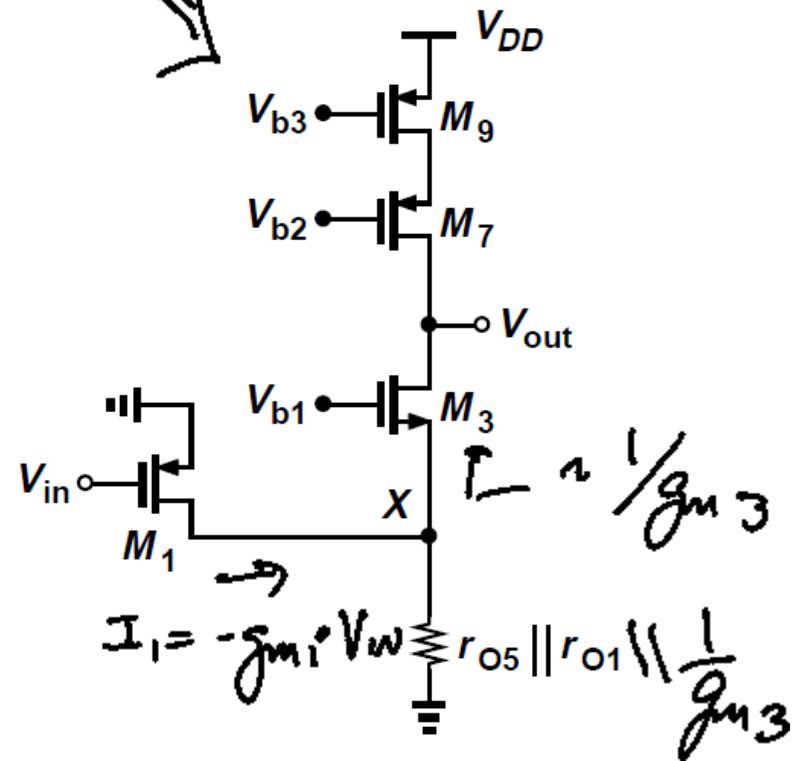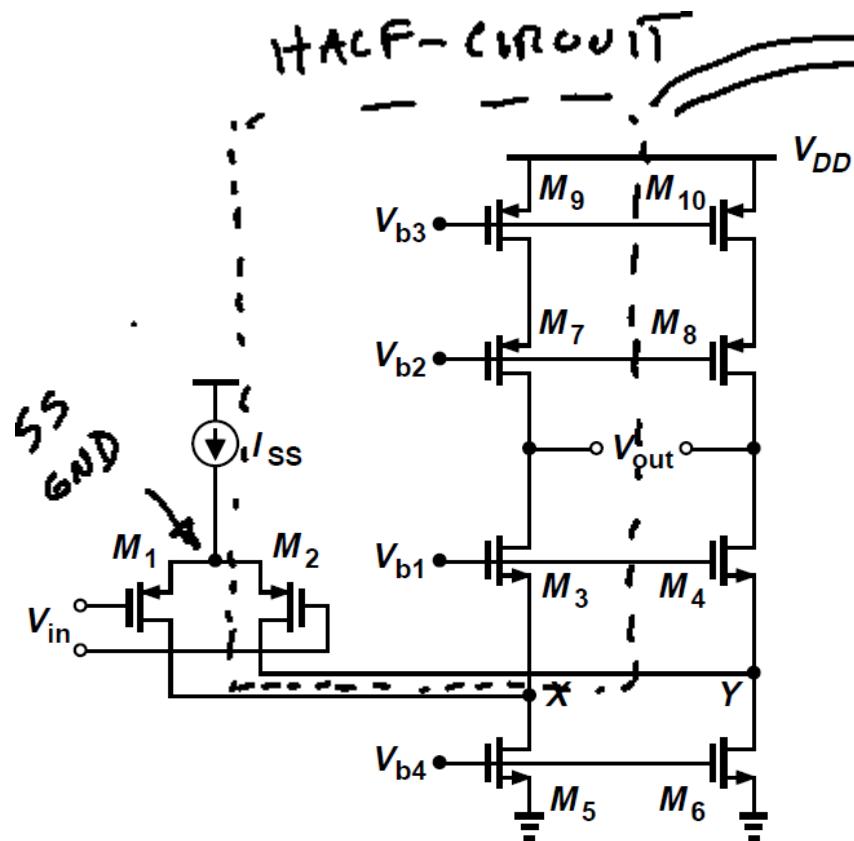



Folded Cascode Voltage Gain

 


Folded Cascode Op Amps

Recall Folded Cascode

 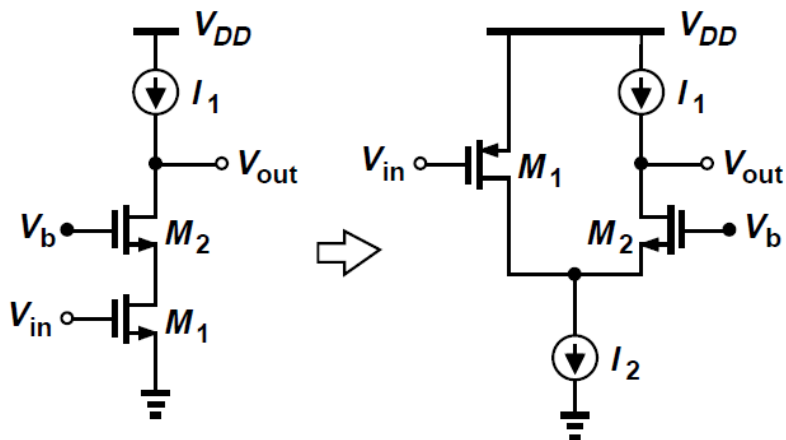
- Not “stack” the cascode transistor on the input device
- Consume higher power
- Output Voltage Swing: $V_{DD} - 4\text{overdrive}$
- Output and input could short together



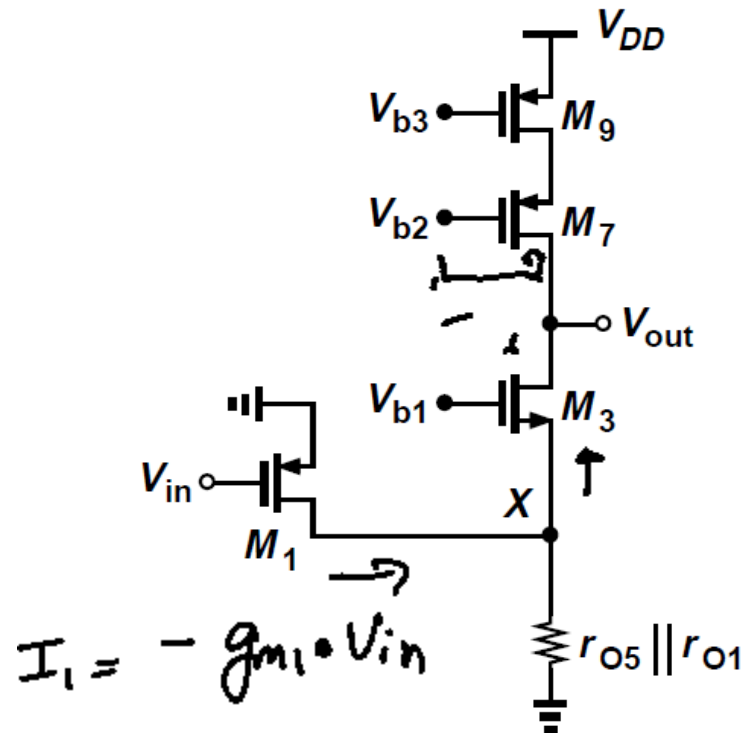SS Current from Diff Pair Shunted Up In Cascode



$$I_1 = -g_{m1} \cdot V_{in}$$

 

$$I_{out} = \frac{r_{o5} \parallel r_{o1}}{r_{o5} \parallel r_{o1} + 1/g_{m3}} \cdot I_1$$





Folded Cascode Voltage Gain

$$|A_v| = G_m R_{out}$$

• Since $(g_{m3} + g_{mb3})^{-1} \parallel r_{O3} \ll r_{O1} \parallel r_{O5}$, thus $G_m \approx g_m$



$$|A_v| \approx g_{m1} [(g_{m3} + g_{mb3}) r_{O3} (r_{O1} \parallel r_{O5})] [(g_{m7} + g_{mb7}) r_{O7} r_{O9}]$$

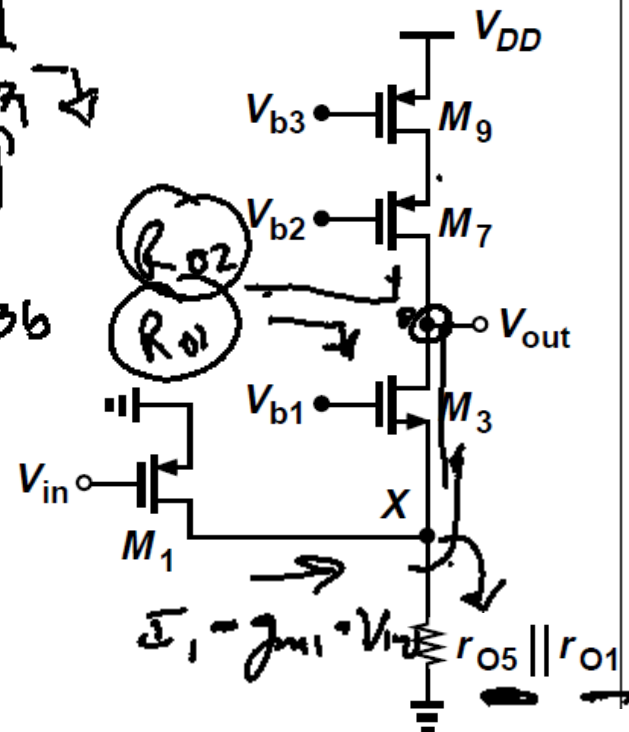   • Two or three times lower than a telescopic topology



Effect capacitance on the nondominant pole

 
 
- At “folding point”, a large capacitance due to a large current device M_5 would be added to the total capacitance.



NMOS vs. PMOS input



- Greater mobility from NMOS input leads to higher gain
- Lowering the pole at folding point
- PMOS input is less sensitive to flicker noise (wider WL)

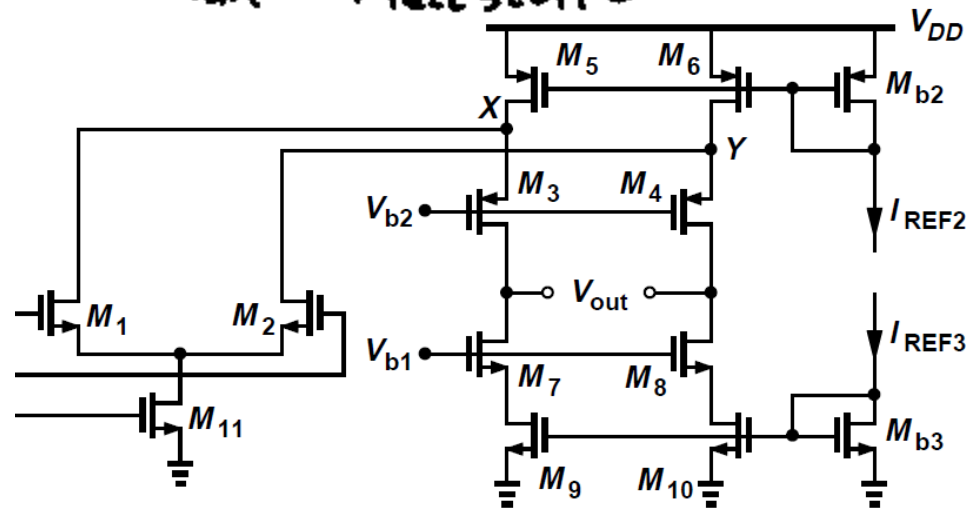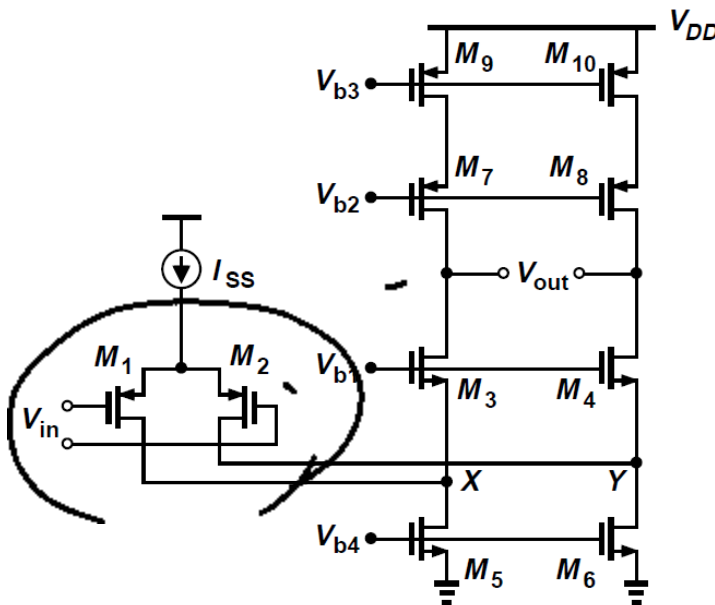$\bullet GAW \cdot 1A \approx g_{m1} (g_{m3} \cdot r_{o5} \cdot r_{o3} / g_{m7} \cdot r_{o9} \cdot r_{o7})$
 $\bullet \text{OUTPUT SWING: } V_{DD} - 4 V_{DSAT5}$
 $\bullet BW: P_{OAM} \approx P_{TELESCOPE}$



Folded Cascode Properties

- Slighter Higher Output Swing than telescopic
- Higher Power dissipation, lower voltage gain, lower pole frequency and higher noise
- Input and output can be shorted: 2overdrive from bound
- A better input CM range

 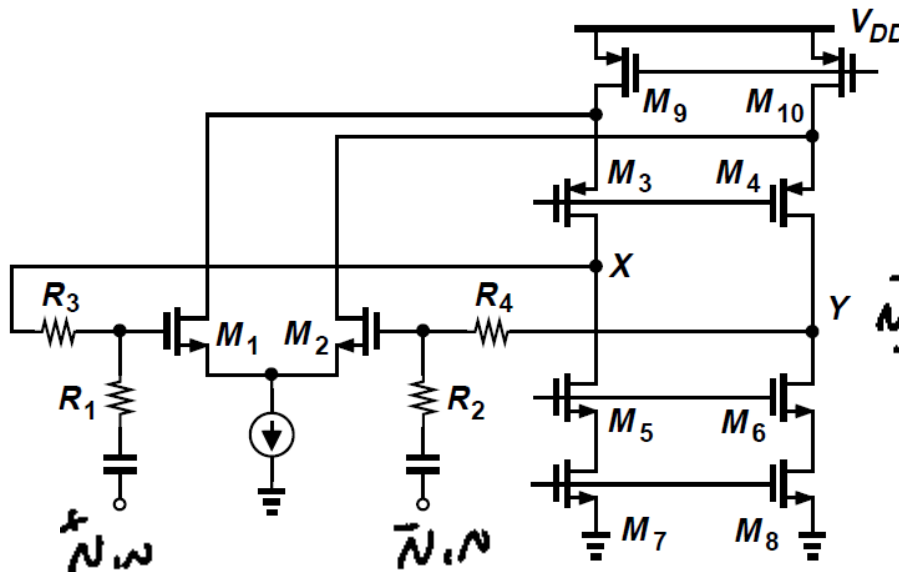

Example 9.9

Design a folded- cascode op amp with an NMOS pair.

Specifications: $V_{DD} = 3V$, differential output swing = $3V$,

Power dissipation = $10mW$, voltage gain = 2000 .

Solution:


(1)Current allocation

(2)Overdrive voltage allocation

(3)Aspect ratio calculation


(4)Small-signal gain with minimal length

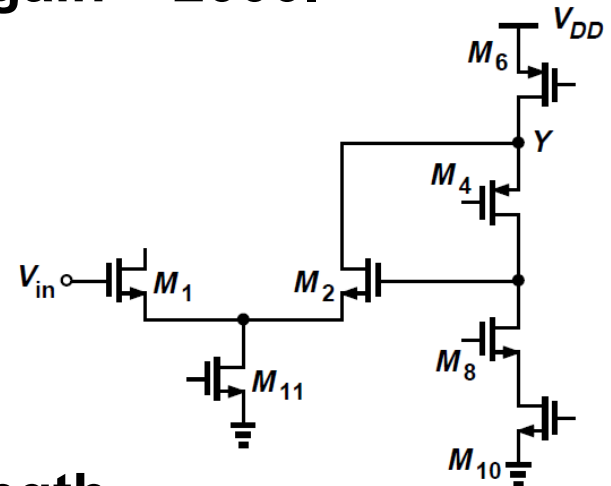(5)Iteration by increase $M_5/M_1/M_4$ in turns



Note that the folding point capacitance may limit here.

Two-Stage Op Amps - Gain

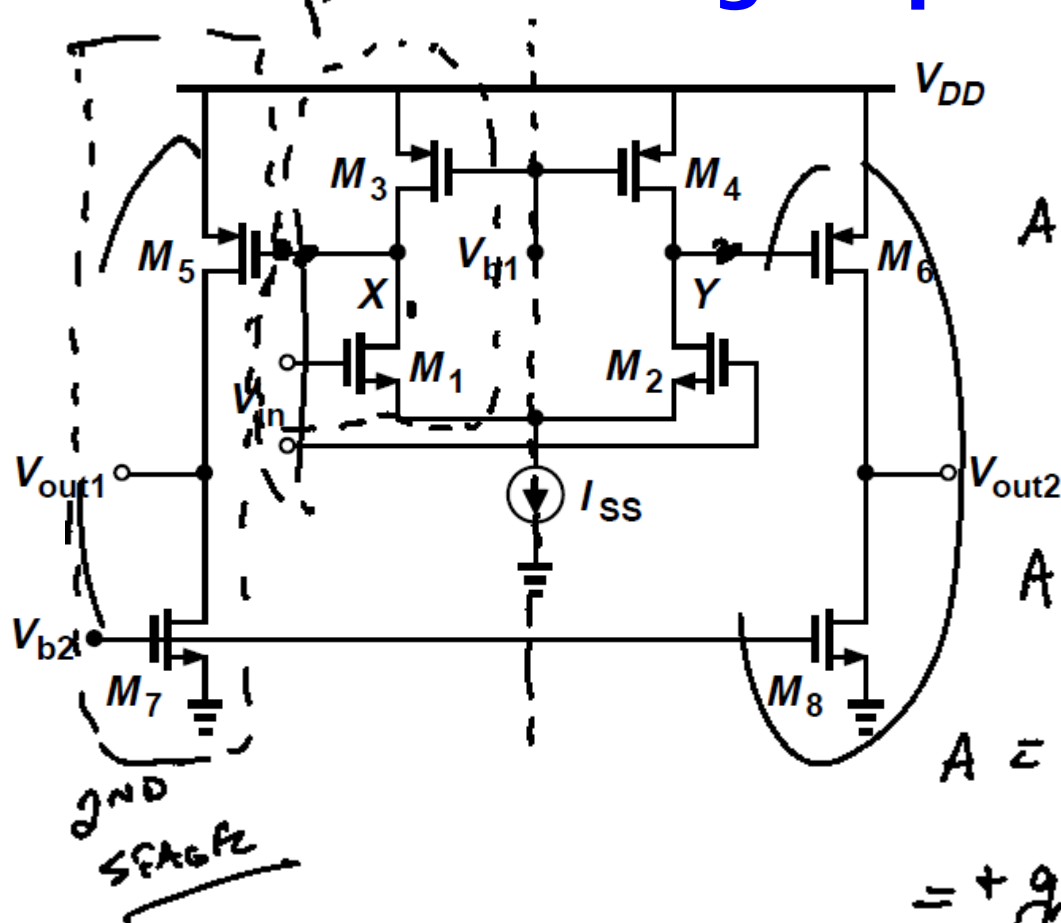

1st STAGE

$$A_{1st} \approx -g_{m1} \cdot (r_{o1} \parallel r_{o3})$$

2nd STAGE


$$A_{2nd} \approx -g_{m5} \cdot (r_{o7} \parallel r_{o5})$$

$$A \approx A_{1st} \cdot A_{2nd}$$

$$= +g_{m1} \cdot g_{m5} (r_{o3} \parallel r_{o1}) (r_{o5} \parallel r_{o7})$$

$$A \propto (g_m \cdot r_o)^2$$

Output Swing Two-Stage Op Amps

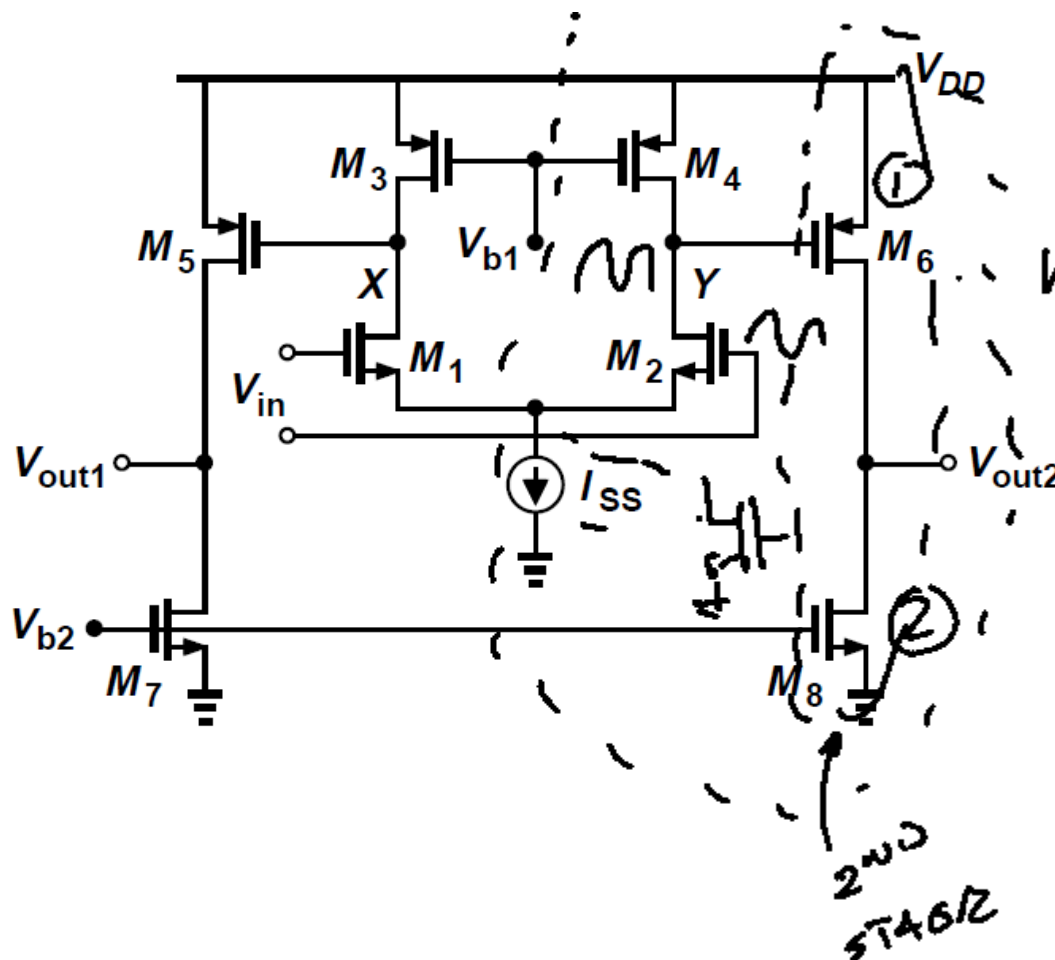

OUTPUT SWING 1ST STAGE
NOV EY

$$V_{out,MAX} = V_{DD} - 3V_{DSAT}$$


OUTPUT SWING 2ND STAGE

$$V_{out,MAX} = V_{DD} - 2V_{DSAT}$$

WHAT IS THE OVERALL HEADROOM?

ANS: 2ND STAGE \rightarrow 2ND STAGE SETS HEADROOM
BECAUSE OF GAIN IN 2ND STAGE

Bandwidth: Two-Stage Op Amps



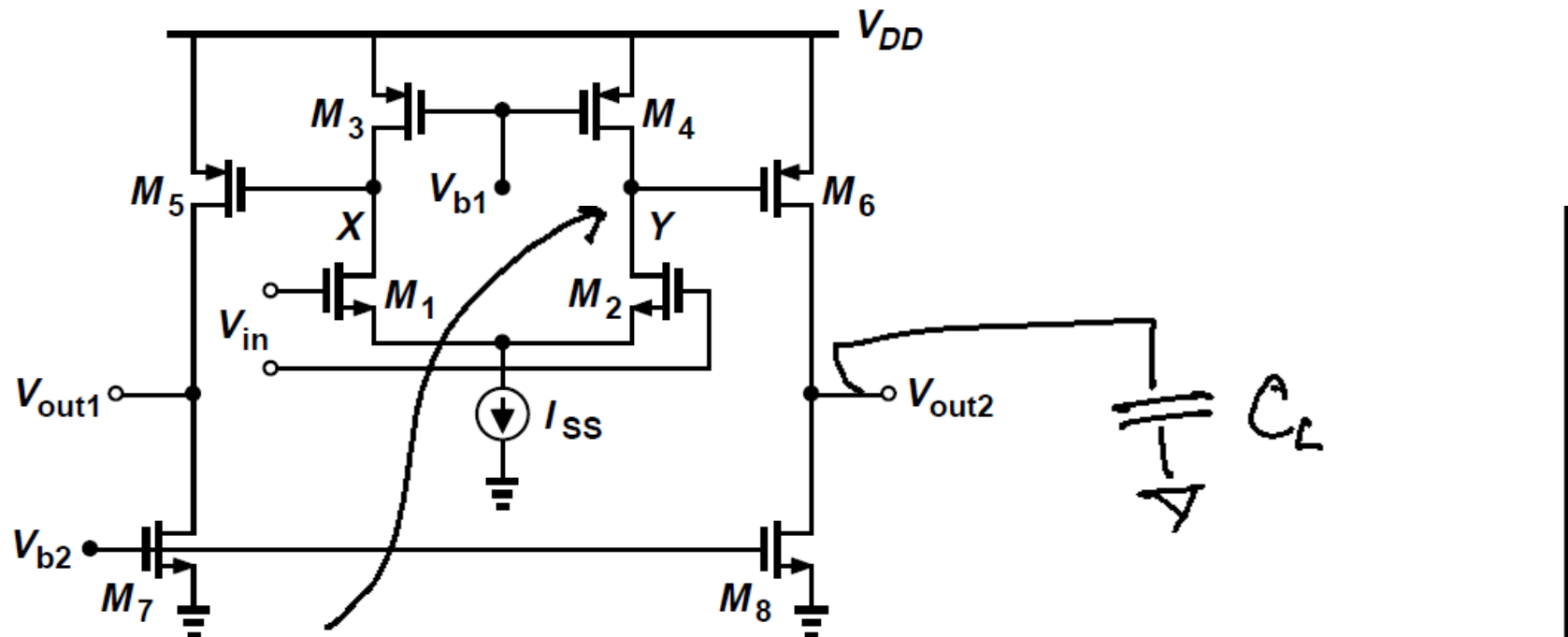


$$P_1 \approx \frac{1}{2\pi (f_{o4} // f_{o2}) (C_{DB4} + C_{DB2} + C_{G6})}$$

$$P_2 \approx \frac{1}{2\pi (f_{o6} // f_{o8}) (C_{DB6} + C_{DB8} + C_L)}$$


Two-Stage Op Amps

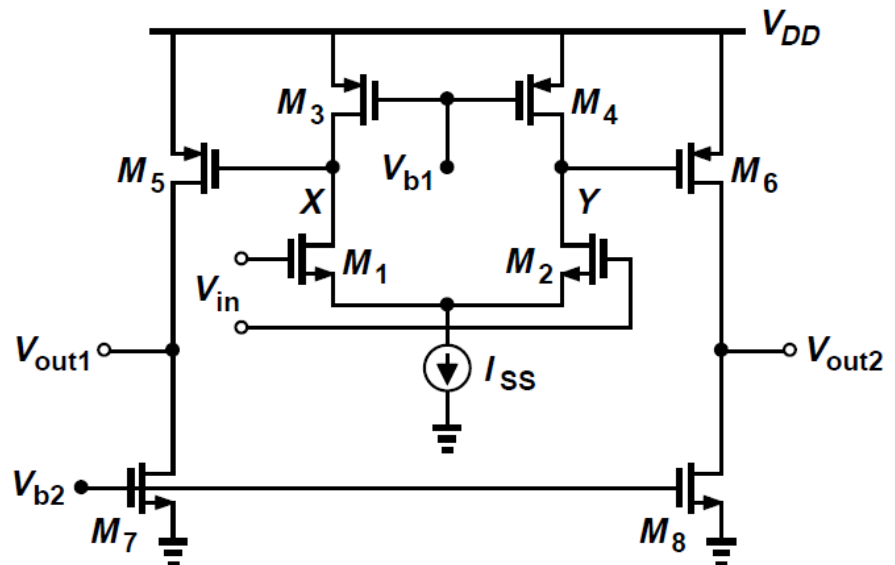  - Voltage headroom in today's design is constrained with low supply voltage and large output swing
- **Gain:** $g_{m1,2}(r_{O1,2} \parallel r_{O3,4}) \quad g_{m5,6}(r_{O5,6} \parallel r_{O7,8})$
- **Output Swing:** $V_{DD} - 2\text{Overdrive}$




Two-Stage Op Amps with cascode devices


- Voltage headroom in today's design is constrained with low supply voltage and large output swing
- **Gain:** $A_v \approx \{g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{O3,4}r_{O1,2}][[(g_{m5,6} + g_{mb5,6})r_{O5,6}r_{O7,8}]]\} \times [g_{m9,10}(r_{O9,10}||r_{O11,12})]$.
- Can we have more stages? Feedback stability limits

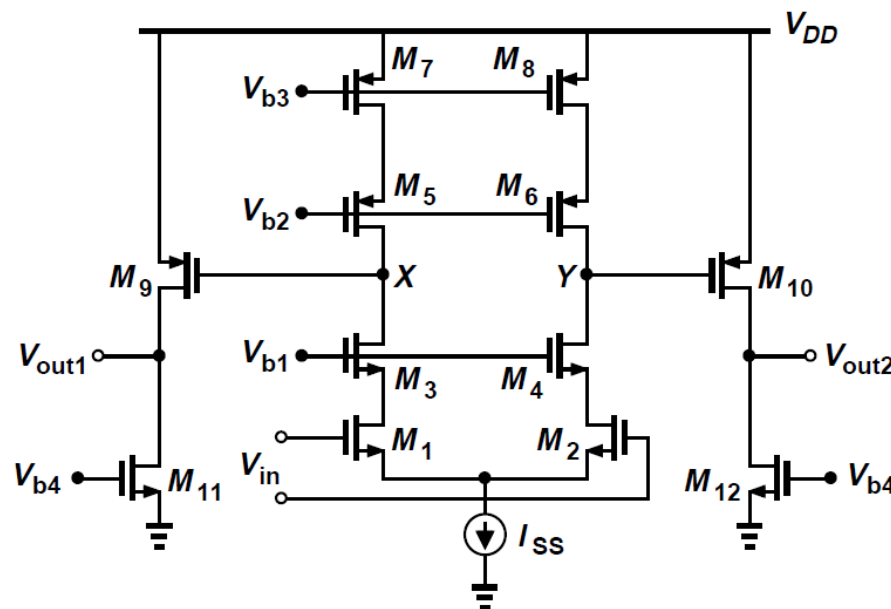


Gain Boosting Techniques: Effective

 


Output Resistance of Gain Boosting Stage

 


Output Resistance of Gain-Boosted Stage

 

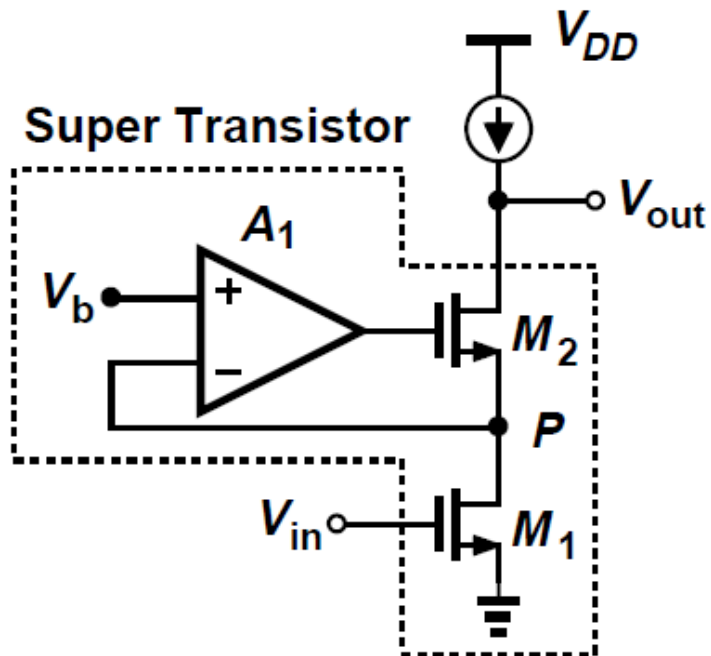Gain-boosting with Active/Regulated Cascode



Example Implementations

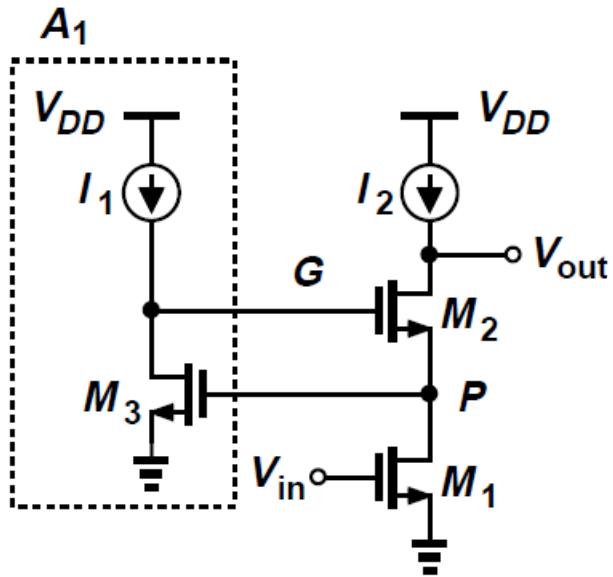


Gain Boosting Circuit Implementation


- Simplest a common-source stage

$$|V_{out}/V_{in}| \approx g_{m1}r_{O1}g_{m2}r_{O2}(g_{m3}r_{O3} + 1)$$

 
- Avoid headroom limitation, PMOS common-source stage is better, but M3 could go in triode
- Folded-cascode inserts one more stage



(a)

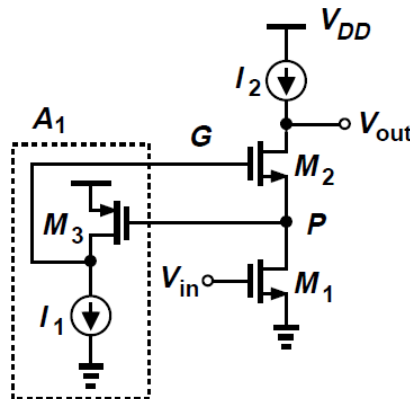


(b)

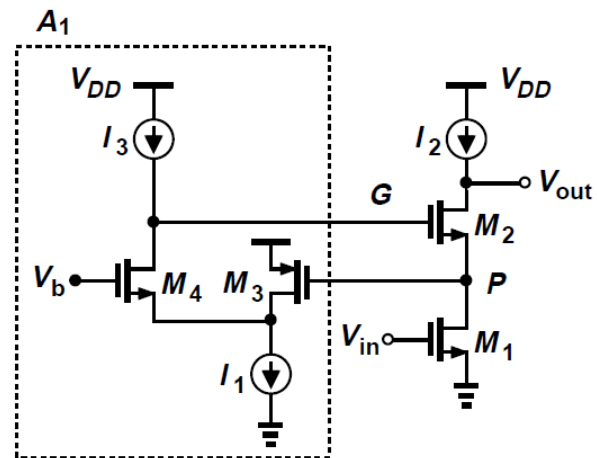


(c)

Scintillator

 


Detector

 


ADC / FPGA(Phase Electronics)



PET Readout Electronics

 

Decay Event

 


Image

 
Example from UW - PET Imaging Front-end

A Front-End Interface ASIC for SiPM based PET Imaging


Samrat Dey, *Student Member*, Thomas K. Lewellen, *Fellow*, Robert S. Miyaoka, *Senior Member*, and Jacques C. Rudell, *Senior Member, IEEE*




Gain Boosting with a Differential Pair

 

(a)

 

(b)

 

(c)

Gain Boosting in Signal Path and Load

- Gain boosting can be utilized in the load current source
- To allow maximum swings, A_2 employs NMOS-input.

