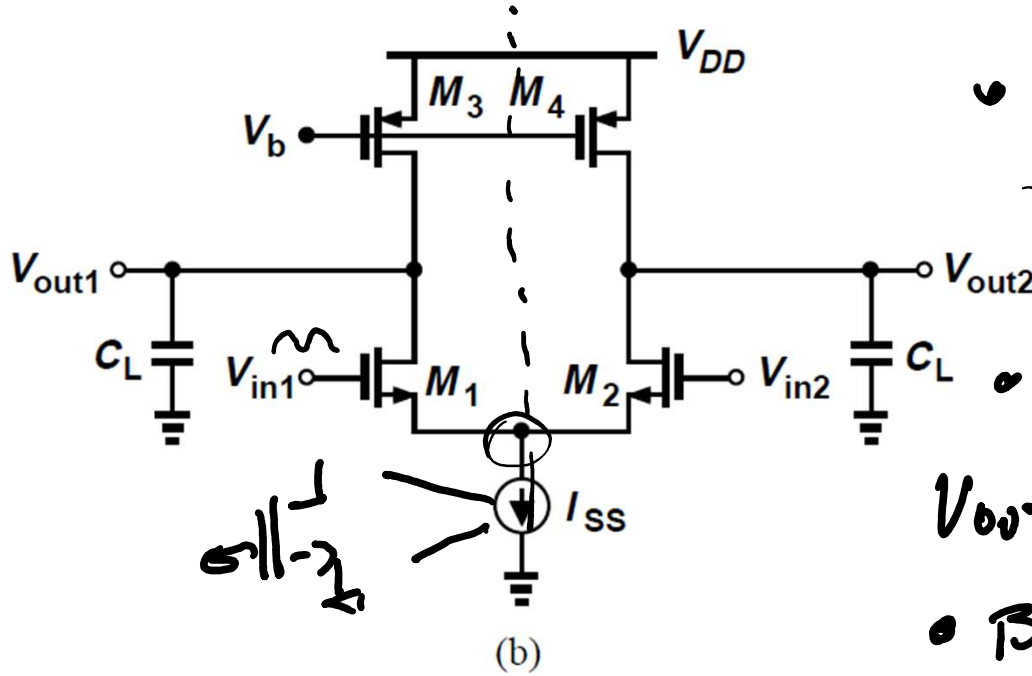


Lecture #15, Feb 11th, 2022

- We will bounce between chapters 8 (Feedback) and 9 (Op Amp design).
- CAD 4 now out.
- Quiz on Monday
- Project 1 Due Next week
- Project 2 coming soon.
- Today:
 - Continue with Op Amp Design
 - SIMPLE DIFF PAIR w/ ACTIVE.
 - TELESCOPIC OP AMP.
 - FOLDED CASCODE
 - ~~OP~~ 2-STAGE OP AMP
 - REGULATED CASCODES.

Output Swing (Headroom), BW and Gain



$$A_v = -g_{m1} \cdot (r_{o1} // r_{o3})$$



DECENT GAIN $10V \leq A_v \leq 100$

• OUTPUT SWING - E.G. HEADROOM

$$V_{out,MAX} = V_{DD} - 3 \cdot V_{DSAT}$$

• BW: ONE DOMINANT POLE
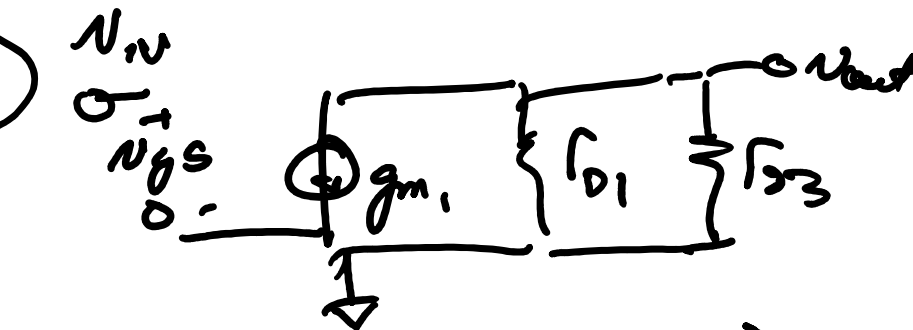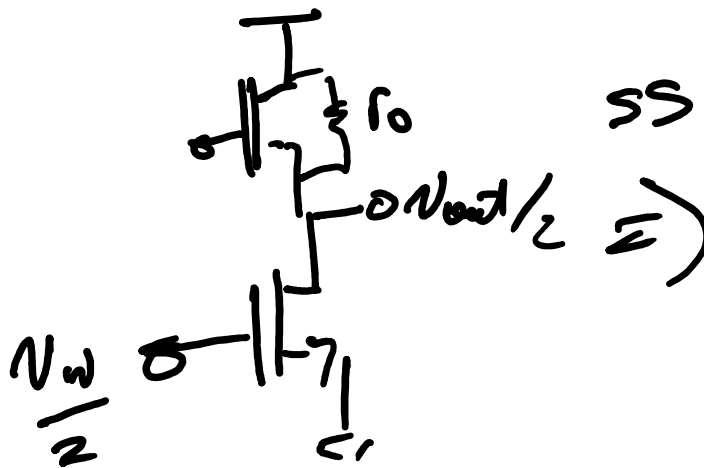
$$P_1 = \frac{1}{2\pi C_L \cdot (r_{o1} // r_{o3})}$$




$$A_v = -g_{m1} (r_{o1} // r_{o3})$$

VERY STABLE


One-Stage Op Amps


- Low-frequency gain:
- Bandwidth: usually proportional to $1/(C_L \cdot R_{out})$
- Output Swing (single-side): $V_{DD} - 3 \cdot V_{overdrive}$
- Mirror pole in single-ended circuit
- Power and noise: good, with four devices \rightarrow input noise

DIFF-TO-SINGLE ENDED AMP

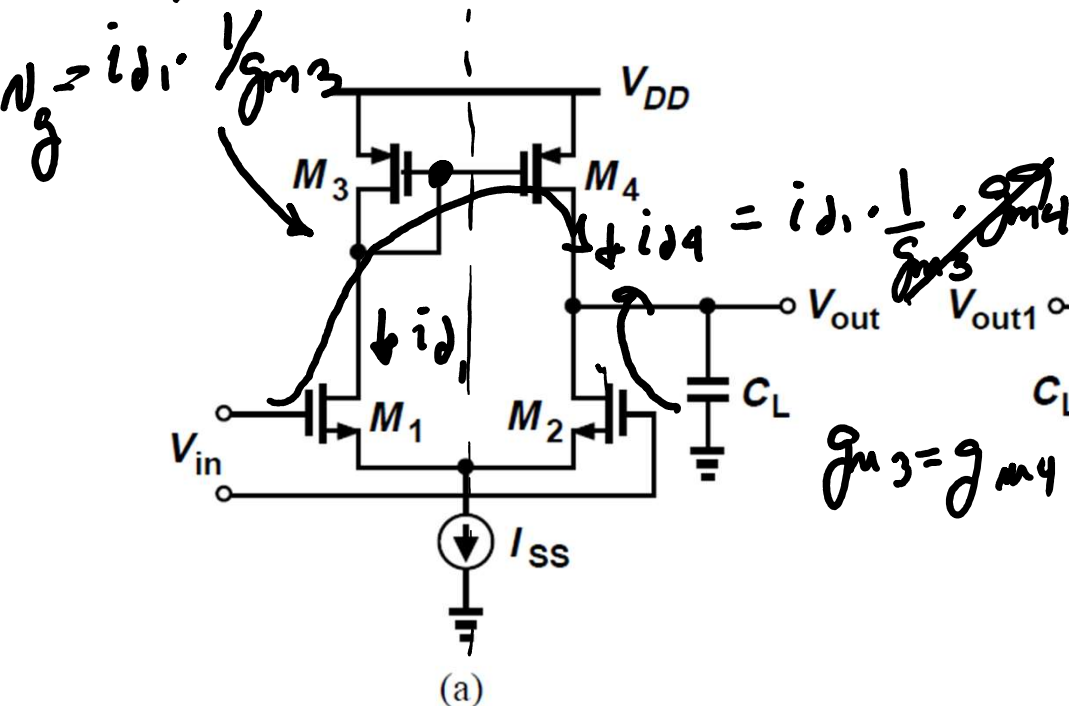


DIFF. AMP

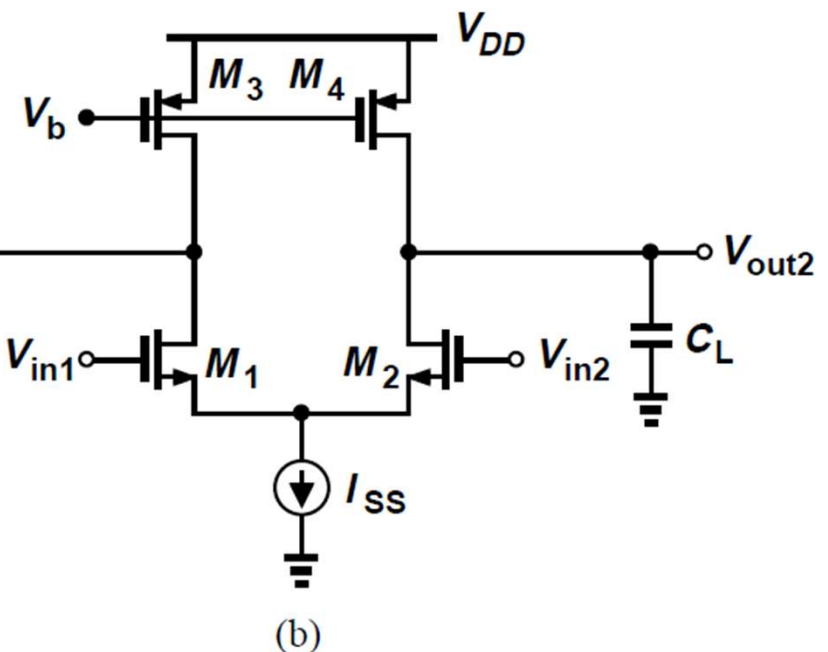


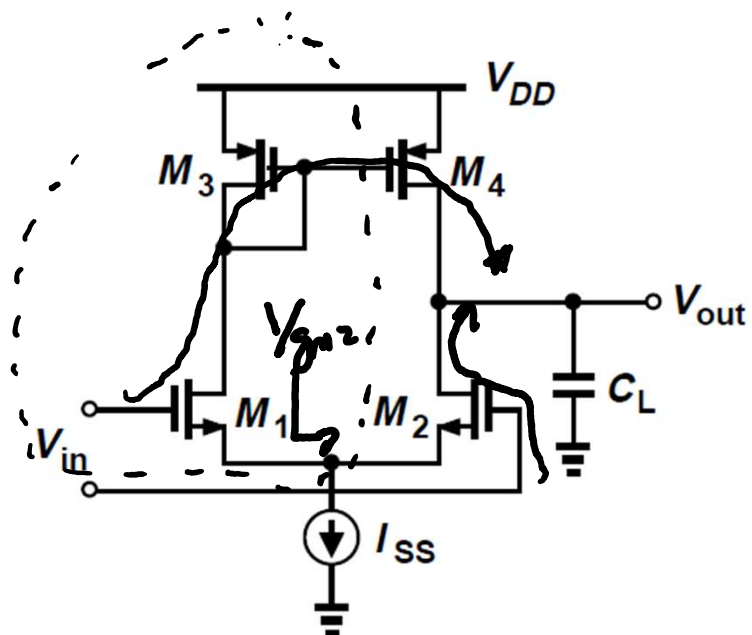

(a) LEFT GAIN

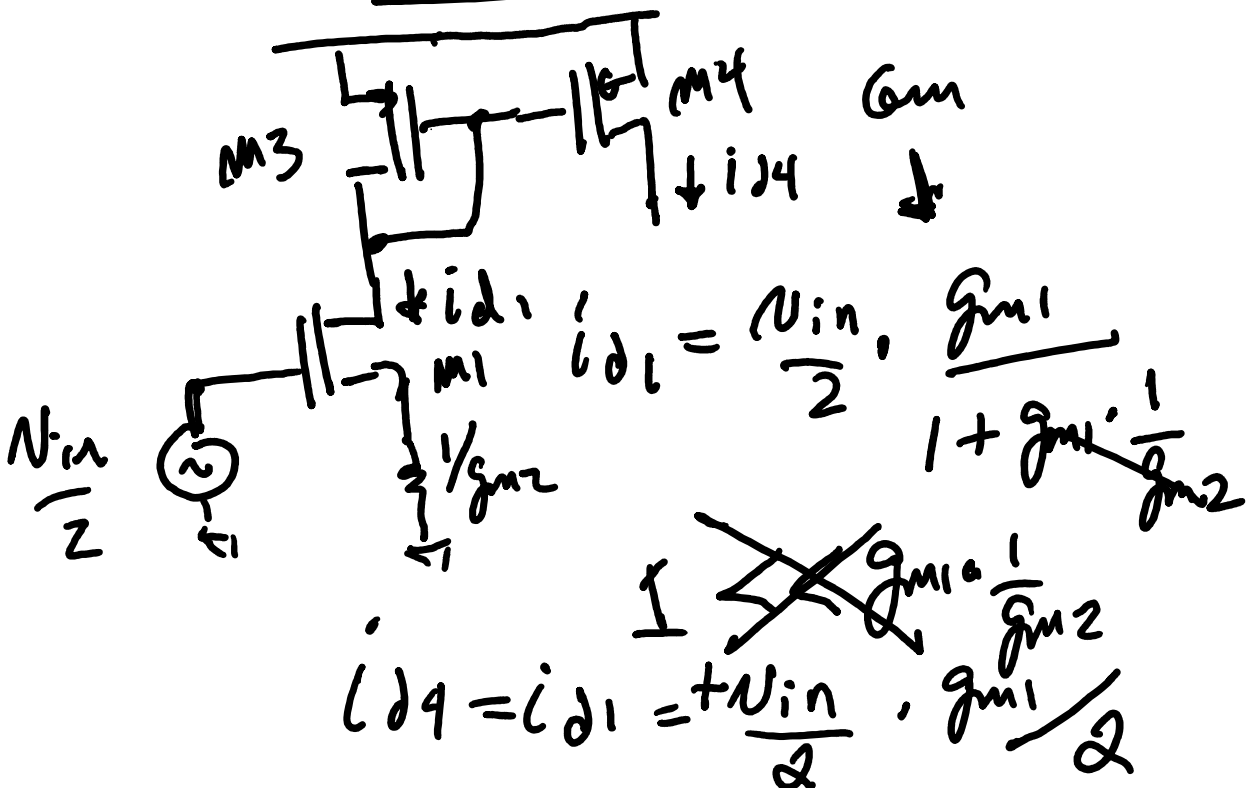


CS w/ RDEGGER

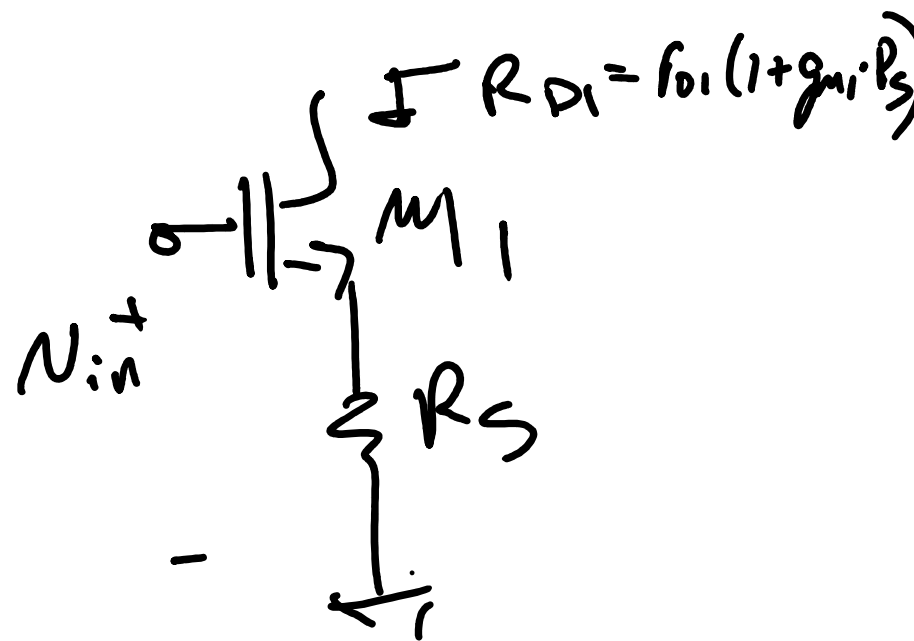


$$G_{m1} \approx \frac{1}{R_S}$$

$$G_{m1} = \frac{g_{m1}}{1 + g_{m1} \cdot R_S}$$
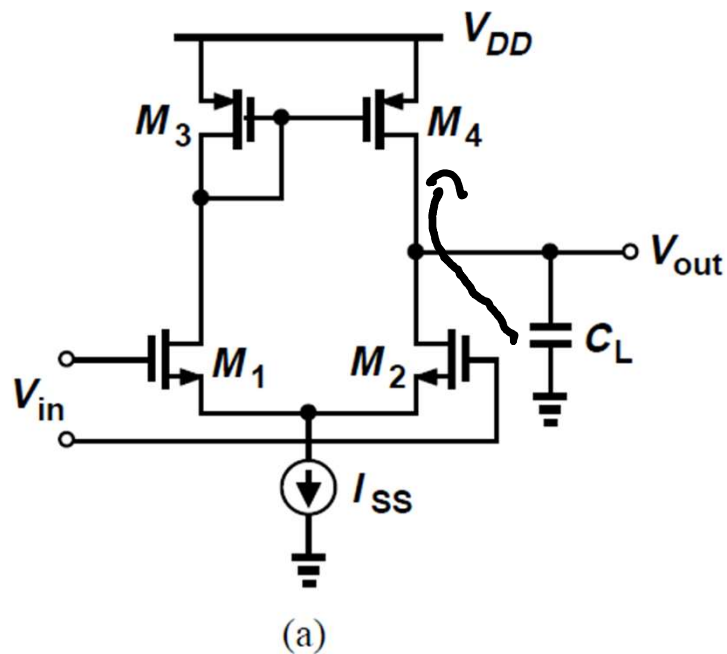
$$[1 \ll g_{m1} R_S] \Rightarrow G_{m1} = \frac{1}{R_S}$$



RIGHT SIDE

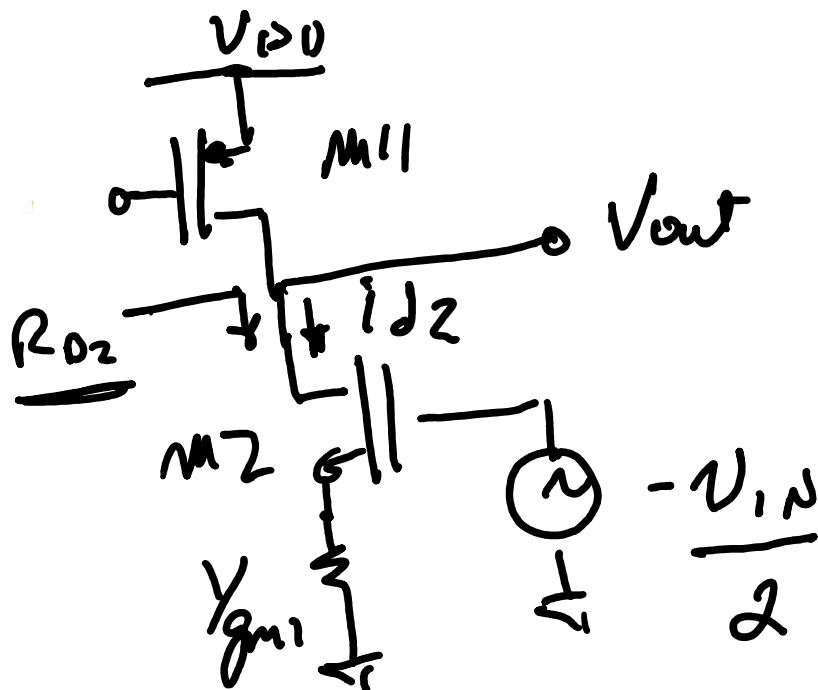


$$i_{d2} = - \left(-\frac{v_{in}}{2} \right) \cdot \frac{g_{m2}}{1 + g_{m2} \cdot \frac{1}{g_{m1}}}$$

$$= + \frac{v_{in}}{2} \cdot \frac{g_{m2}}{2}$$

$$R_{O2} = r_{o2} \left(1 + g_{m2} \cdot \frac{1}{g_{m1}} \right) = r_{o2} \cdot 2$$

$$V_{out} = (i_{d1} + i_{d2}) \cdot (r_{o4} // 2 r_{o2}) v_{in} \Rightarrow A_v = \frac{(g_{m1} + g_{m2}) \cdot (r_{o4} // 2 \cdot r_{o2})}{g_m \cdot (r_{o4} // 2 \cdot r_{o2})}$$

Telescopic Cascode Op Amps

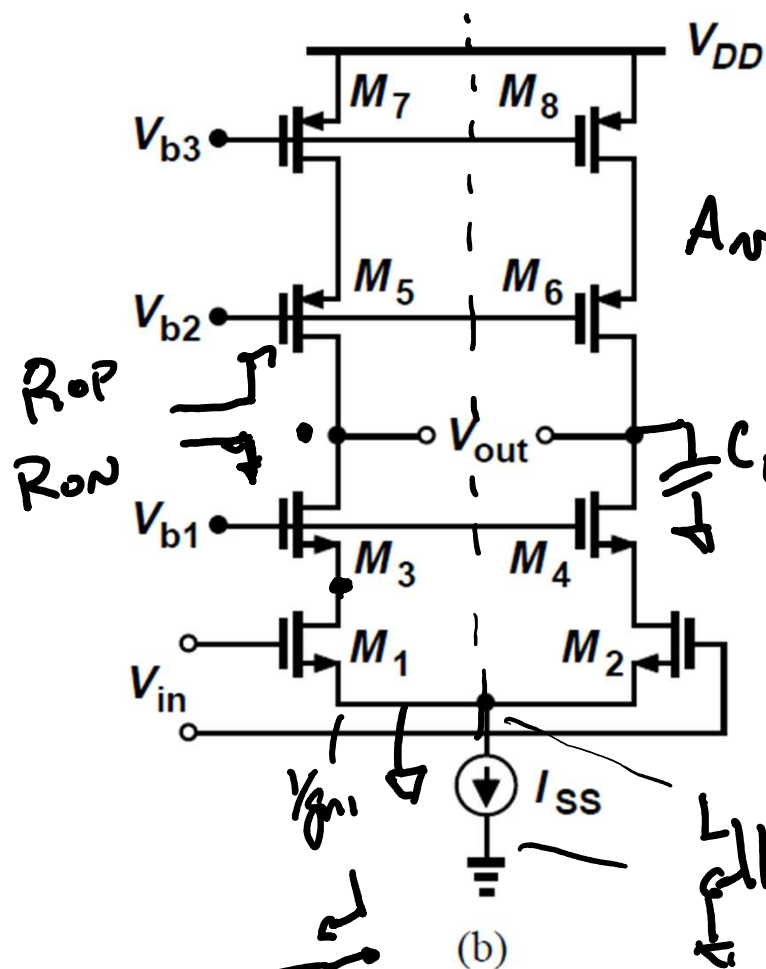

• VOLTAGE GAIN

$$A_v = -g_{m1} \cdot \underbrace{(g_{m3} \cdot r_{o3} \cdot r_{o1} // g_{m5} \cdot r_{o5} \cdot r_{o7})}_{\text{INTRINSIC (10-100)}}$$

C_L • OUTPUT SWING

$$V_{out, MAX} = V_{DD} - 5 V_{DSAT} \quad ; \quad \text{POOR OUT PUT SWING}$$

($V_{b3} - V_{th}$)

• BW

$$P = \frac{1}{2\pi (R_{ON} // R_{OP}) \cdot C_L}$$

DOMINATE POLES
STABLE

