



Kevin Egedy

Unless otherwise stated, in the following problems, use the device data shown in Table 2.1 and assume that $V_{DD} = 3$ V where necessary. All device dimensions are effective values and in microns.


Table 2.1 Level 1 SPICE models for NMOS and PMOS devices.

NMOS Model			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = $9e+14$	LD = $0.08e-6$	UO = 350	LAMBDA = 0.1
TOX = $9e-9$	PB = 0.9	CJ = $0.56e-3$	CJSW = $0.35e-11$
MJ = 0.45	MJSW = 0.2	CGDO = $0.4e-9$	JS = $1.0e-8$
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = $5e+14$	LD = $0.09e-6$	UO = 100	LAMBDA = 0.2
TOX = $9e-9$	PB = 0.9	CJ = $0.94e-3$	CJSW = $0.32e-11$
MJ = 0.5	MJSW = 0.3	CGDO = $0.3e-9$	JS = $0.5e-8$

- 3.1. For the circuit of Fig. 3.13, calculate the small-signal voltage gain if $(W/L)_1 = 50/0.5$, $(W/L)_2 = 10/0.5$, and $I_{D1} = I_{D2} = 0.5$ mA. What is the gain if M_2 is implemented as a diode-connected PMOS device (Fig. 3.16)?

  **Figure 3.13** CS stage with diode-connected load.**Figure 3.16** CS stage with diode-connected PMOS device.

- 3.2. In the circuit of Fig. 3.18, assume that $(W/L)_1 = 50/0.5$, $(W/L)_2 = 50/2$, and $I_{D1} = I_{D2} = 0.5$ mA when both devices are in saturation. Recall that $\lambda \propto 1/L$.
- Calculate the small-signal voltage gain.
 - Calculate the maximum output voltage swing while both devices are saturated.

 **Figure 3.18** CS stage with current-source load.

- 3.3. In the circuit of Fig. 3.4(a), assume that $(W/L)_1 = 50/0.5$, $R_D = 2$ k Ω , and $\lambda = 0$.
- What is the small-signal gain if M_1 is in saturation and $I_D = 1$ mA?
 - What input voltage places M_1 at the edge of the triode region? What is the small-signal gain under this condition?
 - What input voltage drives M_1 into the triode region by 50 mV? What is the small-signal gain under this condition?

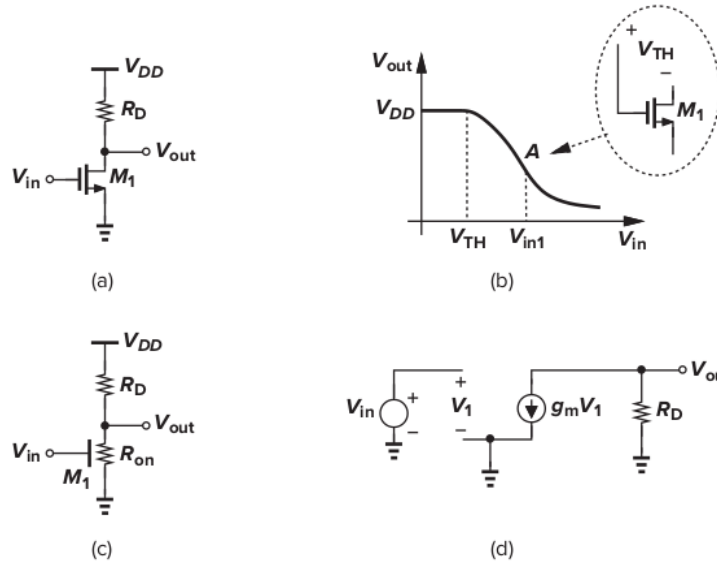


Figure 3.4 (a) Common-source stage, (b) input-output characteristic, (c) equivalent circuit in the deep triode region, and (d) small-signal model for the saturation region.

3.20. Assuming all MOSFETs are in saturation, calculate the small-signal voltage gain of each circuit in Fig. 3.83 ($\lambda \neq 0$, $\gamma = 0$).

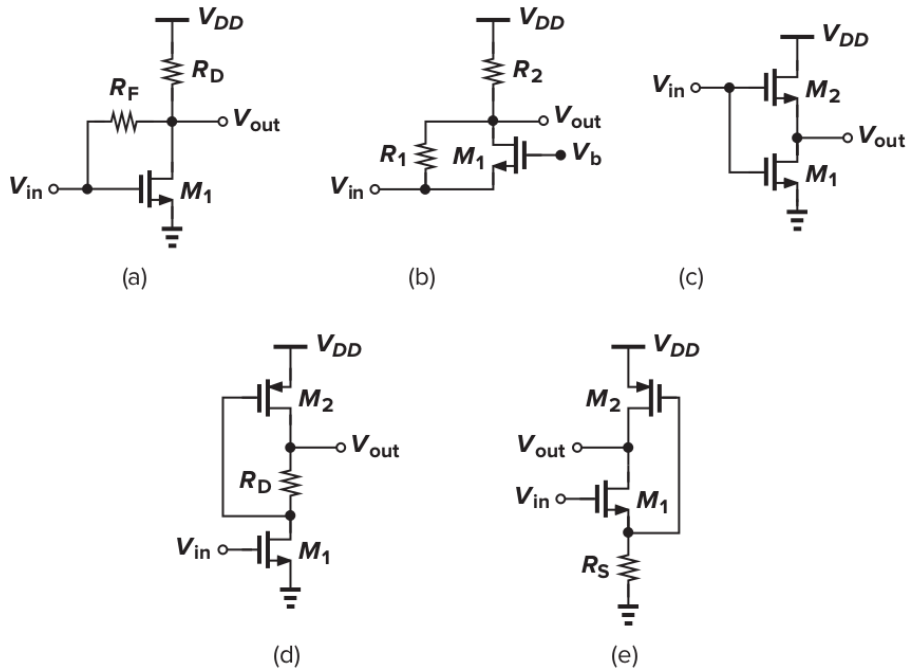


Figure 3.83

3.27. A source follower can operate as a level shifter. Suppose the circuit of Fig. 3.37(b) is designed to shift the voltage level by 1 V, i.e., $V_{in} - V_{out} = 1$ V.

- (a) Calculate the dimensions of M_1 and M_2 if $I_{D1} = I_{D2} = 0.5$ mA, $V_{GS2} - V_{GS1} = 0.5$ V, and $\lambda = \gamma = 0$.
 (b) Repeat part (a) if $\gamma = 0.45$ V⁻¹ and $V_{in} = 2.5$ V. What is the minimum input voltage for which M_2 remains saturated?

 


Figure 3.37 Source follower using (a) an ideal current source, and (b) an NMOS transistor as a current source.

3.32. In the circuit shown in Fig. 3.86, prove that

$$\frac{V_{out1}}{V_{out2}} = \frac{-R_D}{R_S} \quad (3.148)$$

where V_{out1} and V_{out2} are small-signal quantities and $\lambda, \gamma > 0$.

 


Figure 3.86

3.34. Calculate the voltage gain of a source follower using the lemma $A_v = -G_m R_{out}$. Assume that the circuit drives a load resistance of R_L and $\lambda, \gamma > 0$.