

Name:

50 points total

EE 473


Quiz 1

Winter 2022

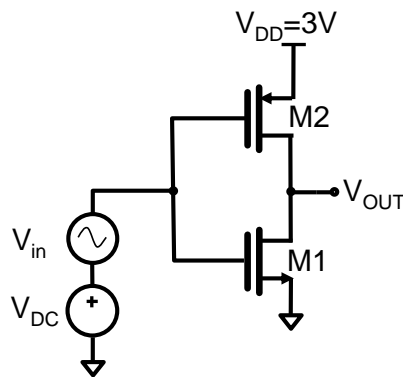- 1) Assume that M1 and M2 are in the saturation region and that V_{DC} is set to produce a DC V_{OUT} which is optimal for maximum headroom and output voltage swing. Also, assume that the drain currents of M1 and M2 are $I_D = 0.5\text{mA}$ (Total: 25 points)

Device characteristics: $\mu_n C_{ox} = 4\text{mA/V}^2$, $\mu_p C_{ox} = 2\text{mA/V}^2$

$(W/L)_{M1} = (10\mu\text{m}/0.5\mu\text{m})$, and $(W/L)_{M2} = (20\mu\text{m}/0.5\mu\text{m})$, $\lambda_p = \lambda_n = 0.1\text{V}^{-1}$ and $V_{THn} = 0.7\text{V}$ and $V_{THp} = 0.8\text{V}$.



- a) What is the small-signal gain $A_v = \frac{V_{OUT}}{V_{in}}$? (15 points)
- b) What is the optimal DC value of V_{OUT} to produce a maximum peak-to-peak output swing? This question is **not** asking you to compute V_{OUT} DC using the drain current equations for M1 and M2, but rather find the optimal V_{OUT} DC given the $(V_{GS} - V_{TH})$ of M1 and M2. (5 points) What is the corresponding peak output swing? (5 points)

- 2) For the below single-transistor amplifier, both an ideal DC current source and ideal AC current are applied to the input. It is fair to assume M_1 is in the saturation region and behaves like a “square law” device. Find the DC value of V_{OUT} (5 points) – note: ignore the body effect ($\lambda=0$) to make the calculation of the DC bias easier. Next, draw the small signal circuit for this amplifier and derive an expression for the small-signal AC transresistance (v_{out}/i_{in}), state any assumptions made to get your answer. Lastly, compute the value of the transresistance. (20 points) Note: for the AC-SS analysis you cannot ignore the body effect – e.g. $\lambda=0.01V^{-1}$
- Device characteristics: $\mu_n C_{ox} = 5mA/V^2$, $(W/L)_{M1} = (10\mu m/1\mu m)$, $\lambda=0.01V^{-1}$ and $V_t=0.7V$.

